

EEEN 322

Communication Engineering

İpek Şen
Spring 2019

Week 6


Modulation - Demodulation Circuits for Amplitude Modulation (DSB+C)

- **Modulation:**
 - All the modulators that are used for DSB-SC can also be used here
However: Since the carrier is not suppressed, there is no need to use balanced modulators; we may use a simple switching modulator with a single diode
- **Demodulation**
 - If $\mu > 1$: Coherent demodulation is a must. Then, use a demodulator that you use for DSB-SC
 - If $\mu \leq 1$: Simpler demodulators are better, such as
 - Rectifier detector
 - Envelope detector

Switching Modulator for Amplitude Modulation (DSB+C)

→ Switching action of diode is controlled by
 $c \cos \omega_c t$

$$c \gg m(t)$$

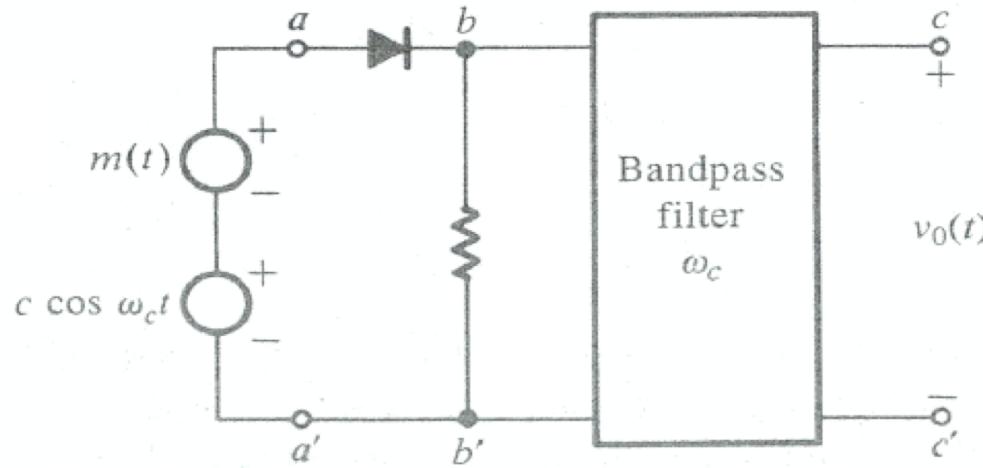

$$v_{bb'}(t) = [c \cos \omega_c t + m(t)] w(t)$$





$$\Rightarrow v_{bb'}(t) = [c \cos \omega_c t + m(t)] \left[\frac{1}{2} + \frac{2}{\pi} \left(\cos \omega_c t - \frac{1}{3} \cos 3\omega_c t + \frac{1}{5} \cos 5\omega_c t - \dots \right) \right]$$


$$\Rightarrow v_{bb'}(t) = \underbrace{\left[\frac{c}{2} + \frac{2}{\pi} m(t) \right] \cos \omega_c t}_{\text{AM signal}} + \text{other_terms}$$

Filtered out by BPF



Signal Rectification

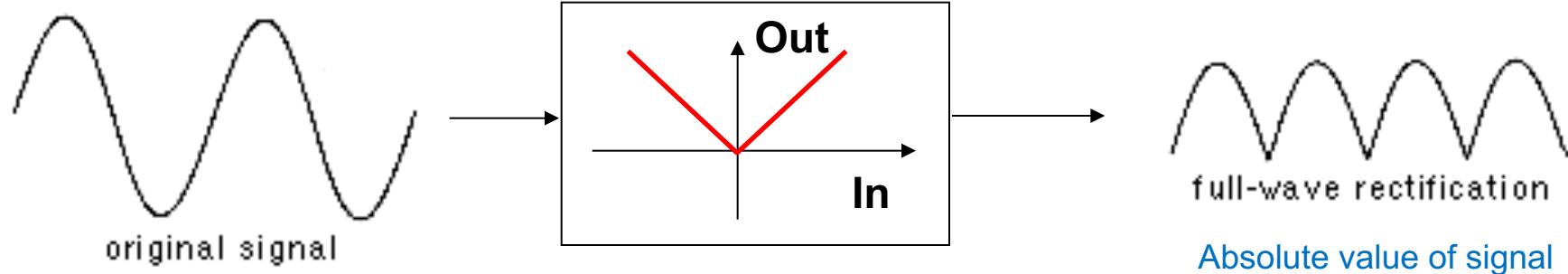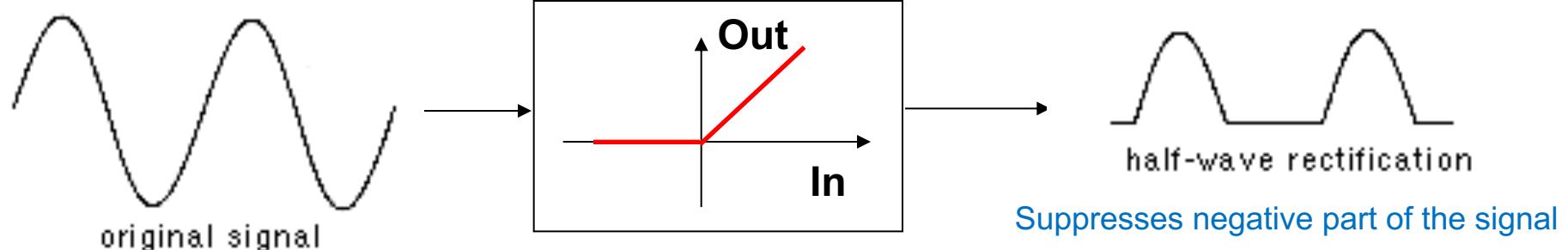

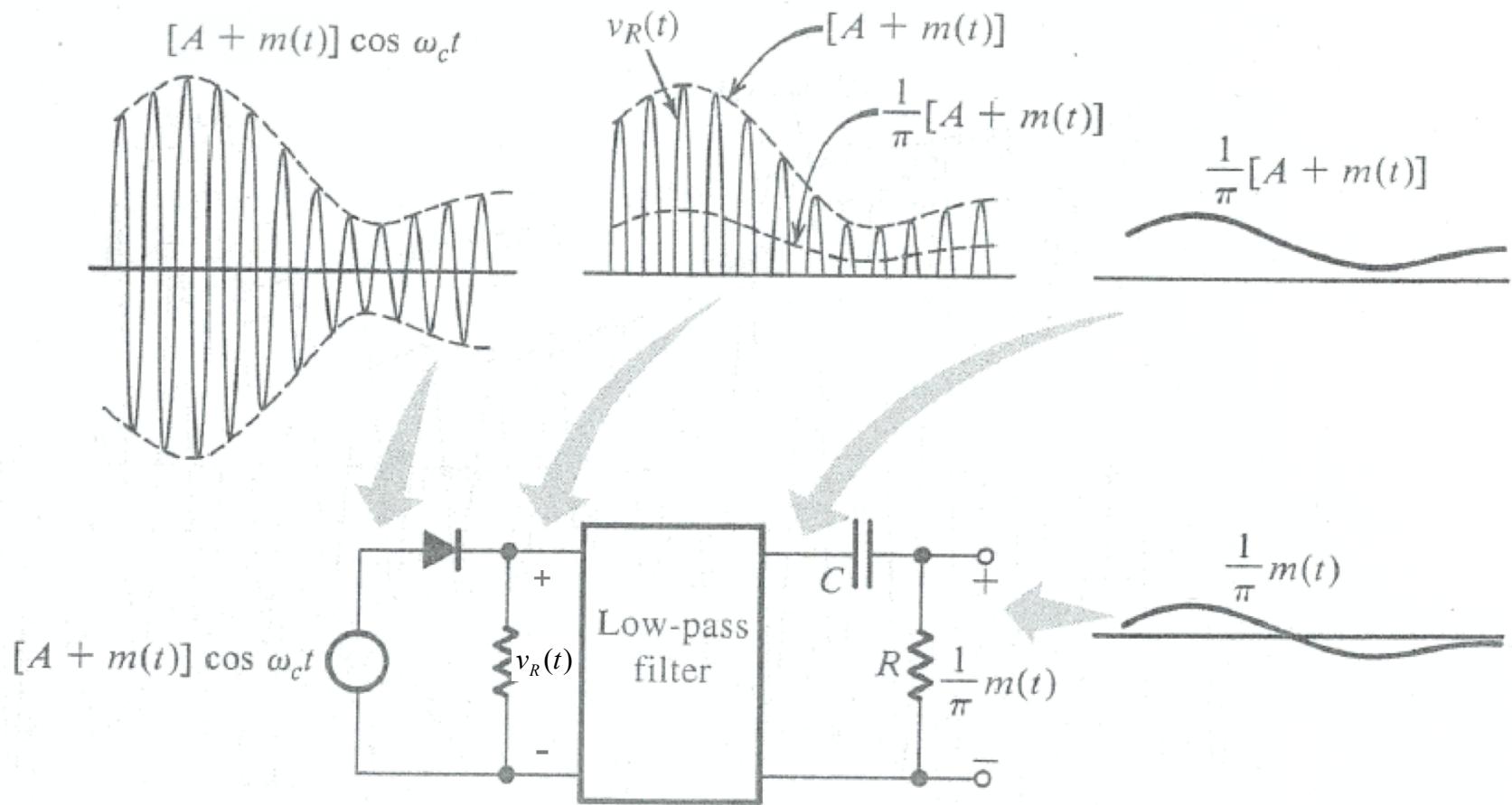Demodulation of AM Signals: Rectifier Detector



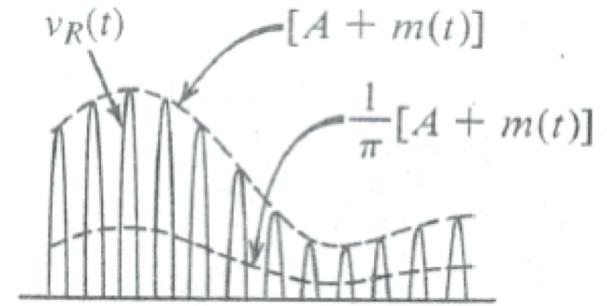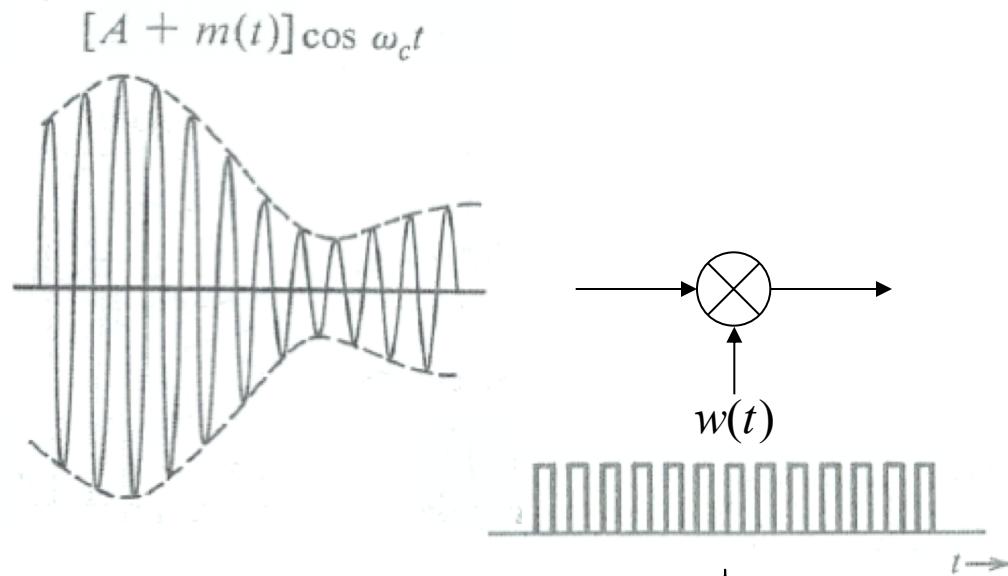Demodulation of AM Signals: Rectifier Detector (cont'd)





$$v_R(t) = [A + m(t)]\cos \omega_c t \left[\frac{1}{2} + \frac{2}{\pi} \left(\cos \omega_c t - \frac{1}{3} \cos 3\omega_c t + \frac{1}{5} \cos 5\omega_c t - \dots \right) \right]$$

$$\Rightarrow v_R(t) = \underbrace{\frac{1}{2}[A + m(t)]\cos \omega_c t}_{\frac{1}{2}[1 + \cos 2\omega_c t]} + \underbrace{\frac{2}{\pi}[A + m(t)]\cos^2 \omega_c t}_{\frac{1}{2}[1 + \cos 2\omega_c t]} + \text{other_terms}$$

$$\Rightarrow v_R(t) = \underbrace{\frac{1}{2}[A + m(t)]\cos \omega_c t}_{\text{Filtered out by LPF}} + \underbrace{\frac{1}{\pi}[A + m(t)]}_{\text{Desired part}} + \underbrace{\frac{1}{\pi}[A + m(t)]\cos 2\omega_c t}_{\text{Filtered out by LPF}} + \text{other_terms}$$

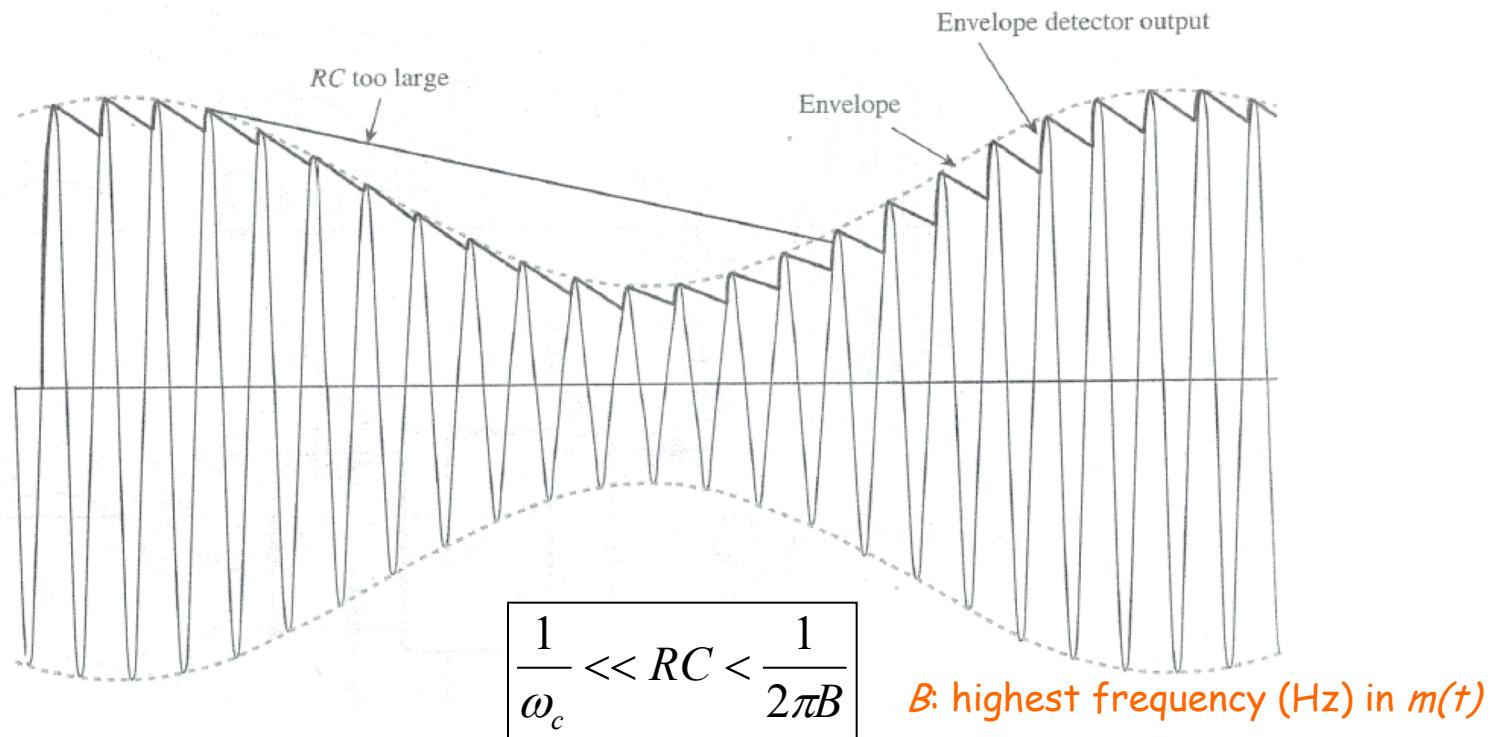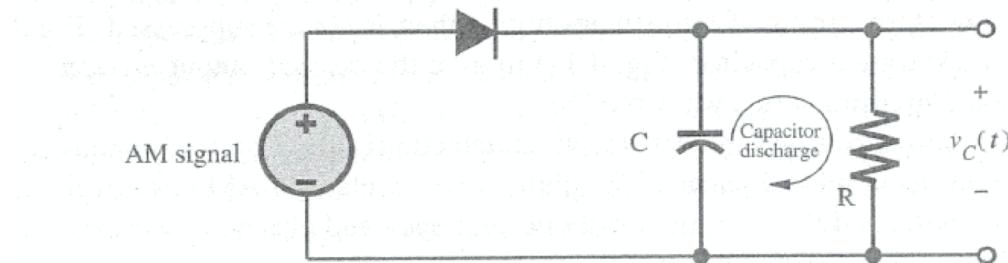Demodulation of AM Signals: Envelope Detector




don't discharge the
capacitor too fast
w.r.t. carrier

↑ be fast enough to
track the envelope

Up to now...

	Suppressed Carrier	With Carrier
Double Sideband (DSB)	DSB-SC	DSB+C (a.k.a. AM)
Single Sideband (SSB)	SSB-SC	SSB+C
Vestigial Sideband (VSB)	VSB-SC	VSB+C

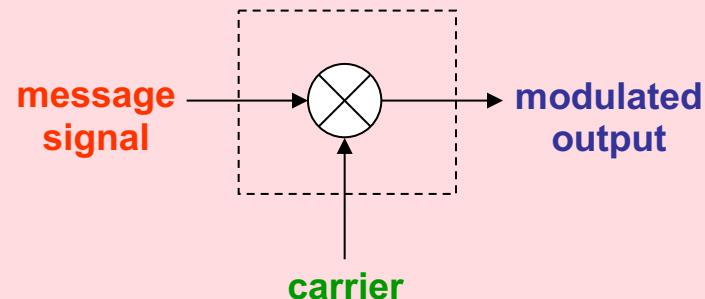In general: The **amplitude** of the **carrier** is changed by the **message signal**



$$\varphi_{DSB-SC}(t) = m(t) \cos \omega_c t$$

Multiplier, nonlinear, switching modulator; coherent demodulator

$$\varphi_{AM}(t) = [A + m(t)] \cos \omega_c t$$

Same modulators and demodulator as in DSB-SC work here also BUT: Simpler modulator (single-diode switching) and simpler demodulator (envelope detector, rectifier detector) also work

$$\mu = \frac{m_p}{A}$$


Condition for envelope detection:
 $A \geq m_p$ or $0 \leq \mu \leq 1$

Sending Two Signals at the Same Time by Using the Same Carrier Frequency: Quadrature Amplitude Modulation (QAM)

$$\varphi_{QAM}(t) = m_1(t) \cos \omega_c t + m_2(t) \sin \omega_c t$$

- **Modulation:**
 - Any modulator you use for DSB-SC
 - Multiply $m_1(t)$ by $\cos \omega_c t$ and $m_2(t)$ by $\sin \omega_c t$
- **Demodulation:**
 - Coherent demodulation (the method you use for DSB-SC)
 - Multiply the modulated signal by $\cos \omega_c t$ to obtain $m_1(t)$ and by $\sin \omega_c t$ to obtain $m_2(t)$
- Used in color TV to multiplex the chrominance signals
- A slight error in the frequency or phase of the carrier at the demodulator results in
 - Loss and distortion of signals
 - Interference between the two channels (co-channel interference)

Modulation and Demodulation for QAM

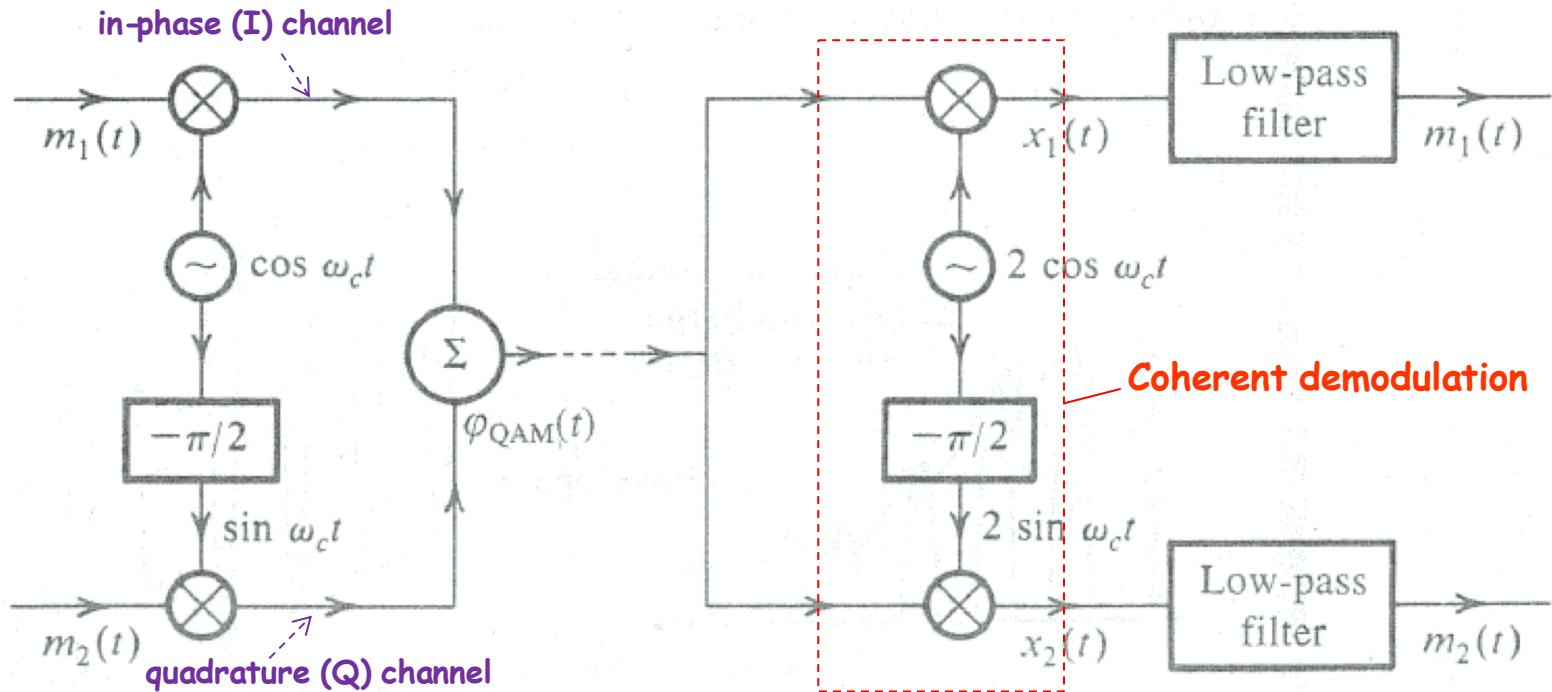

$$\varphi_{QAM}(t) = m_1(t) \cos \omega_c t + m_2(t) \sin \omega_c t$$

$$x_1(t) = 2\varphi_{QAM}(t) \cos \omega_c t = 2[m_1(t) \cos \omega_c t + m_2(t) \sin \omega_c t] \cos \omega_c t = 2[m_1(t) \cos^2 \omega_c t + m_2(t) \cos \omega_c t \sin \omega_c t]$$

$$= m_1(t)(1 + \cos 2\omega_c t) + m_2(t) \sin 2\omega_c t$$

$$= m_1(t) + \underline{m_1(t) \cos 2\omega_c t} + m_2(t) \sin 2\omega_c t$$

$$x_2(t) = 2\varphi_{QAM}(t) \sin \omega_c t = 2[m_1(t) \cos \omega_c t + m_2(t) \sin \omega_c t] \sin \omega_c t = 2[m_1(t) \cos \omega_c t \sin \omega_c t + m_2(t) \sin^2 \omega_c t]$$

$$= m_1(t) \sin 2\omega_c t + m_2(t)(1 - \cos 2\omega_c t)$$

$$= m_2(t) + \underline{m_1(t) \sin 2\omega_c t} - m_2(t) \cos 2\omega_c t$$

Will be
filtered
out by
the LPF