

EEEN 222 / COMP 211
Digital Systems Design

MIDTERM EXAM, Spring 2014-2015

Duration: 100 minutes

Problem 1 (25 points)

Consider a general Boolean algebra which can be defined with more than two elements other than 0 and 1. Given that $A \cdot B = 0$ and $A + B = 1$, use axiom(s) and/or theorems of general Boolean algebra to prove the following identity

$$(A + C) \cdot (A' + B) \cdot (B + C) = B \cdot C$$

(Hint: Note that A , B , and C do not necessarily have to be 0 or 1).

Problem 2 (25 points)

Given the following Boolean function:

$$F(A, B, C, D) = \sum m(1, 2, 9, 10, 13, 14, 15) + d(5, 7, 8)$$

- Simplify the function $F(A, B, C, D)$ using Quine-McCluskey tabulation method. Show all the tables that you use. (9 pts.)
- Implement the simplified expression using NOR gates. (8 pts.)
- Implement the simplified expression using NAND gates. (8 pts.)

Problem 3 (25 points)

Consider a combinational circuit that accepts a 4-bit binary number and generates an output 1 if the number of 1s in the 4-bit binary number is even and yields an output 0 if the number of 1s in the 4-bit binary number is odd.

- Simplify the output Boolean function f using Karnaugh map approach.
- Draw the corresponding circuit diagram as a 2-level NOR gate logic circuit.

Problem 4 (25 points)

Given the following Boolean function:

$$F(A, B, C) = A'B + B'C + A'BC'$$

- Implement $F(A, B, C)$ using a 3×8 decoder and any simple logic gate if necessary. (7 pts.)
- Implement $F(A, B, C)$ using an 8-to-1 multiplexer and any simple logic gate if necessary. (9 pts.)
- Implement $F(A, B, C)$ using a single 4-to-1 multiplexer and any simple logic gate if necessary. (9 pts.)

EEEN 222 Midterm Exam
Solution Key

Problem 1) We have

$$A \cdot B = 0$$

$$A + B = 1$$

then we find that

$$\begin{aligned}(A+C) \cdot (A'+B) \cdot (B+C) &= (A+C) \cdot (B+C) \cdot (A'+B) && (05) \\&= (A \cdot B + C) \cdot 1 \cdot (A'+B) && (05) \\&= (0+C) \cdot (A+B) \cdot (A'+B) && (05) \\&= C \cdot (A \cdot A' + B) && (05) \\&= C \cdot (0+B) && (05) \\&= CB \\&= BC\end{aligned}$$

$$2) F(A, B, C, D) = \sum m(1, 2, 9, 10, 13, 14, 15)$$

$$d(A, B, C, D) = \sum m(5, 7, 8)$$

List 1

m_i	A	B	C	D	
1	0	0	0	1	✓
2	0	0	1	0	✓
8	1	0	0	0	✓
5	0	1	0	1	✓
9	1	0	0	1	✓
10	1	0	1	0	✓
7	0	1	1	1	✓
13	1	1	0	1	✓
14	1	1	1	0	✓
15	1	1	1	1	✓

List 2

Product terms	A	B	C	D	
(1, 5)	0	-	0	1	✓
(1, 9)	-	0	0	1	✓
(2, 10)	-	0	1	0	PI 7
(8, 9)	1	0	0	-	PI 6
(8, 10)	1	0	-	0	PI 5
(5, 7)	0	1	-	1	✓
(5, 13)	-	1	0	1	✓
(9, 13)	1	-	0	1	✓
(10, 14)	1	-	1	0	PI 4
(7, 15)	-	1	1	1	✓
(13, 15)	1	1	-	1	✓
(14, 15)	1	1	1	-	PI 3

List 3

Product terms	A	B	C	D	
(1, 5), (9, 13)	-	-	0	1	PI 1 = C'D
(1, 9), (5, 13)	-	-	0	1	
(5, 7), (13, 15)	-	1	-	1	PI 2 = BD
(5, 13), (7, 15)	-	1	-	1	

Problem 3)

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

(2.5)

$$F(A, B, C, D) = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$$

Q.

AB \ CD	CD			
	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

(05)

$$F(A, B, C, D) = A'B'C'D' + A'B'CD + A'BC'D + A'BCD' + ABC'D' + ABCD + AB'C'D + AB'CD'$$

(05)

b. We consider sum of minterms representation for $F'(A, B, C, D)$ as follows

$$F'(A, B, C, D) = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$


AB \ CD	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

$$F'(A, B, C, D) = A'B'C'D + A'B'CD' + A'BC'D' + A'BCD + ABC'D + ABCD' + AB'C'D' + AB'CD$$

(25)

$$\Rightarrow [F'(A, B, C, D)]' = F(A, B, C, D) = (A+B+C+D') \cdot (A+B+C'+D) \cdot (A+B'+C+D) \cdot (A+B'+C'+D') \cdot (A'+B'+C+D') \cdot (A'+B'+C'+D) \cdot (A'+B+C+D) \cdot (A'+B+C'+D')$$

(65)

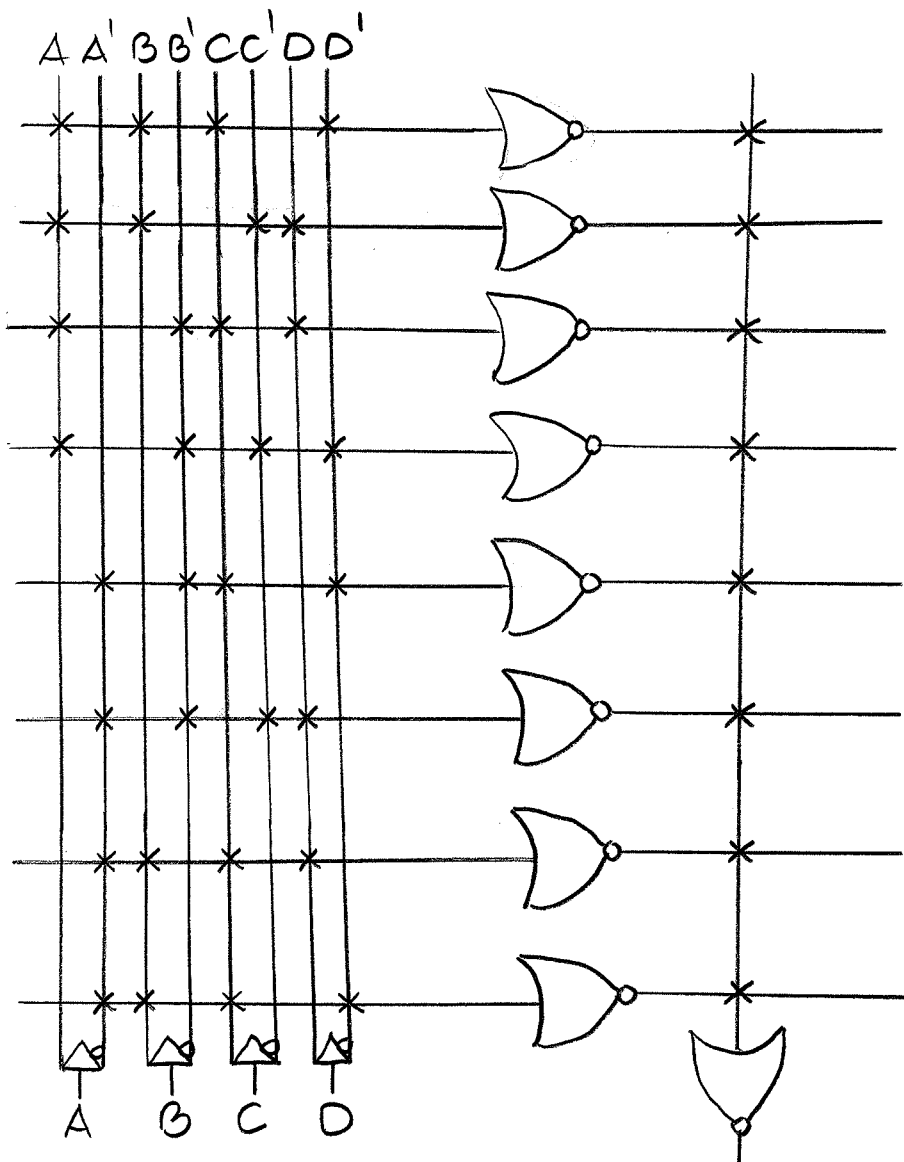



(05)

4)

$$F = A'B + B'C + A'BC'$$

A \ BC	00	01	11	10
0		1	1	1
1		1		

$$F = \sum m(1, 2, 3, 5)$$

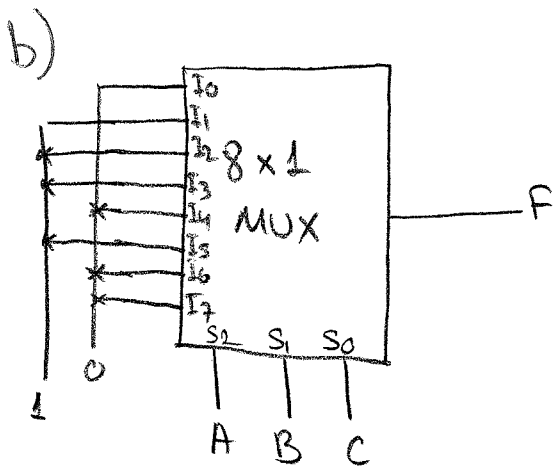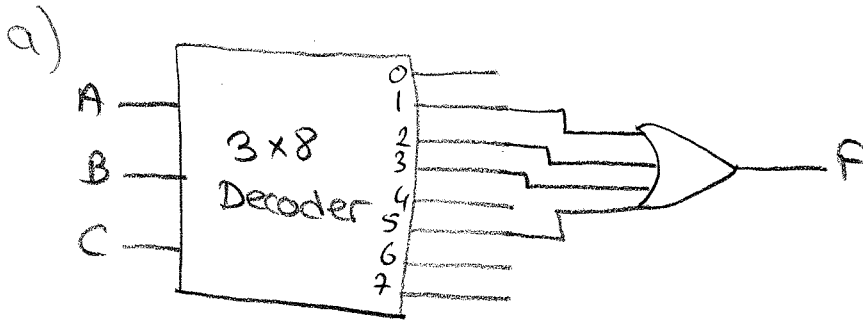

c)

$$F = A'B'C + A'BC' + A'BC + AB'C$$

$$= A(B'C) + A'(B'C + BC' + BC) \quad (i)$$

$$= B(A'C' + A'C) + B'(A'C + AC) \quad (ii)$$

$$= C(A'B' + A'B + AB') + C'(A'B) \quad (iii)$$

