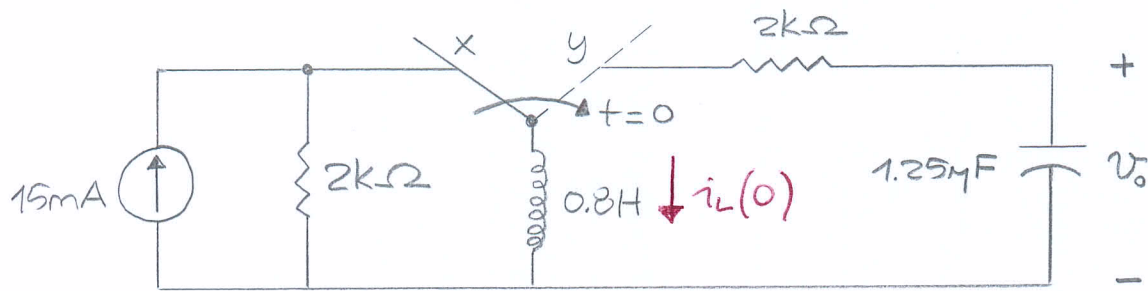


## Selected Problems - XIII

**Problem 1)** The switch has been in position x for a long time in the circuit shown as a long time in the circuit shown as



At  $t=0$ , the switch moves instantaneously to position y


a. Construct an s-domain circuit for  $t > 0$ .

b. Find  $V_o$ .

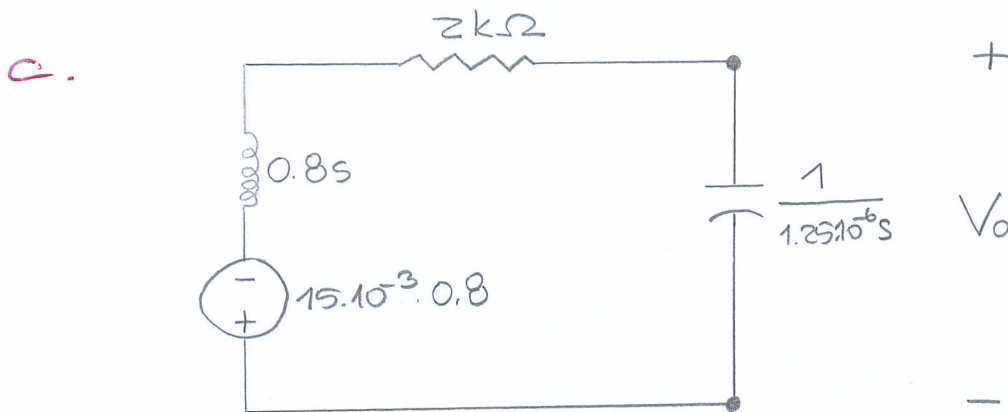c. Find  $v_o$ .

**Solution.** We find that

$$i_L(0^-) = i_L(0) = i_L(0^+) = 15 \text{ mA}$$



b.

$$\frac{V_o + 12 \cdot 10^{-3}}{0.8s + 2000} + \frac{V_o}{1/(1.25 \cdot 10^{-6}s)} = 0$$

$$\Rightarrow V_o + 12 \cdot 10^{-3} + 1.25 \cdot 10^{-6}s (0.8s + 2000) V_o = 0$$

$$\Rightarrow (1 + 10^{-6}s^2 + 2.5 \cdot 10^{-3}s) V_o = -12 \cdot 10^{-3}$$

$$\Rightarrow V_0 = - \frac{12000}{s^2 + 2500s + 10^6}$$

C. We shall write

$$V_0 = - \frac{12000}{(s+500)(s+2000)} = \frac{C_1}{s+500} + \frac{C_2}{s+2000}$$

$$\Rightarrow C_1 = - \frac{12000}{s+2000} \Big|_{s=-500} = -8$$


$$C_2 = - \frac{12000}{s+500} \Big|_{s=-2000} = 8$$

Hence ;

$$v_0 = \mathcal{L}^{-1} \left\{ -\frac{8}{s+500} + \frac{8}{s+2000} \right\}$$

$$= (-8e^{-500t} + 8e^{-2000t})u(t)$$

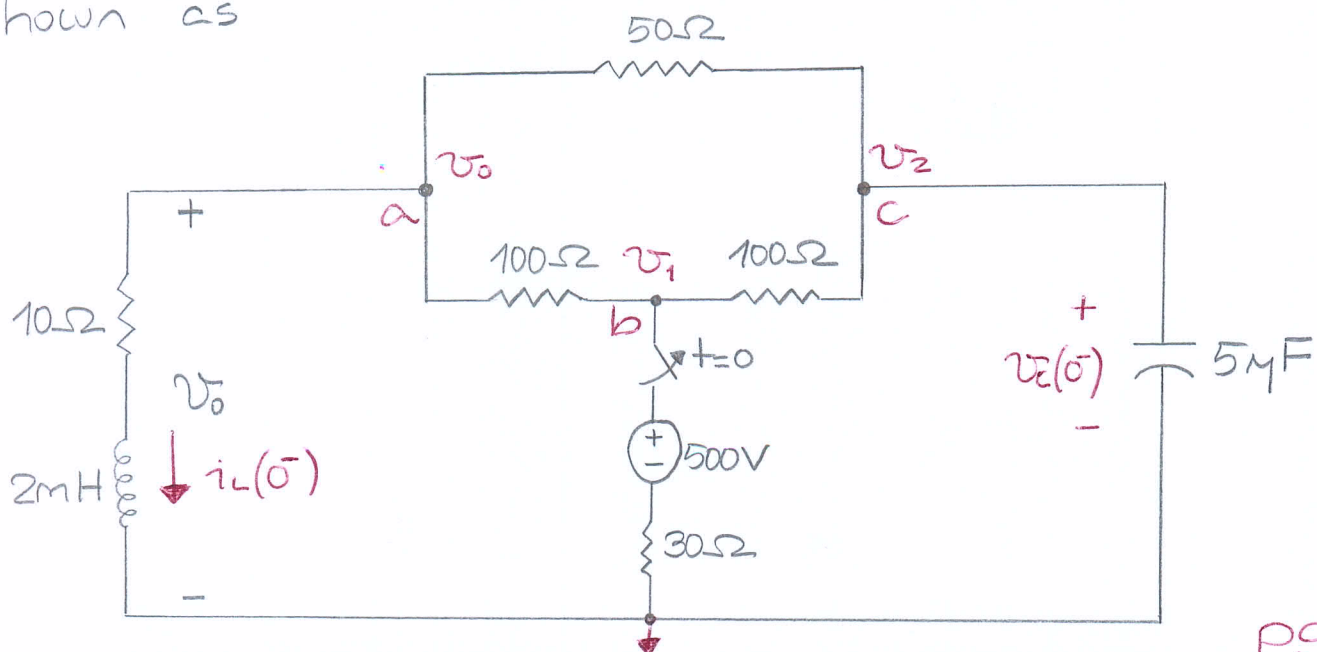**Problem 2)** The switch has been closed for a long time before opening at  $t=0$  in the circuit shown as



a. Construct the s-domain equivalent circuit for  $t > 0$ .

b. Find  $V_o$ .

c. Find  $v_o$  for  $t \geq 0$ .

**Solution.** Before  $t=0$ , we use node-voltage method to get (inductor is short-circuit, capacitor is open-circuit)

$$\textcircled{a} : \frac{v_o}{\frac{10}{(10)}} + \frac{v_o - v_1}{\frac{100}{(1)}} + \frac{v_o - v_2}{\frac{50}{(2)}} = 0$$

$$\Rightarrow 13v_o - v_1 - 2v_2 = 0 \quad (1)$$

$$\textcircled{b} : \frac{v_1 - v_o}{\frac{100}{(3)}} + \frac{v_1 - 500}{\frac{30}{(10)}} + \frac{v_1 - v_2}{\frac{100}{(3)}} = 0$$

$$\Rightarrow -3v_o + 16v_1 - 3v_2 = 5000 \quad (2)$$

$$\textcircled{c} : \frac{v_2 - v_1}{\frac{100}{(1)}} + \frac{v_2 - v_o}{\frac{50}{(2)}} = 0$$

$$\Rightarrow -2v_o - v_1 + 3v_2 = 0 \Rightarrow v_1 = -2v_o + 3v_2 \quad (3)$$

Hence ;

$$\begin{aligned} (3) \text{ in } (1) : 13v_o - (-2v_o + 3v_2) - 2v_2 &= 0 \\ \Rightarrow 15v_o - 5v_2 &= 0 \Rightarrow v_2 = 3v_o \quad (4) \end{aligned}$$

$$\begin{aligned} (3) \text{ in } (2) : -3v_o + 16(-2v_o + 3v_2) - 3v_2 &= 5000 \\ \Rightarrow -35v_o + 45v_2 &= 5000 \quad (5) \end{aligned}$$


$$\begin{aligned} (4) \text{ in } (5) : -35v_o + 45(3v_o) &= 5000 \\ \Rightarrow v_o &= 50 \text{ V}, \quad v_2 = 150 \text{ V} \quad \text{PS 13.3} \end{aligned}$$

Hence ;

$$i_L(0^-) = i_L(0) = i_L(0^+) = \frac{v_0}{10} = \frac{50}{10} = 5A$$

$$v_c(0^-) = v_c(0) = v_c(0^+) = v_2 = 150V$$

a.

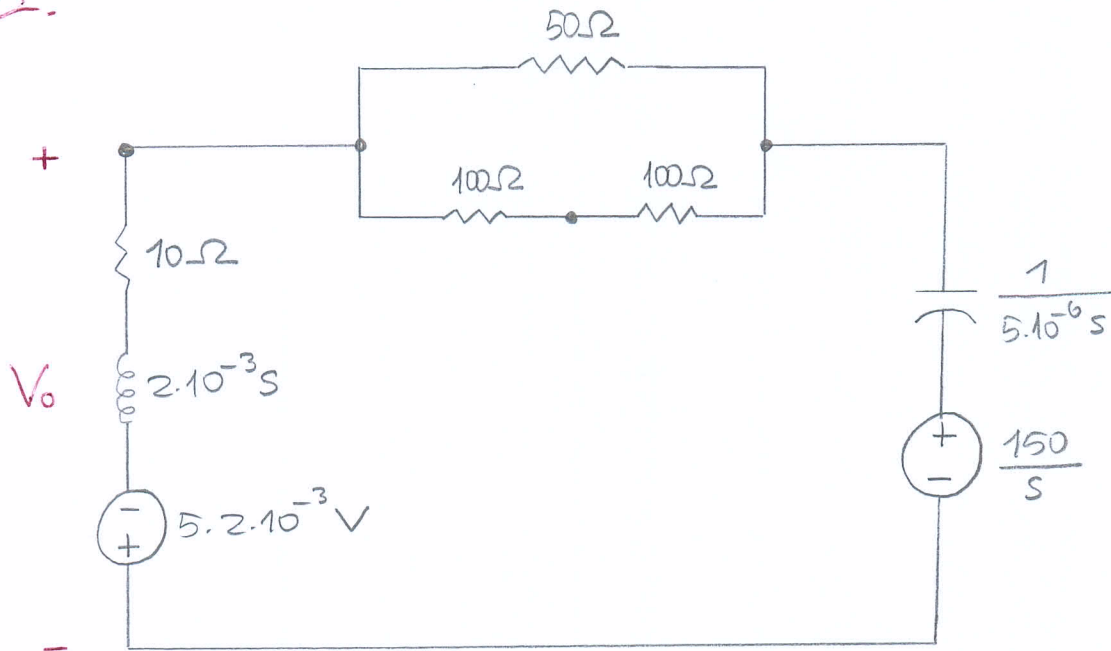

$$50\Omega \parallel (100\Omega \sim 100\Omega) \Rightarrow R_{eq} = \frac{50 \cdot 200}{50 + 200} = 40\Omega$$

b.

Hence ;

$$\frac{V_0 + 0.01}{2 \cdot 10^{-3} s + 10} + \frac{V_0 - (150/s)}{(2 \cdot 10^5/s) + 40} = 0$$

$$\Rightarrow \frac{500V_0 + 5}{s + 5000} + \frac{sV_0 - 150}{40s + 2 \cdot 10^5} = 0$$


$$\Rightarrow \frac{500V_0 + 5}{s + 5000} + \frac{s(V_0/40) - (15/4)}{s + 5000} = 0$$

$$\Rightarrow \left(\frac{s}{40} + 500\right)V_0 + \frac{5}{4} = 0 \Rightarrow V_0 = -\frac{50}{s + 20000}$$

Therefore;

$$c. v_o = \mathcal{L}^{-1} \{ V_o \} = -50 e^{-20000t} u(t)$$

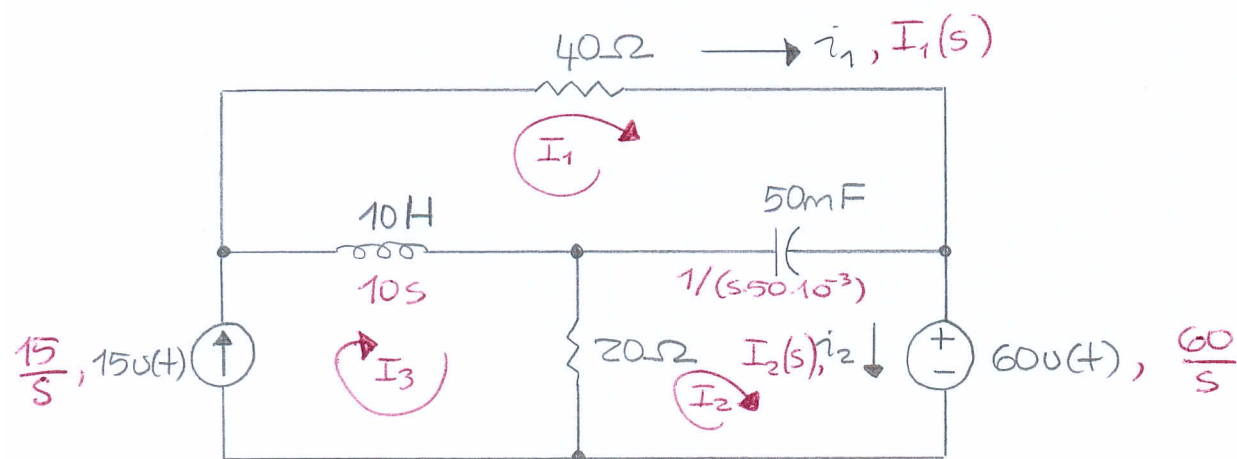**Problem 3)** There is no energy stored at the time the sources are energized in the circuit shown as



a. Find  $I_1(s)$  and  $I_2(s)$ .

b. Use the initial- and final-value theorems to check the initial- and final-values of  $i_1(t)$  and  $i_2(t)$ .

c. Find  $i_1(t)$  and  $i_2(t)$  for  $t \geq 0$ .

**Solution.** Note that

$$I_3 = \frac{15}{s}$$

a. We first write mesh equations as follows

Mesh 1 :

$$40 I_1 + \frac{20}{s} (I_1 - I_2) + 10s \left( I_1 - \frac{15}{s} \right) = 0$$

$$\Rightarrow \left( 40 + \frac{20}{s} + 10s \right) I_1 - \frac{20}{s} I_2 = 150 \quad (1)$$



Mesh 2 :

$$20 \left( I_2 - \frac{15}{s} \right) + \frac{20}{s} (I_2 - I_1) + \frac{60}{s} = 0$$

$$\Rightarrow -\frac{20}{s} I_1 + \left( 20 + \frac{20}{s} \right) I_2 = \frac{240}{s} \quad (2)$$

-we elaborately obtain

$$(s+1)/(s^2+4s+2) I_1 - 2 I_2 = 15s$$

$$2/-I_1 + (s+1) I_2 = 12$$

$$\Rightarrow [(s+1)(s^2+4s+2)-2] I_1 = 15s(s+1)+24$$

$$\Rightarrow (s^3+5s^2+6s) I_1 = 15s^2+15s+24$$

$$\Rightarrow I_1 = \frac{15s^2+15s+24}{s(s+2)(s+3)}$$

and

$$I_2 = \frac{1}{s+1} \left[ 12 + \frac{15s^2+15s+24}{s^3+5s^2+6s} \right]$$

$$= \frac{12s^3+75s^2+87s+24}{s(s+1)(s+2)(s+3)}$$

$$= \frac{\cancel{(s+1)}(12s^2+63s+24)}{s\cancel{(s+1)}(s+2)(s+3)}$$

$$= \frac{12s^2+63s+24}{s(s+2)(s+3)}$$

b.

$$i_1(0) = \lim_{s \rightarrow \infty} s I_1(s)$$

$$= \lim_{s \rightarrow \infty} \cancel{s} \frac{15s^2 + 15s + 24}{\cancel{s}(s+2)(s+3)}$$

$$= \lim_{s \rightarrow \infty} \frac{\cancel{s}^2 \left( 15 + \frac{15}{s} + \frac{24}{s^2} \right)}{\cancel{s}^2 \left( 1 + \frac{2}{s} + \frac{3}{s^2} \right)}$$

$$= 15$$

$$i_1(\infty) = \lim_{s \rightarrow 0} s I_1(s)$$

$$= \lim_{s \rightarrow 0} \cancel{s} \frac{15s^2 + 15s + 24}{\cancel{s}(s+2)(s+3)}$$

$$= \frac{24}{2 \cdot 3}$$

$$= 4$$

end

$$i_2(0) = \lim_{s \rightarrow \infty} s I_2(s)$$

$$= \lim_{s \rightarrow \infty} \cancel{s} \frac{12s^2 + 63s + 24}{\cancel{s}(s+2)(s+3)}$$

$$= \lim_{s \rightarrow \infty} \frac{\cancel{s}^2 \left( 12 + \frac{63}{s} + \frac{24}{s^2} \right)}{\cancel{s}^2 \left( 1 + \frac{2}{s} + \frac{3}{s^2} \right)}$$

$$= 12$$

$$i_2(\infty) = \lim_{s \rightarrow 0} s I_2(s)$$

$$= \lim_{s \rightarrow 0} \cancel{s} \frac{12s^2 + 63s + 24}{\cancel{s}(s+2)(s+3)}$$

$$= \frac{24}{2 \cdot 3}$$

$$= 4$$

c. We find that

$$I_1(s) = \frac{15s^2 + 15s + 24}{s(s+2)(s+3)} = \frac{C_1}{s} + \frac{C_2}{s+2} + \frac{C_3}{s+3}$$

$$\Rightarrow C_1 = \left. \frac{15s^2 + 15s + 24}{(s+2)(s+3)} \right|_{s=0} = \frac{24}{2 \cdot 3} = 4$$

$$C_2 = \left. \frac{15s^2 + 15s + 24}{s(s+3)} \right|_{s=-2} = \frac{60 - 30 + 24}{(-2) \cdot 1} = -27$$

$$C_3 = \left. \frac{15s^2 + 15s + 24}{s(s+2)} \right|_{s=-3} = \frac{135 - 45 + 24}{(-3) \cdot (-1)} = 38$$

Hence;

$$i_1(t) = \mathcal{L}^{-1}\{I_1(s)\} = (4 - 27e^{-2t} + 38e^{-3t})u(t)$$

and

$$I_2(s) = \frac{12s^2 + 63s + 24}{s(s+2)(s+3)} = \frac{d_1}{s} + \frac{d_2}{s+2} + \frac{d_3}{s+3}$$

$$\Rightarrow d_1 = \left. \frac{12s^2 + 63s + 24}{(s+2)(s+3)} \right|_{s=0} = \frac{24}{2 \cdot 3} = 4$$

$$d_2 = \left. \frac{12s^2 + 63s + 24}{s(s+3)} \right|_{s=-2} = \frac{48 - 126 + 24}{(-2) \cdot 1} = 27$$


$$d_3 = \left. \frac{12s^2 + 63s + 24}{s(s+2)} \right|_{s=-3} = \frac{108 - 189 + 24}{(-3) \cdot (-1)} = -19$$

Thus;

$$i_2(t) = \mathcal{L}^{-1}\{I_2(s)\} = (4 + 27e^{-2t} - 19e^{-3t})u(t) \quad \text{PS 13.8}$$



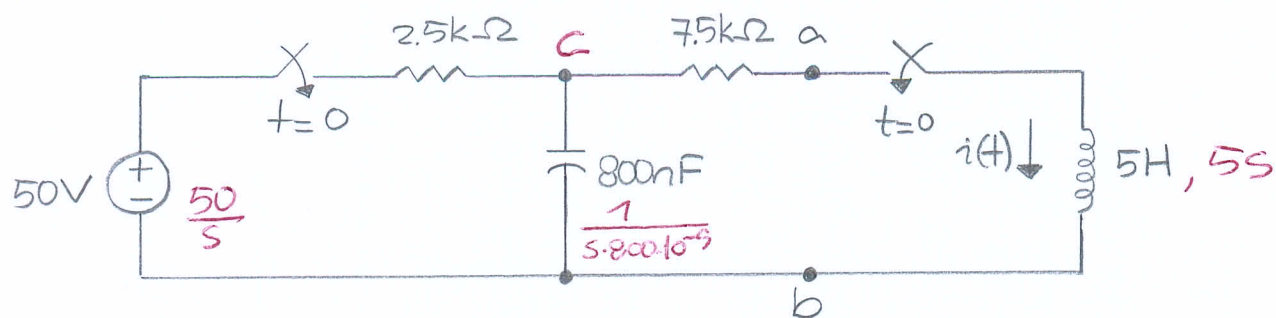**Problem 4)** The two switches operate simultaneously in the circuit shown as



There is no energy stored in the circuit at the instant the switches close. Find  $i(t)$  for  $t \geq 0^+$  by first finding the s-domain Thévenin equivalent of the circuit to the left of the terminals c, b.

**Solution.** we notice that

$$V_{Th} = V_{cb} = V_{cd} = \frac{50}{s} \frac{10^7/8s}{2500 + \frac{10^7}{8s}}$$

$$= \frac{5 \cdot 10^8}{s(20000s + 10^7)} = \frac{5 \cdot 10^4}{s(2s + 1000)} = \frac{25000}{s(s+500)}$$

- for the Thévenin impedance, we calculate the equivalent impedance seen through a, b:

$$2500 \Omega \parallel \frac{10^7}{8s} \Rightarrow Z_{eq1} = \frac{2500 \cdot 10^7/8s}{2500 + \frac{10^7}{8s}}$$

$$\Rightarrow Z_{eq1} = \frac{25 \cdot 10^7}{20000s + 10^7}$$


$$Z_{eq1} \sim 7500 \Omega \Rightarrow Z_{Th} = 7500 + \frac{25 \cdot 10^3}{20000s + 10^7}$$

$$= 7500 + \frac{25 \cdot 10^5}{2s + 1000} \text{ PS139}$$

Hence;

$$\begin{aligned} Z_{Th} &= \frac{15000s + 75 \cdot 10^5 + 25 \cdot 10^5}{2s + 1000} \\ &= \frac{7500s + 5 \cdot 10^6}{s + 500} \end{aligned}$$

- we thus have

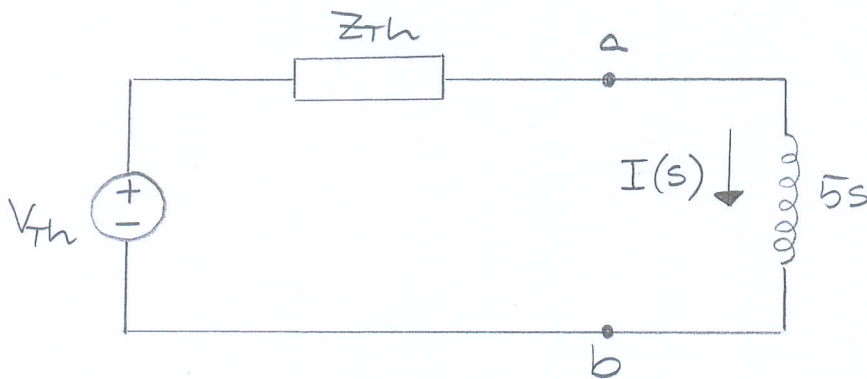

$$\begin{aligned} I(s) &= \frac{V_{Th}}{Z_{Th} + 5s} = \frac{25000 / [s(s+500)]}{\frac{7500s + 5 \cdot 10^6}{s + 500} + 5s} \\ &= \frac{25000}{s(7500s + 5 \cdot 10^6) + 5s^2(s + 500)} \\ &= \frac{25000}{5s^3 + 10000s^2 + 5 \cdot 10^6 s} \\ &= \frac{\overset{5}{\cancel{25}}000}{5s(s^2 + 2000s + 10^6)} \\ &= \frac{5 \cdot 10^3}{s(s + 1000)^2} \end{aligned}$$

$$= \frac{C_1}{s} + \frac{C_2}{(s+1000)^2} + \frac{C_3}{s+1000}$$

$$\Rightarrow C_1 = \frac{5 \cdot 10^3}{(s+1000)^2} \Big|_{s=0} = 5 \cdot 10^{-3}$$

$$C_2 = \frac{5 \cdot 10^3}{s} \Big|_{s=-1000} = -5$$

$$C_3 = \frac{d}{ds} \left( \frac{5 \cdot 10^3}{s} \right) \Big|_{s=-1000} = - \frac{5 \cdot 10^3}{s^2} \Big|_{s=-1000} = -5 \cdot 10^{-3}$$

Hence;

$$\mathcal{L}^{-1}\{I(s)\} = i(t) = 5 \cdot 10^{-3} - 5 + e^{-1000t} - 5 \cdot 10^{-3} e^{-1000t}, t \geq 0$$

$$\Rightarrow i(t) = 5 (1 - 1000t e^{-1000t} - e^{-1000t}) u(t) \text{ mA}$$