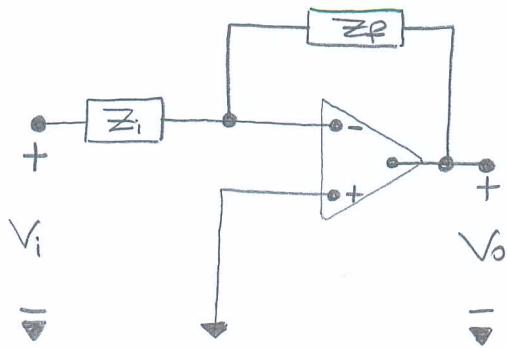


Selected Problems IV

Problem 1) Find the transfer function V_o/V_i for the circuit shown as



where Z_f is the equivalent impedance of the feedback circuit, and Z_i is the equivalent impedance of the input circuit, and op amp is ideal.

Solution. We have


$$V_n = V_p = 0, i_n = i_p = 0$$

KCL at inverting input of the op amp :

$$\frac{0 - V_i}{Z_i} + \frac{0 - V_o}{Z_f} = 0$$

$$\Rightarrow -\frac{V_i}{Z_i} - \frac{V_o}{Z_f} = 0 \Rightarrow \frac{V_o}{V_i} = -\frac{Z_f}{Z_i}$$

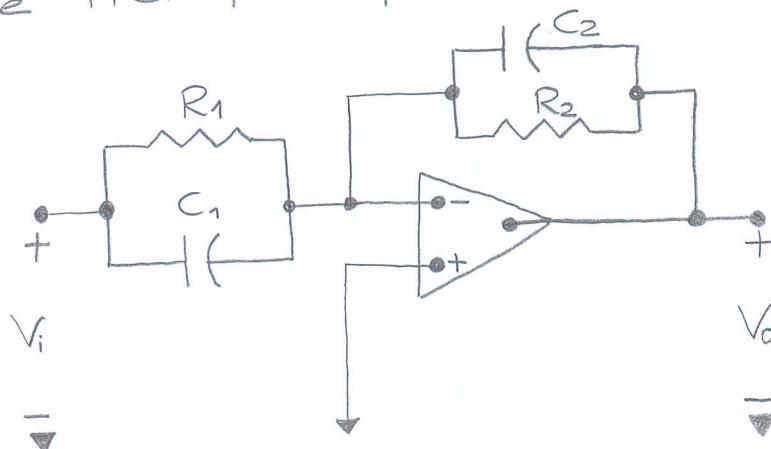Problem 2) Use the results of Problem 1 to find the transfer function of the following circuit :



- a. What is the gain of the circuit as $\omega \rightarrow 0$?
 b. What is the gain of the circuit as $\omega \rightarrow \infty$?
 c. Do your answers to (b) and (c) make sense in terms of known circuit behavior?

Solution. We calculate

$$Z_i : R_1 \parallel \frac{1}{sC_1} \Rightarrow Z_i = \frac{R_1 \cdot (1/sC_1)}{R_1 + (1/sC_1)} = \frac{R_1}{sR_1C_1 + 1}$$

$$Z_f : R_2 \parallel \frac{1}{sC_2} \Rightarrow Z_f = \frac{R_2 \cdot (1/sC_2)}{R_2 + (1/sC_2)} = \frac{R_2}{sR_2C_2 + 1}$$

Hence ;

$$\begin{aligned} \frac{V_o}{V_i} &= -\frac{R_2 / sR_2 C_2 + 1}{R_1 / sR_1 C_1 + 1} = -\frac{R_2 (sR_1 C_1 + 1)}{R_1 (sR_2 C_2 + 1)} \\ &= -\frac{sR_1 R_2 C_1 + R_2}{sR_1 R_2 C_2 + R_1} \\ &= -\frac{\cancel{R_1 R_2 C_1} \left(s + \frac{1}{R_1 C_1} \right)}{\cancel{R_1 R_2 C_2} \left(s + \frac{1}{R_2 C_2} \right)} \\ &= -\frac{C_1}{C_2} \frac{s + (1/R_1 C_1)}{s + (1/R_2 C_2)} \triangleq H(s) \end{aligned}$$

2. We let $s = j\omega$ in $H(s)$ to get

$$H(j\omega) = -\frac{C_1}{C_2} \frac{j\omega + (1/R_1 C_1)}{j\omega + (1/R_2 C_2)}$$

$$\begin{aligned} H(j\omega) &= -\frac{C_1}{C_2} \frac{1/R_1 C_1}{1/R_2 C_2} \\ &= -\frac{\cancel{C_1}}{\cancel{C_2}} \frac{R_2 \cancel{C_2}}{R_1 \cancel{C_1}} = -\frac{R_2}{R_1} \end{aligned}$$

b.

$$\lim_{\omega \rightarrow \infty} H(j\omega) = \lim_{\omega \rightarrow \infty} -\frac{C_1}{C_2} \frac{j\omega(1 + \frac{1}{j\omega R_1 C_1})}{j\omega(1 + \frac{1}{j\omega R_2 C_2})}$$

$$= -\frac{C_1}{C_2}$$

c. As $\omega \rightarrow 0$, the capacitors behave as an open-circuit

(b) the circuit becomes a resistive inverting amplifier with a gain of $-\frac{R_2}{R_1}$

As $\omega \rightarrow \infty$, the capacitors behave as a short-circuit

(c) we obtain an indeterminate situation, i.e.
 $v_n \rightarrow v_i$ BUT $v_n = 0$ (ideal op amp)

Moreover;

-the gain of the ideal op amp is infinite

(d) $v_o \rightarrow \infty$. 0 INDETERMINATE case


However;

-for finite values of ω , $H(j\omega) \rightarrow -\frac{C_2}{C_1}$

(e) the circuit approaches a purely capacitive inverting amplifier

Problem 3) Repeat Problem 2 using the circuit shown

as

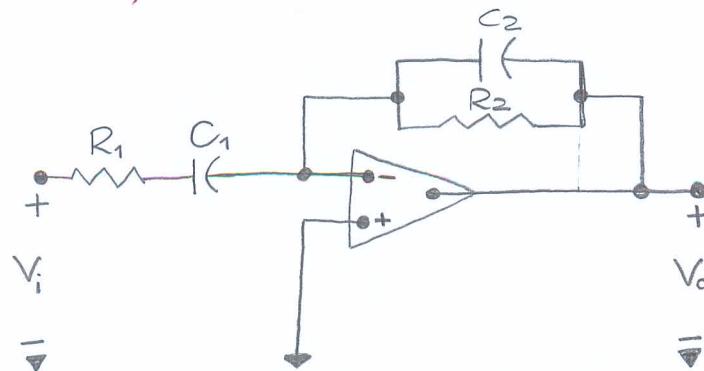

Solution. We have

$$Z_i = R_1 + \frac{1}{sC_1}, \quad Z_f = -\frac{R_2 \cdot (1/sC_2)}{R_2 + (1/sC_2)} = \frac{R_2}{sR_2C_2 + 1}$$

-then

$$\frac{V_o}{V_i} \triangleq H(s) = -\frac{Z_f}{Z_i} = -\frac{R_2 / (sR_2C_2 + 1)}{(sR_1C_1 + 1) / sC_1}$$
$$= -\frac{sR_2C_1}{(sR_1C_1 + 1)(sR_2C_2 + 1)}$$

c. We let $s = j\omega$ to obtain

$$H(j\omega) = -\frac{j\omega R_2 C_1}{(j\omega R_1 C_1 + 1)(j\omega R_2 C_2 + 1)}$$

$$H(j\omega) = -\frac{0 \cdot R_2 C_1}{(0 \cdot R_1 C_1 + 1)(0 \cdot R_2 C_2 + 1)} = 0$$

b.

$$\lim_{\omega \rightarrow \infty} H(j\omega) = \lim_{\omega \rightarrow \infty} -\frac{j\omega R_2 C_2}{j\omega R_1 C_1 \left(1 + \frac{1}{j\omega R_1 C_1}\right) j\omega R_2 C_2 \left(1 + \frac{1}{j\omega R_2 C_2}\right)}$$
$$= 0$$

c. As $\omega \rightarrow 0$, the capacitor C_1 becomes open-circuit and disconnects V_i and V_n

(\hookrightarrow) thus, $V_o = V_n = 0$

As $\omega \rightarrow \infty$, the capacitor C_2 becomes short-circuit and connects output with the inverting input of the op amp (\hookrightarrow) thus, $V_o = V_n = 0$

Problem 4) Consider the circuit in Problem 1.

- a. Design a low-pass filter with a passband gain of 15 dB and a cutoff frequency of 10 kHz. Assume a 5 nF capacitor is available.
- b. Draw the circuit diagram and label all components.

Solution. We choose

$$Z_i \equiv R_1, \quad Z_P : R_2 // \frac{1}{sC}$$

$$\Rightarrow H(s) = -\frac{Z_P}{Z_i} = -\frac{\frac{R_1 \cdot (1/sC)}{R_1 + \frac{1}{sC}}}{R_2}$$

$$= -\frac{R_1}{R_2} \frac{1}{sR_1 C + 1}$$

$$= -\frac{R_1}{R_2} \frac{1/R_1 C}{s + (1/R_1 C)} \stackrel{\triangle}{=} -K \frac{\omega_c}{s + \omega_c}$$

where


$$\omega_c = \frac{1}{R_1 C}, \quad K = \frac{R_1}{R_2}$$

$$2\pi \cdot 10 \cdot 10^3 = \frac{1}{R_1 \cdot 5 \cdot 10^{-9}} \Rightarrow R_1 = \frac{10000}{\pi} \approx 31831 \text{ k}\Omega$$

$$20 \log_{10} |H(j\omega)| = 15 \Rightarrow 20 \log_{10} K = 15^3$$

$$\Rightarrow K = 10^{3/4} = 5.6234 \Rightarrow R_2 = \frac{3.1831 \cdot 10^3}{5.6234} = 566.0439 \Omega$$

b.

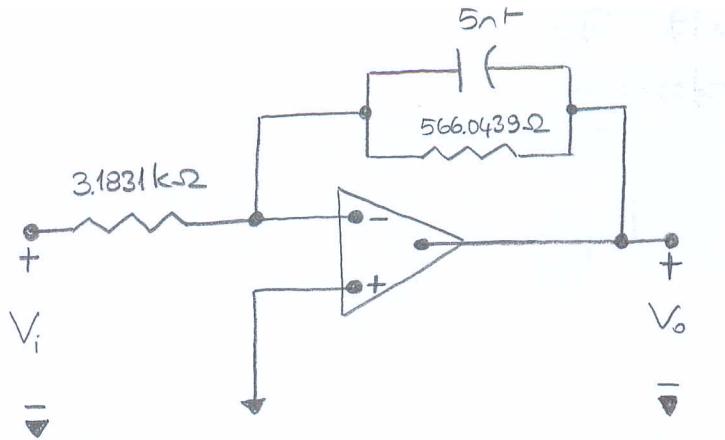

Problem 5) Design an op-amp-based high pass filter with a cutoff frequency of 300 Hz and a passband gain of 5 using a 100 nF capacitor.

Solution. We let Z_i, Z_f in the circuit of Problem 1 to be chosen as

$$Z_i = R_1 + \frac{1}{sC}, \quad Z_f = R_2$$

-then we get

$$H(s) = -\frac{Z_f}{Z_i} = -\frac{R_2}{R_1 + \frac{1}{sC}}$$

$$= -\frac{sR_2 C}{sR_1 C + 1}$$

$$= -\frac{R_2}{R_1} \frac{s}{s + (1/R_1 C)}$$

$$\triangleq -K \frac{s}{s + \omega_c}$$

where

$$K = \frac{R_2}{R_1}, \quad \omega_c = \frac{1}{R_1 C}$$


$$R_1 = \frac{1}{2\pi \cdot (300) \cdot 100 \cdot 10^{-9}} = 5.3052 \text{ k}\Omega$$

and

$$R_2 = 5 \cdot 5.3052 \cdot 10^3 = 26.526 \text{ k}\Omega$$

Hence ;

-we shall draw the op amp-based highpass filter circuit as

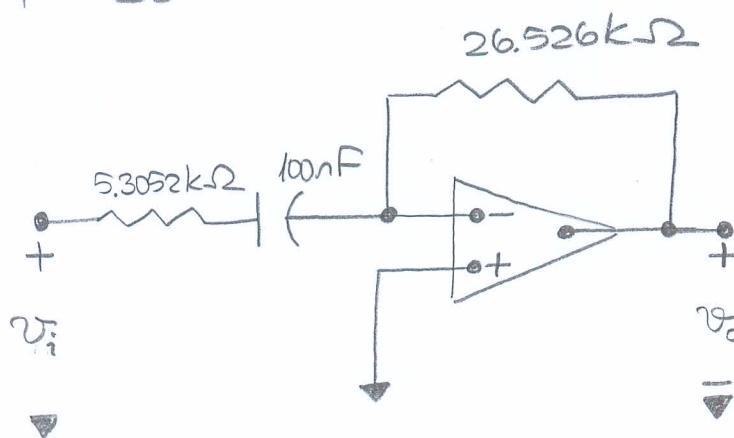

Problem 6) The input to the high pass filter designed in Problem 5 is $150 \cos \omega t \text{ mV}$.

a. Suppose the power supplies are $\pm V_{cc}$. What is the smallest value of V_{cc} that will cause the op amp to operate in its linear region?

b. Find the output voltage when $\omega = \omega_c$.

Solution. It follows from Problem 5 that we have

$$\omega_c = 2\pi \cdot 300 = 600\pi = 1885 \text{ rad/s}$$

$$K = 5$$

$$\Rightarrow H(s) = -5 \frac{s}{s + 1885} = \frac{V_o}{V_i}, \quad V_i = 150 \angle 0^\circ \text{ mV}$$

$$\Rightarrow H(j\omega) = -5 \frac{j\omega}{j\omega + 1885}$$

and

$$H_{max} = \lim_{\omega \rightarrow \infty} |H(j\omega)| = 5$$

Hence;

$$V_{cc} \geq H_{max} \cdot (V_i)_{max} = 5 \cdot 150 = 750 \text{ mV}$$

b.

$$H(j\omega_c) = -5 \frac{j \cdot 1885}{j1885 + 1885} = 5 \frac{1885 \angle -90^\circ}{1885\sqrt{2} \angle 45^\circ}$$
$$= \frac{5}{\sqrt{2}} \angle -135^\circ$$


$$V_o = H(j1885) \cdot V_i$$

$$= \frac{5}{\sqrt{2}} \angle -135^\circ \cdot 0.15 \angle 0^\circ$$

$$= 0.5303 \angle -135^\circ$$

$$\Rightarrow v_o(t) = 0.5303 \cos(\omega t - 135^\circ) \quad \checkmark$$

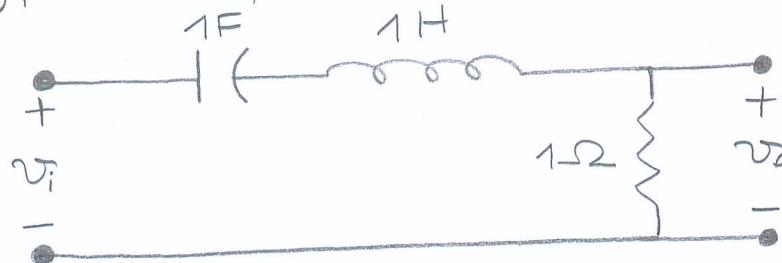Problem 7) The voltage transfer function of the prototype bandpass filter shown as



$$\frac{V_o}{V_i} = H(s) = \frac{\left(\frac{1}{\alpha}\right)s}{s^2 + \left(\frac{1}{\alpha}\right)s + 1}$$

Show that if the circuit is scaled in both magnitude and frequency, the scaled transfer function is

$$\left(\frac{1}{\alpha}\right)\left(\frac{s}{k_f}\right)$$

$$H(s) = \frac{(s)^2}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{\alpha}\right)\left(\frac{s}{k_f}\right) + 1}$$

Solution. Let k_m and k_f denote magnitude and frequency scaling factor, respectively

$$R' \rightarrow k_m R$$

$$L' \rightarrow \frac{k_m}{k_f} L$$

$$C' \rightarrow \frac{1}{k_m k_f} C$$

$$H'(s) = \frac{k_m R}{\frac{1}{s \frac{C}{k_m k_f}} + s \frac{k_m}{k_f} L + k_m R}$$

$$= \frac{k_f R}{\frac{k_f k_p}{s C} + s \frac{k_f}{k_p} L + k_f R}$$

$$= \frac{R}{\frac{k_f}{s C} + \frac{s}{k_f} L + R}$$

$$= \frac{R \cdot (s C / k_f)}{1 + \left(\frac{s}{k_f}\right)^2 L C + \left(\frac{s}{k_f}\right)^2 R C}$$

$$= \frac{\left(\frac{R}{L}\right) \left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \frac{R}{L} \left(\frac{s}{k_f}\right) + \frac{1}{LC}} \stackrel{\Delta}{=} \frac{\beta \left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \beta \left(\frac{s}{k_f}\right) + \omega_0^2}$$

Note that;

- for a prototype bandpass filter, we have


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1.1}} = 1 \text{ rad/sec}$$

$$Q = \frac{\omega_0}{\beta} \Rightarrow \beta = \frac{1}{Q}$$

Hence;

$$H'(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_p}\right)}{\left(\frac{s}{k_p}\right)^2 + \left(\frac{1}{Q}\right)\left(\frac{s}{k_p}\right) + 1}$$

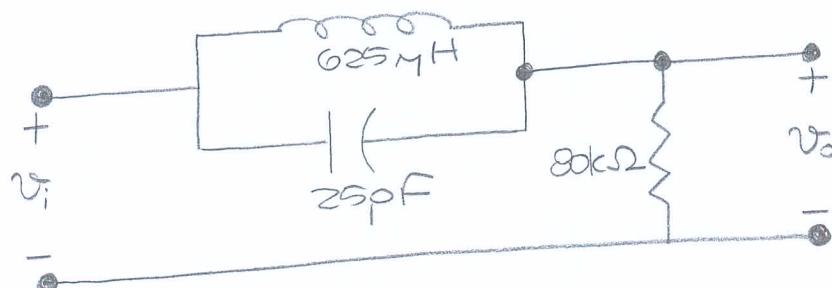Problem 8) Consider the following bandreject filter.



Scale this bandreject filter to get a center frequency of 500 kHz using a 50 μH inductor.

Determine the values of the resistor, the capacitor and bandwidth of the scaled filter.

Solution. We first calculate the center frequency of the unscaled filter:

$$\omega_0 = \frac{1}{\sqrt{625 \cdot 10^{-6} \cdot 25 \cdot 10^{-12}}} = \frac{1}{25 \cdot 5 \cdot 10^{-9}} = \frac{1000}{125} \cdot 10^6 = 8 \text{ Mrad/s}$$

$$\Rightarrow k_p = \frac{500 \cdot 10^3}{8 \cdot 10^6} = 62.5 \cdot 10^{-3}$$

and

$$50 \text{ M H} = \frac{k_m}{k_f} \cdot 625 \text{ M H}$$

$$\Rightarrow 5\phi = \frac{k_m}{62.5 \cdot 10^{-3}} \cdot \frac{10}{625} \Rightarrow k_m = 5 \cdot 10^{-3}$$

Hence;

$$C' = \frac{C}{k_m k_f} = \frac{25 \cdot 10^{-12}}{5 \cdot 10^{-3} \cdot 62.5 \cdot 10^{-3}} = 8 \cdot 10^{-8} = 80 \text{ nF}$$


//

and

$$R' = k_m R = 5 \cdot 10^{-3} \cdot 80 \cdot 10^3 = 400 \Omega$$

$$\beta' = \frac{1}{R' C'} = \frac{1}{400 \cdot 80 \cdot 10^{-8}} = \frac{10^6}{32} = 31250 \text{ rad/sec}$$

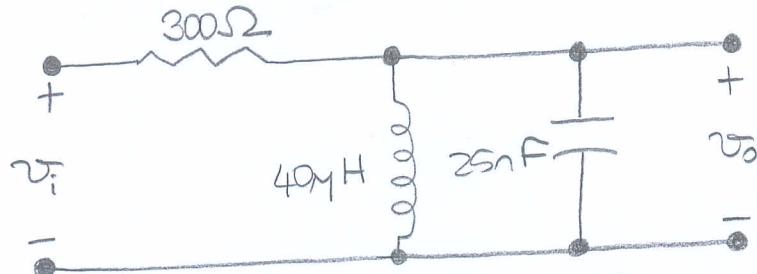Problem 9) Consider the following bandpass filter shown as



Scale this bandpass filter so that the center frequency is 250 kHz and the quality factor is 7.5 using a 10nF capacitor. Determine the value of the resistor, the inductor, and the two cutoff frequencies of the scaled filter.

Solution. We first calculate the center frequency of the unscaled filter:

$$\omega_0 = \frac{1}{\sqrt{40 \cdot 10^{-6} \cdot 25 \cdot 10^9}} = \frac{1}{\sqrt{10^{-12}}} = 10^6 \text{ rad/sec}$$

$$\Rightarrow k_f = \frac{2\pi \cdot 250 \cdot 10^3}{10^3} = 0.5\pi = 1.5708$$

- For the magnitude scaling factor, we have

$$\frac{10^2 \cdot 10^{-8}}{10^2 \cdot 10^{-8}} = \frac{25 \cdot 10^{-8}}{1.5708 \cdot k_m} \Rightarrow k_m = 1.5315$$

Hence ;

$$R' = 1.5315 \cdot 300 = 477.4648 \Omega$$

$$L' = \frac{1.5315}{1.5708} \cdot 40 \text{ mH} = 40.5271 \text{ mH}$$

$$\beta' = \frac{1}{R' \cdot C'} = \frac{1}{477.4648 \cdot 10 \cdot 10^{-9}} = 210k \text{ rad/sec}$$

$$\omega_{c1}' = -\frac{\beta'}{2} + \sqrt{\left(\frac{\beta'}{2}\right)^2 + (\omega_0')^2}$$

$$= -\frac{210k}{2} + \sqrt{\left(\frac{210k}{2}\right)^2 + (2\pi \cdot 250k)^2}$$

$$= 1469.3 \text{ rad/sec}$$

$$\omega_{c2}' = -\frac{\beta'}{2} + \sqrt{\left(\frac{\beta'}{2}\right)^2 + (\omega_0')^2}$$

$$= \frac{210k}{2} + \sqrt{\left(\frac{210k}{2}\right)^2 + (2\pi \cdot 250k)^2}$$

$$= 1679.3 \text{ rad/sec}$$