

## Selected Problems - IX

**Problem 1)** Design a sequential circuit with two JK flip-flops A and B and two inputs E and F. If  $E=0$ , the circuit remains in the same state regardless of the value of F. When  $E=1$  and  $F=1$ , the circuit goes through the state transitions from 00 to 01, to 10, to 11, back to 00, and repeats. When  $E=1$  and  $F=0$ , the circuit goes through the state transitions from 00 to 11, to 10, to 01, back to 00, and repeats.

**Solution.** We have the following extended state table

inputs		present states		next states		flip-flop inputs			
E	F	$y_A$	$y_B$	$Y_A$	$Y_B$	$J_A$	$K_A$	$J_B$	$K_B$
0	d	0	0	0	0	0	d	0	d
0	d	0	1	0	1	0	d	d	0
0	d	1	0	1	0	d	0	0	d
0	d	1	1	1	1	d	0	d	0
1	1	0	0	0	1	0	d	1	d
1	1	0	1	1	0	1	d	d	1
1	1	1	0	1	1	d	0	1	d
1	1	1	1	0	0	d	1	d	1
1	0	0	0	1	1	1	d	1	d
1	0	0	1	0	0	0	d	d	1
1	0	1	0	0	1	d	1	1	d
1	0	1	1	1	0	d	0	1	d

$J_A$ : E	$F y_B$	00	01	11	10
	0		d	d	
1	1	<span style="border: 1px solid black; padding: 2px;">1</span>		<span style="border: 1px solid black; padding: 2px;">1</span>	

$$\begin{aligned}
 J_A &= EF'y_B + EFy_B \\
 &= E(F \oplus y_B)'
 \end{aligned}$$

$K_A :$

	$Fy_B$	00	01	11	10
$E$					
0		.	d	d	.
1		1	.	1	.

$$K_A = EF'y_B + EFy_B$$

$$= E(F \oplus y_B)'$$

$J_B :$


	$Fy_A$	00	01	11	10
$E$					
0		.	.	.	.
1		1	1	1	1

$$J_B = E$$


	$Fy_A$	00	01	11	10
$E$					
0		.	.	.	.
1		1	d	1	1

$$K_B = E$$

-and the circuit diagram can be drawn as

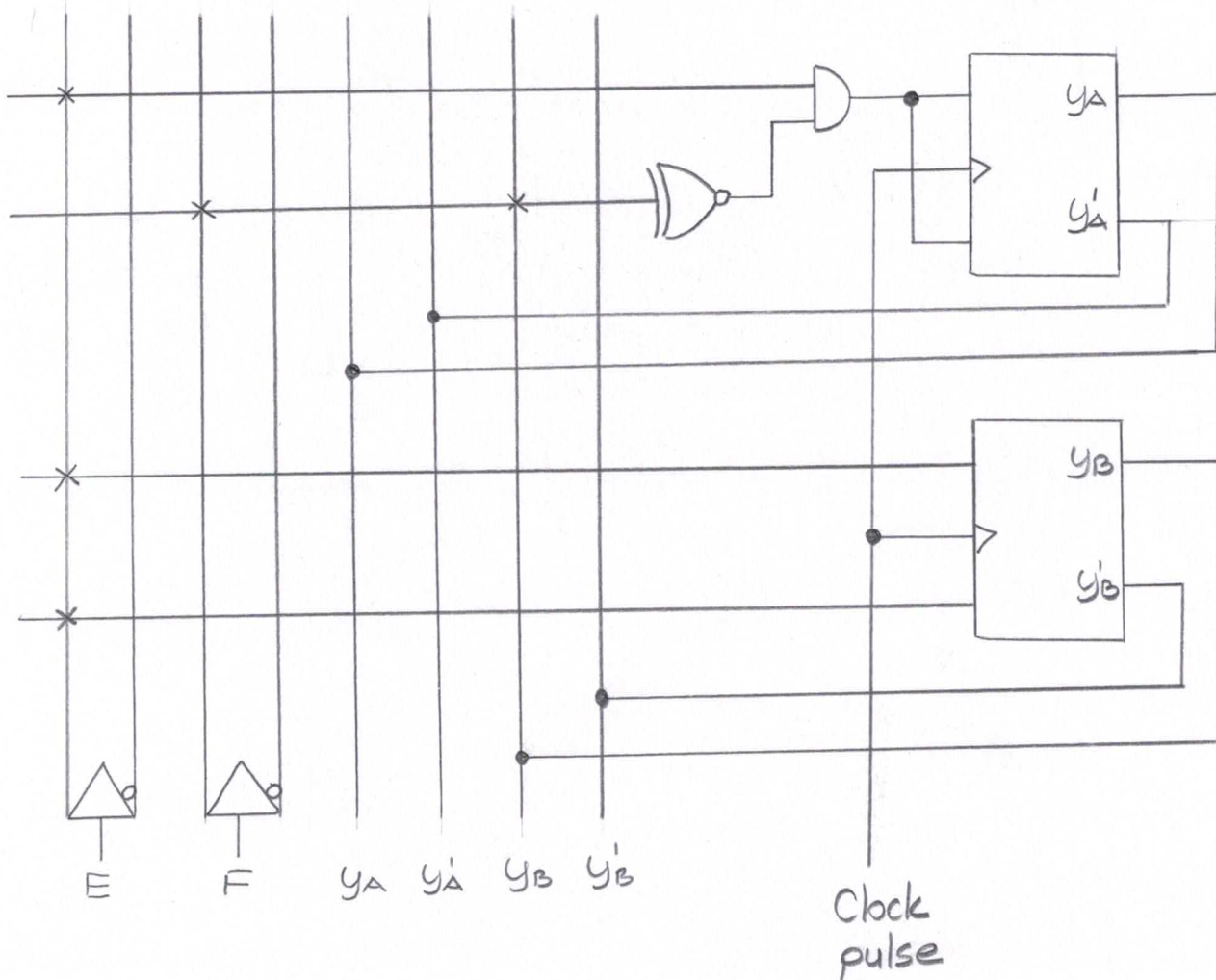

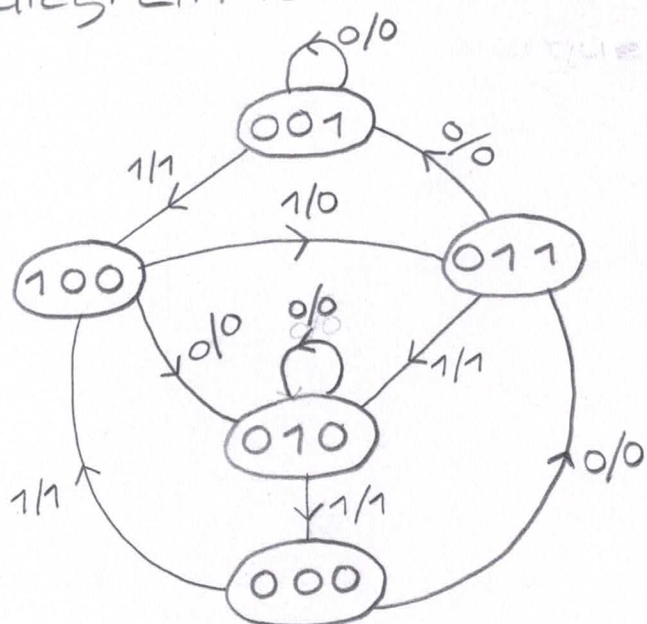**Problem 2)** A sequential circuit has three flip-flops A, B, and C; one input  $x$  and one output  $y$ . The state diagram is shown as



The circuit is to be designed by treating the unused states as don't care conditions. Analyze the circuit obtained from the design to determine the effect of the unused states.

- Use D flip-flops in the design.
- Use JK flip-flops in the design.

**Solution.**

- We construct the extended state table as

$x$	$y_A$	$y_B$	$y_C$	$Y_A$	$Y_B$	$Y_C$	$D_A$	$D_B$	$D_C$	$z$
0	0	0	0	0	1	1	0	1	1	0
1	0	0	0	1	0	0	1	0	0	1
0	0	0	1	0	0	1	0	0	1	0
1	0	0	1	1	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1	0	0
1	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	1	0	0	1	0
1	0	1	1	0	1	0	0	1	0	1
0	1	0	0	0	1	0	0	1	0	0
1	1	0	0	0	1	1	0	1	1	0

- we treat the unused states 101, 110, 111 as don't



$D_A :$

$y_B y_C$	00	01	11	10
$x y_A$				
00				
01		d	d	d
11		d	d	d
10	1	1		

$$D_A = x y_A' y_B'$$

$D_B :$

$y_B y_C$	00	01	11	10
$x y_A$				
00	1			1
01	1	d	d	d
11	1	d	d	d
10			1	

$$D_B = x' y_C' + y_A + x y_B y_C$$

$D_C :$


$y_B y_C$	00	01	11	10
$x y_A$				
00	1	1	1	
01		d	d	d
11	1	d	d	d
10				

$$D_C = x y_A + x' y_C + x' y_A' y_B'$$

$Z :$

$y_B y_C$	00	01	11	10
$x y_A$				
00				
01		d	d	d
11		d	d	d
10	1	1	1	1

$$Z = x y_A'$$

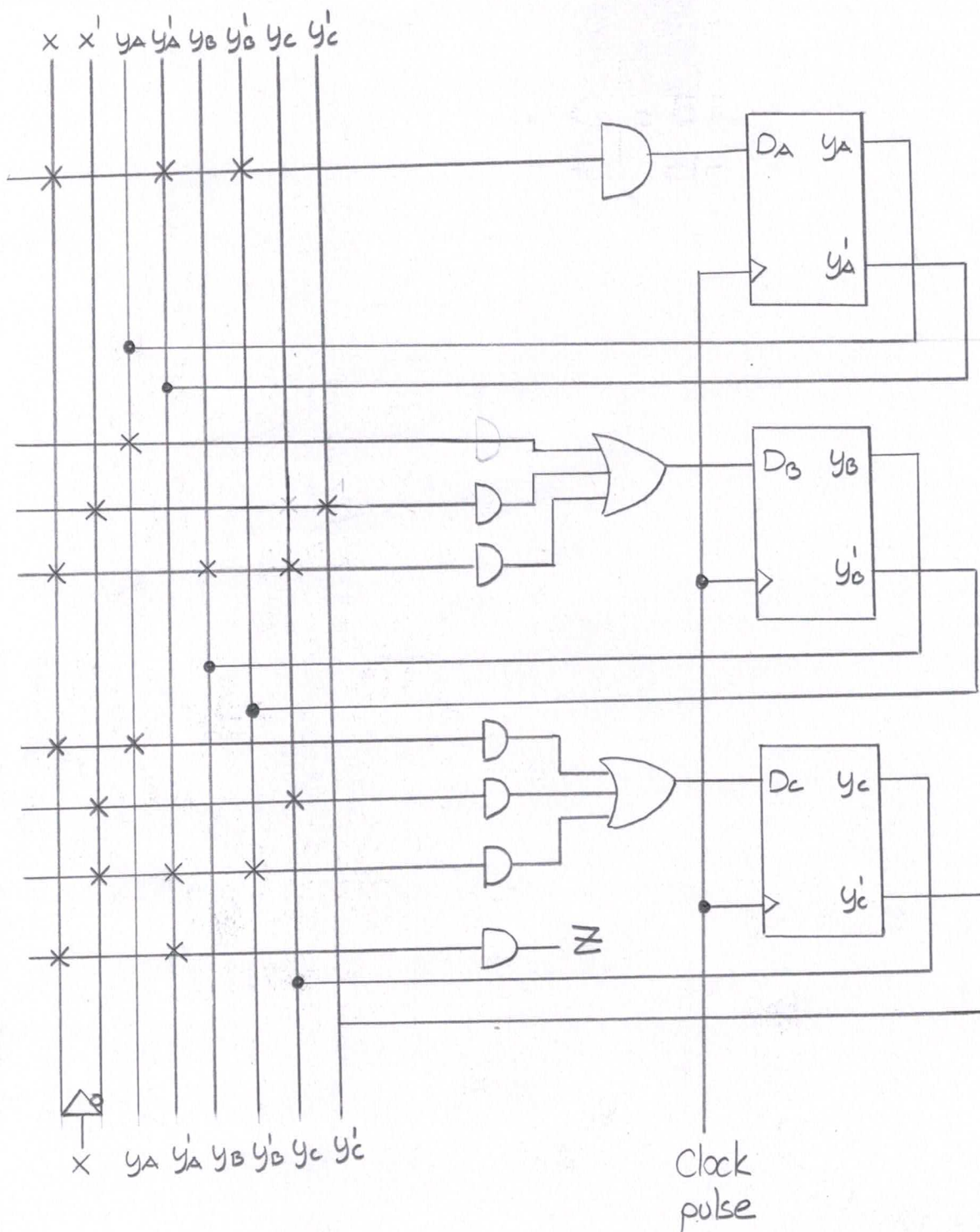

Now ;

-we check if the sequential circuit is locked or not

-when the state machine goes to the unused states

x	y <sub>A</sub>	y <sub>B</sub>	y <sub>C</sub>	y <sub>A</sub>	y <sub>B</sub>	y <sub>C</sub>
0	1	0	1	0	1	1
1	1	0	1	0	1	1
0	1	1	0	0	1	0
1	1	1	0	0	1	1
0	1	1	1	0	1	1
1	1	1	1	0	1	1

⇒ it returns to one of the used states

Hence ;

-the state machine is NOT a locked type,  
that is ;

(1) it is self-correcting

b. We again construct the extended state  
table

X	y <sub>A</sub>	y <sub>B</sub>	y <sub>C</sub>	Y <sub>A</sub>	Y <sub>B</sub>	Y <sub>C</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>	z
0	0	0	0	0	1	1	0	d	1	d	1	d	0
1	0	0	0	1	0	0	1	d	0	d	0	d	1
0	0	0	1	0	0	1	0	d	0	d	d	0	0
1	0	0	1	1	0	0	1	d	0	d	d	1	1
0	0	1	0	0	1	0	0	d	d	0	0	d	0
1	0	1	0	0	0	0	0	d	d	1	0	d	1
0	0	1	1	0	0	1	0	d	d	1	d	0	0
1	0	1	1	0	1	0	0	d	d	0	d	1	1
0	1	0	0	0	1	0	d	1	1	d	0	d	0
1	1	0	0	0	1	1	d	1	1	d	1	d	0

J <sub>A</sub> , K <sub>A</sub>		y <sub>B</sub> y <sub>C</sub>			
		00	01	11	10
x y <sub>A</sub>	00	.	.	.	d
	01	d	d	d	d
	11	d	d	d	d
	10	1	1	.	.

J <sub>B</sub> , K <sub>B</sub>		y <sub>B</sub> y <sub>C</sub>			
		00	01	11	10
x y <sub>A</sub>	00	1	.	d	d
	01	1	d	d	d
	11	1	d	d	d
	10	.	.	d	d

$$J_A = x y_B$$

$$J_A = x y_B', \quad K_A = 1$$

$$K_A =$$

$$J_B = y_A + x' y_C$$



xy <sub>A</sub>	y <sub>B</sub> y <sub>C</sub>			
	00	01	11	10
00	d	d	1	.
01	d	d	d	d
11	d	d	d	d
10	d	d	.	1

$$K_B = x'y_c + xy_c'$$


$$= x \oplus y_c$$

xy <sub>A</sub>	y <sub>B</sub> y <sub>C</sub>			
	00	01	11	10
00	1	d	d	.
01	.	d	d	d
11	1	d	d	d
10	.	d	d	.

$$J_c = xy_A + x'y'_Ay_B$$

xy <sub>A</sub>	y <sub>B</sub> y <sub>C</sub>			
	00	01	11	10
00	d	.	.	d
01	d	d	d	d
11	d	d	d	d
10	d	1	1	d

$$K_C = X$$

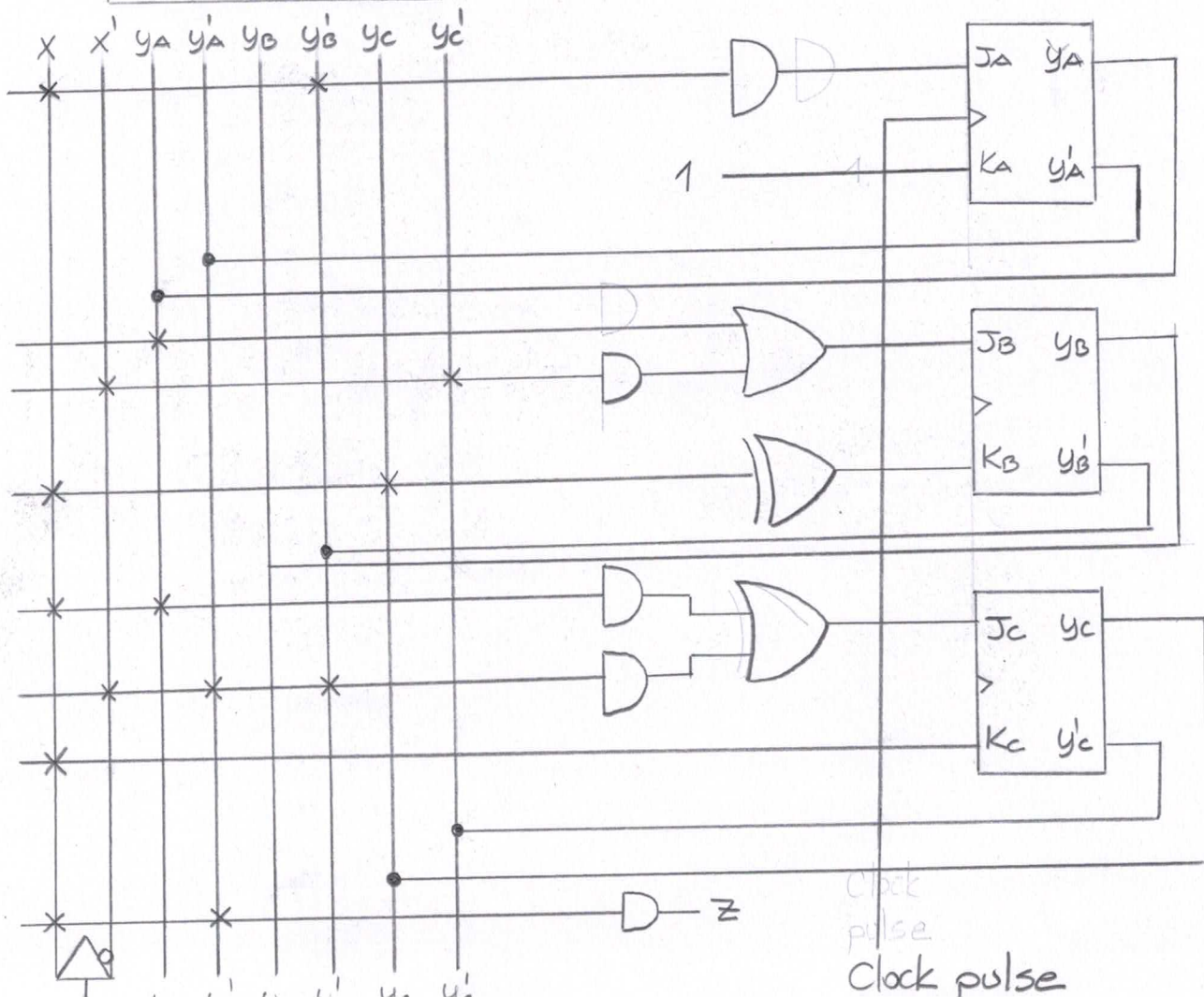

Now ;

- we check if the sequential circuit is locked or not
- when the state machine goes to the unused states

X	$y_A$	$y_B$	$y_C$	$Y_A$	$Y_B$	$Y_C$
0	1	0	1	0	1	0
1	1	0	1	0	1	0
0	1	1	0	0	1	0
1	1	1	0	0	0	1
0	1	1	1	0	0	0
1	1	1	1	0	1	0




it returns to one of the used states

Therefore ;

- the state machine is NOT a locked type one

(b) that is, it is self-correcting

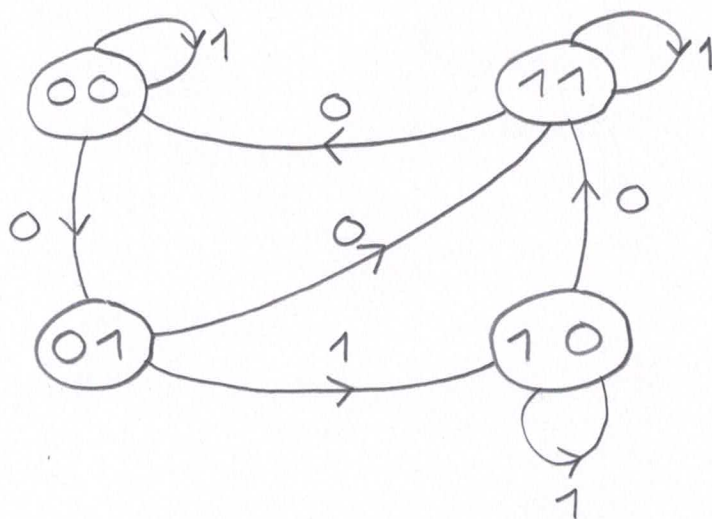**Problem 3)** Consider the following state-diagram





Design the sequential circuit specified by the state diagram depicted above using T type flip-flops.

**Solution.** We construct the extended state table

X	$y_A$	$y_B$	$Y_A$	$Y_B$	$T_A$	$T_B$
0	0	0	0	1	0	1
1	0	0	0	0	0	0
0	0	1	1	1	1	0
1	0	1	1	0	1	1
0	1	0	1	1	0	1
1	1	0	1	0	0	0
0	1	1	0	0	1	1
1	1	1	1	1	0	0

$x \backslash y_A y_B$	00	01	11	10
0		1	1	
1		1		

$$T_A = x'y_B + y_A y_B$$

$x \backslash y_A y_B$	00	01	11	10
0	1		1	1
1		1		

$$T_B = x'y_B + x'y_A + xy_A y_B$$

