

Selected Problems - VI

Problem 1) Using half adders and/or full adders


- Design a four-bit combinational circuit incrementer (a circuit that adds 1 to a four-bit binary number)
- Design a four-bit combinational circuit decrementer (a circuit that subtracts 1 from a four-bit binary number)

Solution.

a. We consider

$$\begin{array}{r}
 X_3 \ X_2 \ X_1 \ X_0 \\
 + \ 0 \ 0 \ 0 \ 1 \\
 \hline
 C_3 \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}$$

Hence;

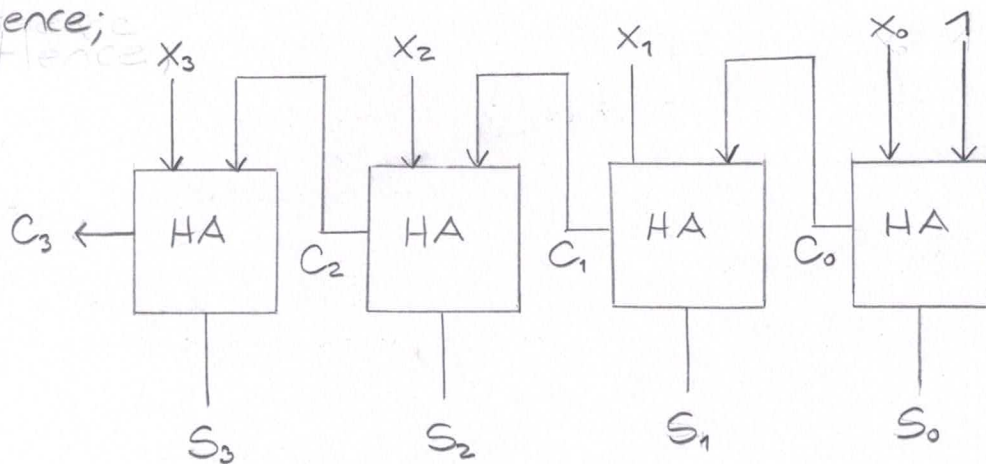

b. We consider

$$\begin{array}{r}
 X_3 \ X_2 \ X_1 \ X_0 \\
 - \ 0 \ 0 \ 0 \ 1 \\
 \hline
 \end{array}$$

-now employing the technique of 2's complement, we shall redefine subtraction as follows

$$\begin{array}{r}
 X_3 \ X_2 \ X_1 \ X_0 \\
 + \ 2's \ complement \ of \ (0001) \\
 \hline
 \end{array}$$


-and we calculate

$$\begin{aligned}
 2's \text{ complement of } 0001 &= 1's \text{ complement of } 0001 \\
 &+ 0001 \\
 &= 1110 + 0001 \\
 &= 1111
 \end{aligned}$$

Therefore ;


$$\begin{array}{r}
 X_3 \ X_2 \ X_1 \ X_0 \\
 0 \ 0 \ 0 \ 1 \\
 \hline
 \end{array}
 =
 \begin{array}{r}
 X_3 \ X_2 \ X_1 \ X_0 \\
 1 \ 1 \ 1 \ 1 \\
 + \\
 \hline
 \end{array}$$

$C_3 \quad S_3 \ S_2 \ S_1 \ S_0$

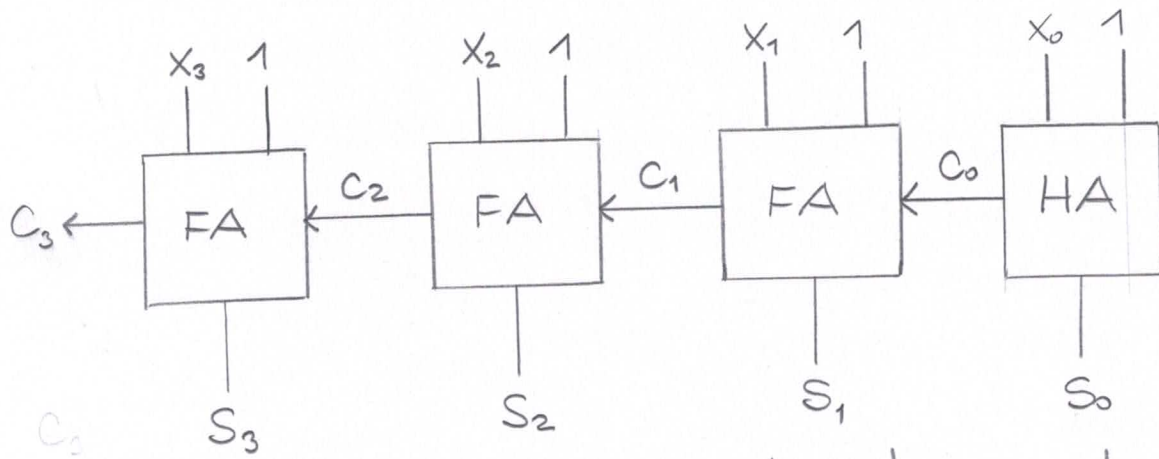

 Problem 2) Design a combinational circuit that compares two four-bit numbers to check if they are equal. The circuit output is equal to 1 if the two numbers are equal and 0 otherwise.


Solution. Note that we shall check if two single bits are equal or not by XNOR'ing them, that is



Therefore ;

- we shall XNOR each bit of the four-bit number with the corresponding bit of the other four-bit number and then AND all four results

 - we consider to compare $X_3 X_2 X_1 X_0$ and $Y_3 Y_2 Y_1 Y_0$



$$F(X_3, \dots, X_0, Y_3, \dots, Y_0) = (X_0 \oplus Y_0)' \cdot (X_1 \oplus Y_1)' \cdot (X_2 \oplus Y_2)' \cdot (X_3 \oplus Y_3)'$$

Problem 3) Design a four-input priority encoder with inputs D_0, D_1, D_2 , and D_3 such that input D_0 has the highest priority and input D_3 has the lowest priority.

Solution. We shall list the truth table of the priority encoder as follows

D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	d	d	0
1	d	d	d	0	0	1
0	1	d	d	0	1	1
0	0	1	d	1	0	1
0	0	0	1	1	1	1

where V denotes the valid bit indicator that is set to 1 when one or more inputs are equal to 1.

$D_2 D_3$	00	01	11	10
$D_0 D_1$				
00	0	1	1	1
01				
11				
10				


$$x = D_0' D_1' D_2$$

$D_2 D_3$	00	01	11	10
$D_0 D_1$				
00	0	1		
01	1	1	1	1
11				
10				

$$y = D_0' D_2 + D_0' D_1$$

and

$$V = D_0 + D_1 + D_2 + D_3$$

 

Problem 4) Implement a full adder with two 4-to-1-line multiplexers.

Solution. We know that

$$\begin{aligned}
 S &= X \oplus Y \oplus C_{in} \\
 &= (x'y + xy')' C_{in} + (x'y + xy') C_{in}' \\
 &= x'y' C_{in} + xy C_{in} + x'y C_{in}' + xy' C_{in}'
 \end{aligned}$$

and

$$C = (X \oplus Y) C_{in} + XY$$

$$= (X'Y + XY') C_{in} + XY$$

$$= X'Y C_{in} + XY' C_{in} + XY$$


-we shall select inputs X and Y as the control inputs of the 4-to-1-line multiplexers

Therefore ;

$$S = m_0 \cdot C_{in} + m_3 \cdot C_{in} + m_1 \cdot C_{in}' + m_2 \cdot C_{in}'$$

$$C = m_1 \cdot C_{in} + m_2 \cdot C_{in} + m_3 \cdot 1 + m_0 \cdot 0$$

where m_i 's, $i=0,1,2,3$ are the minterms wrt the variables X and Y

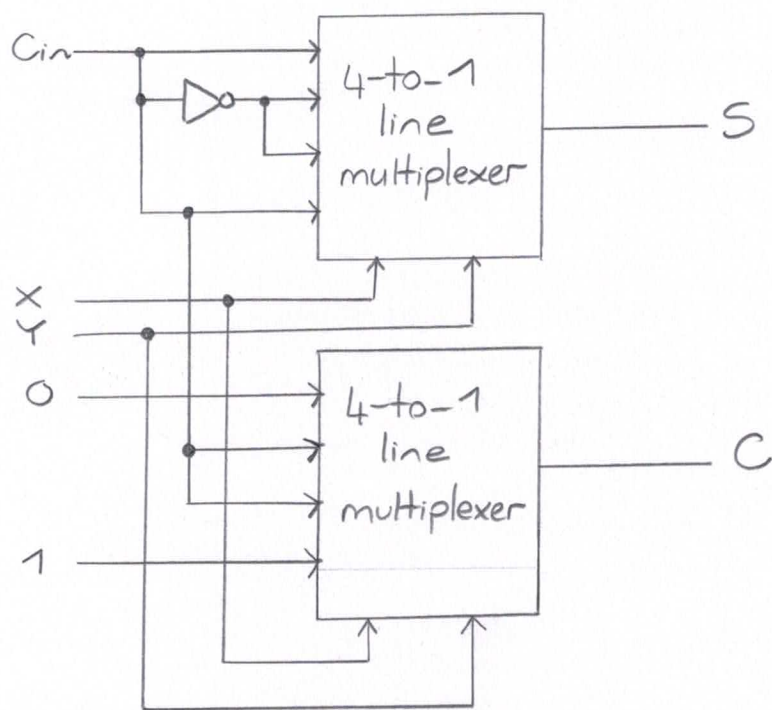

Problem 5) Tabulate the PLA programming table for the four Boolean functions listed below. Minimize the number of product terms.

$$A(x,y,z) = \sum m(1,2,4,6)$$

$$B(x,y,z) = \sum m(0,1,6,7)$$

$$C(x,y,z) = \sum m(2,6)$$

$$D(x,y,z) = \sum m(1,2,3,5,7)$$

Solution.

$x \backslash yz$	00	01	11	10
0	0	1	0	1
1	1	0	0	1

$x \backslash yz$	00	01	11	10
0	1	1	0	0
1	0	0	1	1

$$A(x,y,z) = yz' + xz' + x'y'z$$

$$B(x,y,z) = x'y' + xy$$

$$A'(x,y,z) = x'y'z' + xz + yz$$

$$B'(x,y,z) = x'y + xy'$$

$x \backslash yz$	00	01	11	10
0	0	0	0	1
1	0	0	0	1

$x \backslash yz$	00	01	11	10
0	0	1	1	1
1	0	1	1	0

$$C(x,y,z) = yz'$$

$$D(x,y,z) = x'y + z$$

$$C'(x,y,z) = z + xy' + x'y'z'$$

$$D'(x,y,z) = xz' + x'y'z'$$

- we find that we need to utilize 6 product terms to implement these functions

Remark. The set of (A', B', C', D) can also be considered as only 6 terms are required.

Product terms	x	y	z	(T) A	(C) B	(T) C	(T) D
yz'	-	1	0	1	-	1	-
xz'	1	-	0	1	-	-	1
$x'y$	0	1	-	-	1	-	1
xy'	1	0	-	-	1	1	-
z	-	-	1	-	-	1	1
$x'y'z'$	0	0	1	1	-	1	1

PLA

programming

table

Problem 6) Using an appropriate size ROM, design a combinational circuit that squares a 3-bit number.

Solution. The largest 3-bit number is 7 and its square is 49 which needs at least 6 bits to represent in binary form. Let us now tabulate the truth table

A	B	C	S_5	S_4	S_3	S_2	S_1	S_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

- we find that $S_1 = 0$ for all cases

Hence,

- we require an 8×5 ROM

$$S_0 = \sum m(1, 3, 5, 7)$$


$$S_1 = 0$$

$$S_2 = \sum m(2, 6, 7)$$

$$S_3 = \sum m(3, 5)$$

$$S_4 = \sum m(4, 5, 7)$$

$$S_5 = \sum m(6, 7)$$

 

Problem 7) The following is a truth table of a three-input, four-output combinational circuit:

x	y	z	A	B	C	D
0	0	0	0	1	0	0
0	0	1	1	1	1	1
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	0	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1

Tabulate the PAL programming table for the circuit and mark the fuse map in the logic circuit diagram of the PAL.

Solution. We have

$$A(x, y, z) = \sum m(1, 2, 4, 6)$$

$$B(x, y, z) = \sum m(0, 1, 3, 6, 7)$$

$$C(x, y, z) = \sum m(1, 2, 4, 6, 7)$$

$$D(x, y, z) = \sum m(1, 2, 3, 5, 7)$$

x \ yz	00	01	11	10
0		1		1
1	1			1

x \ yz	00	01	11	10
0	1	1	1	
1			1	1

$$A(x, y, z) = yz' + x'y'z + xy'z'$$

$$B(x, y, z) = x'y' + yz + xy$$

x \ yz	00	01	11	10
0		1		1
1	1		1	1

x \ yz	00	01	11	10
0		1	1	1
1		1	1	

$$C(x, y, z) = yz' + x'y'z + xy'z'$$

$$D(x, y, z) = z + x'y$$

$$+ xy$$

$$= A + xy$$


- it appears that A can be used to express the Boolean function, C

(1) thus, the function output of A can be sent as an additional input in the feedback path

Hence;

- we are able to implement each Boolean function with AT MOST 3 product terms

Product term	Inputs x y z A	Outputs
1	- 1 0 -	$A = yz' + x'y'z + xy'z'$
2	0 0 1 -	
3	1 0 0 -	
1	0 0 - -	$B = x'y' + yz + xy$
2	- 1 1 -	
3	1 1 - -	
1	- - - 1	$C = A + xy$
2	1 1 - -	
3	0 - - -	
1	- - 1 -	$D = z + x'y$
2	0 1 - -	
3	0 - - -	

 

PAL circuit diagram