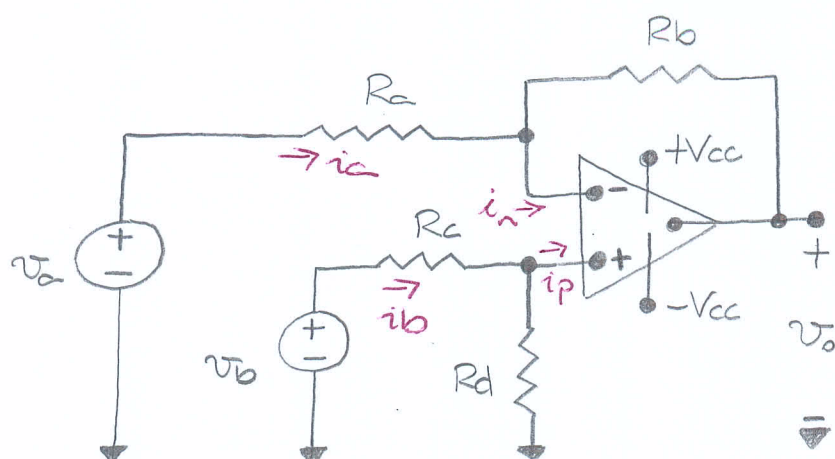


Selected Problems II

Problem 1) The resistors in a difference amplifier shown as



are

$$R_a = 20\text{k}\Omega, R_b = 80\text{k}\Omega, R_c = 47\text{k}\Omega, R_d = 33\text{k}\Omega$$

The signal voltages v_a and v_b are

$$v_a = 0.45\text{V}, v_b = 0.9\text{V}$$

and $V_{cc} = \pm 9\text{V}$. Assume that the op amp is ideal.

- Find v_o .
- What is the resistance seen by the signal source v_a ?
- What is the resistance seen by the signal source v_b ?

Solution.

a. We have $v_p = v_n$ and $i_p = i_n = 0$

KCL at noninverting input:

$$\frac{v_p - 0.9}{47\text{k}} + \frac{v_p}{33\text{k}} = 0 \Rightarrow 33(v_p - 0.9) + 47v_p = 0$$

$$\Rightarrow 80v_p = 0.9 \cdot 33 \Rightarrow v_p = 0.3712\text{V} \Rightarrow v_n = 0.3712$$

KCL at inverting input:

$$\frac{0.3712 - 0.45}{20\text{k}} + \frac{0.3712 - v_o}{80\text{k}} = 0 \Rightarrow 5 \cdot 0.3712 - 0.45 = v_o$$

$$\Rightarrow v_o = 1.4062\text{V}$$

- we then have

$$i_c = \frac{0.45 - 0.3712}{20k} = 0.0039 \text{ mA}$$


$$i_b = \frac{0.9 - 0.3712}{47k} = 0.0113 \text{ mA}$$

tence ;

$$R_{\text{seen by } v_c} = \frac{v_c}{i_c} = \frac{0.45}{0.0039 \cdot 10^{-3}} = 115.3846 \text{ k}\Omega$$

$$R_{\text{seen by } v_b} = \frac{v_b}{i_b} = \frac{0.9}{0.0113 \cdot 10^{-3}} = 79.6460 \text{ k}\Omega$$

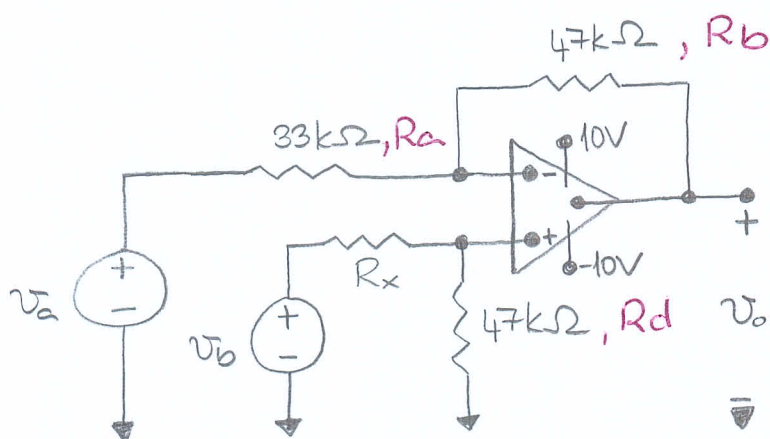Problem 2) In the difference amplifier shown as



What range of values of R_x yields a CMRR ≥ 750 ?

Solution. We have

$$\text{CMRR} = \left| \frac{A_{dm}}{A_{cm}} \right| \geq 750$$

- it follows from the difference amplifier formulation :

$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_x + R_d)} v_b - \frac{R_b}{R_a} v_a$$

- defining

$$v_{dm} = v_b - v_a$$

$$v_{cm} = (v_a + v_b)/2$$

\Rightarrow

$$v_a = v_{cm} - \frac{1}{2} v_{dm}$$

$$v_b = v_{cm} + \frac{1}{2} v_{dm}$$

Hence;

$$v_o = \frac{R_d (R_a + R_b)}{R_a (R_x + R_d)} \left(v_{cm} + \frac{1}{2} v_{dm} \right) - \frac{R_b}{R_a} \left(v_{cm} - \frac{1}{2} v_{dm} \right)$$
$$= A_{cm} v_{cm} + A_{dm} v_{dm}$$

where

$$A_{cm} = \frac{R_d (R_a + R_b)}{R_a (R_x + R_d)} - \frac{R_b}{R_a} = \frac{R_a R_d - R_b R_x}{R_a (R_x + R_d)}$$

$$A_{dm} = \frac{R_d (R_a + R_b)}{2 R_a (R_x + R_d)} + \frac{R_b}{2 R_a} = \frac{R_d (R_a + R_b) + R_b (R_x + R_d)}{2 R_a (R_x + R_d)}$$

-we now calculate

$$A_{cm} = \frac{33k \cdot 47k - 47k \cdot R_x}{33k (R_x + 47k)} = \frac{47 (33 - R_x)}{33 (R_x + 47)}$$

$$A_{dm} = \frac{47k (33k + 47k) + 47k (R_x + 47k)}{2 \cdot 33k \cdot (R_x + 47k)}$$

$$= \frac{47 (R_x + 120)}{66 (R_x + 47)}$$

$$\frac{A_{dm}}{A_{cm}} = \frac{47 (R_x + 120)}{206 (R_x + 47)} \cdot \frac{33 (R_x + 47)}{47 (33 - R_x)} \geq 750$$

$$\Rightarrow R_x + 120 \geq 33 \cdot 1500 - 1500 R_x$$

$$\Rightarrow 1501 R_x \geq 49380$$

$$\Rightarrow R_x \geq 32.8981 k\Omega$$

OR

$$\frac{A_{dm}}{A_{cm}} = \frac{R_x + 120}{2(33 - R_x)} \leq -750$$


$$\Rightarrow R_x + 120 \leq -33.1500 + 1500R_x$$

$$\Rightarrow R_x \leq 33.1021 \text{ k}\Omega$$

Hence ;

$$32.8981 \text{ k}\Omega \leq R_x \leq 33.1021 \text{ k}\Omega$$

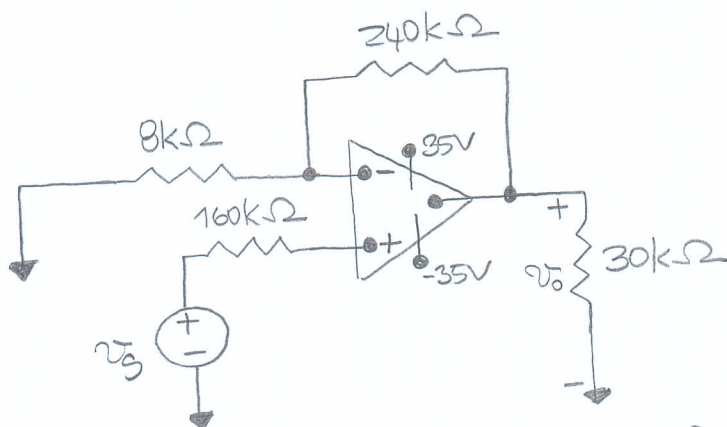
Problem 3) The op amp in the noninverting amplifier circuit has an input resistance of $440 \text{ k}\Omega$, an output resistance of $5 \text{ k}\Omega$, and an open-loop gain of 10^5 .



Assume that the op amp is operating in its linear region.

- Calculate the voltage gain (v_o/v_g).
- Find the inverting and noninverting input voltages v_n and v_p (in millivolts) if $v_g = 1 \text{ V}$.
- Calculate the difference ($v_p - v_n$) in microvolts when $v_g = 1 \text{ V}$.
- Find the current drain in picoamperes on the signal source when $v_g = 1 \text{ V}$.

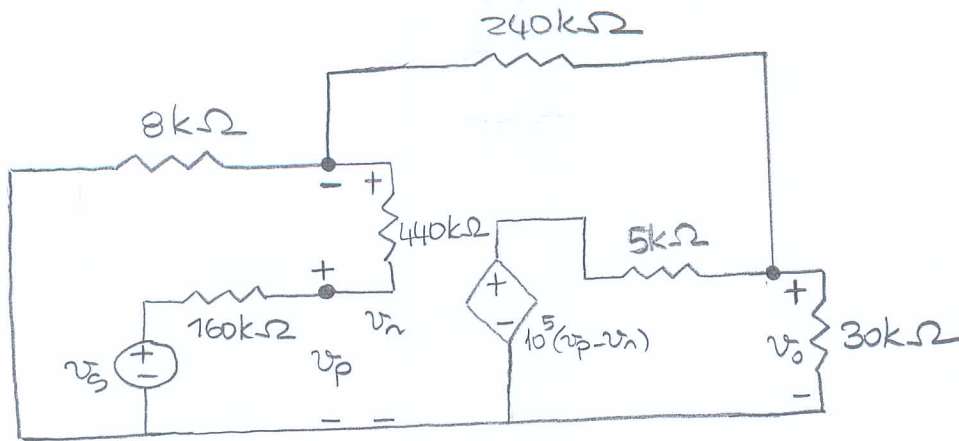Solution. We first redraw the op amp circuit using the realistic model of the op amp as follows



2.

KCL at noninverting input:

$$\frac{v_p - v_s}{160k} + \frac{v_p - v_n}{440k} = 0 \Rightarrow 15v_p - 11v_s - 4v_n = 0$$

(11) (4)

KCL at inverting input:

$$\frac{v_n}{8k} + \frac{v_n - v_o}{240k} + \frac{v_n - v_p}{440k} = 0 \Rightarrow 347v_n - 11v_o - 6v_p = 0$$

(330) (11) (6)

KCL at output terminal:

$$\frac{v_o - v_n}{240k} + \frac{v_o - 10^5(v_p - v_n)}{5k} + \frac{v_o}{30k} = 0$$

(48) (8)

$$\Rightarrow 57v_o - 48 \cdot 10^5 v_p + 48 \cdot 10^5 v_n = 0$$

-we have

$$\left. \begin{array}{l} 2/15 v_p - 4v_n = 11v_s \\ 5/-6 v_p + 347v_n = 11v_o \end{array} \right\} \Rightarrow 1727v_n = \frac{2}{2} v_s + \frac{5}{5} v_o$$

$$\Rightarrow v_n = \frac{2v_s + 5v_o}{157}, \quad v_p = \frac{4(2v_s + 5v_o)}{15 \cdot 157} + \frac{11}{15} v_s$$

$$= \frac{1735v_s + 20v_o}{15 \cdot 157}$$

-then we have

$$57v_o - 48 \cdot 10^5 \left(\frac{1735v_3 + 20v_o}{15.157} - \frac{2v_3 + 5v_o}{157(15)} \right)$$

$$\Rightarrow 134235v_o - 81840 \cdot 10^5 v_3 + 2640 \cdot 10^5 v_o = 0$$

$$\Rightarrow 264134235v_o = 81840 \cdot 10^5 v_3$$

$$\Rightarrow \frac{v_o}{v_3} = 30.9842$$

b.

$$v_o = 30.9842 \cdot 1 = 30.9842 \text{ V}$$

$$v_p = \frac{1735 \cdot 1 + 20 \cdot 30.9842}{2355} = 999.8658 \text{ mV}$$


$$v_n = \frac{2 \cdot 1 + 5 \cdot 30.9842}{157} = 999.4968 \text{ mV}$$

c. $v_p - v_n = 999.8658 - 999.4968$
 $= 369.0021 \text{ } \mu\text{V}$

d. $i_g = \frac{(1000 - 999.8658) \cdot 10^{-3}}{160 \cdot 10^3}$

$$= 838.6412 \text{ pA}$$

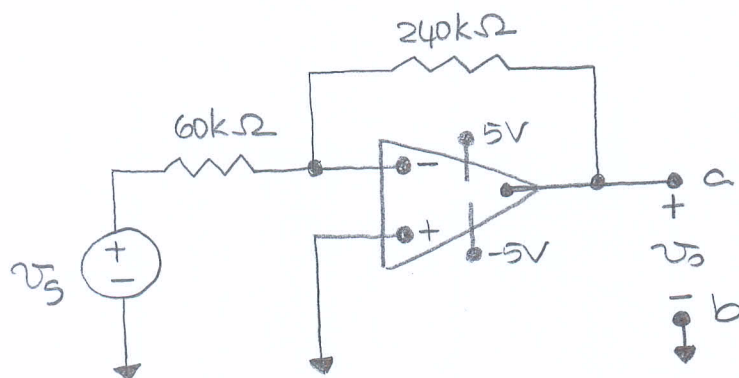Problem 4) Consider the following inverting amplifier circuit




a. Find the Thévenin equivalent circuit with respect to the output terminals a, b. The dc signal source PS 2.6

has a value of 150 mV . The op amp has an input resistance of 750Ω and an open-loop gain of $5 \cdot 10^4$.

B. What is the output resistance of the inverting amplifier?

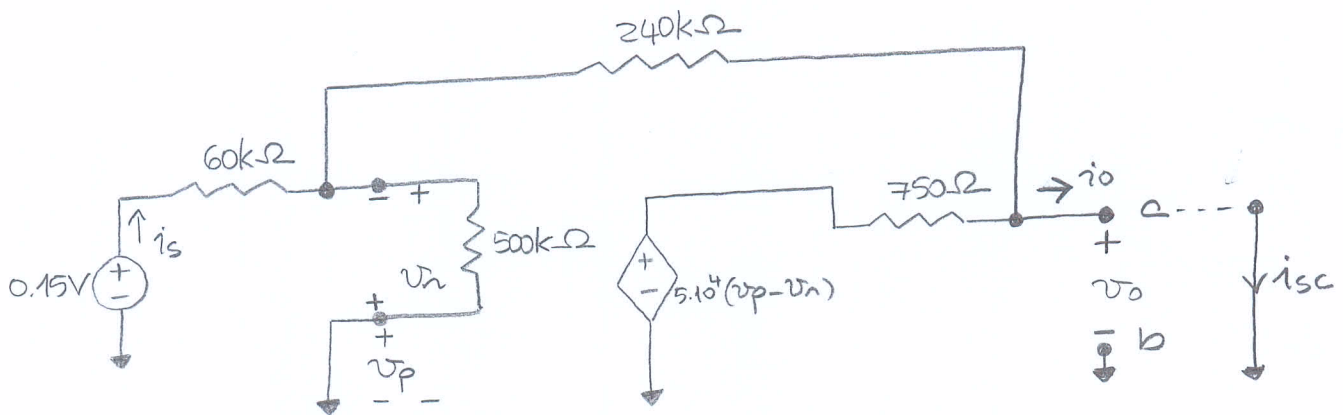C. What is the resistance (in ohms) seen by the signal source v_s when the load at the terminals a, b is 150Ω ?

Solution. We consider the realistic model of the op amp



$$v_{Th} \equiv v_o, \quad v_p = 0$$

KCL at inverting input:

$$\frac{v_n - 0.15}{60k} + \frac{v_n - v_{Th}}{240k} + \frac{v_n}{500k} = 0$$

(100) (25) (12)

$$\Rightarrow 137v_n - 15 - 25v_{Th} = 0 \quad \Rightarrow \quad v_n = \frac{25v_{Th} + 15}{137}$$

KCL at output terminal:

$$\frac{v_{Th} - v_n}{240k} + \frac{v_{Th} - 5 \cdot 10^4 (v_p - v_n)}{750} = 0$$

(25) (8k)

$$\Rightarrow 8025v_{Th} + 4 \cdot 10^8 v_n = 0$$

$$\Rightarrow 8025 v_{Th} + 4 \cdot 10^8 \frac{25 v_{Th} + 15}{137} = 0$$

$$\Rightarrow v_{Th} \approx -\frac{15}{25} = -0.6 \text{ V}$$

then we find the short-circuit current, i_{sc}

KCL at inverting input:

$$\frac{v_n - 0.15}{60k} + \frac{v_n}{240k} + \frac{v_n}{500k} = 0$$

(100) (25) (12)


$$\Rightarrow 137 v_n = 15 \Rightarrow v_n = 0.1095 \text{ V}$$

$$\Rightarrow i_{sc} = \frac{-5 \cdot 10^4 \cdot 0.1095}{750} + \frac{0.1095}{240k} \approx -7.3 \text{ A}$$

Hence;

$$R_{Th} = \frac{v_{Th}}{i_{sc}} = \frac{-0.6}{-7.3} = 82.2 \text{ m}\Omega$$


we have

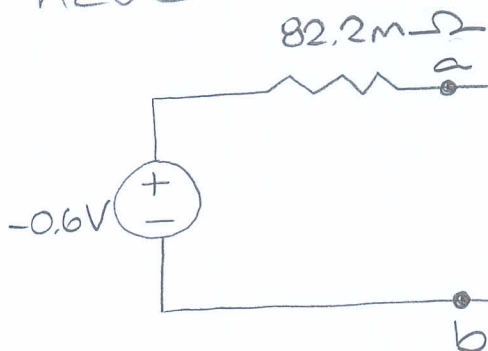

The output resistance is the same as the Thévenin resistance, i.e.

$$R_o = R_{Th} = 82.2 \text{ m}\Omega$$

we consider

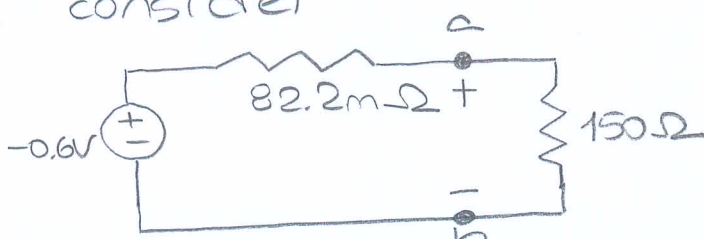

$$v_{ab} = \frac{150}{150 + 0.0822} (-0.6)$$

$$= -0.5997 \text{ V} \quad \text{PS 2.8}$$

-then we apply KCL at inverting input:

$$\frac{v_n - 0.15}{60k} + \frac{v_n + 0.5937}{240k} + \frac{v_n}{500k} = 0$$

(100) (25) (12)

$$\Rightarrow 137v_n - 15 + 14.9918 = 0 \quad \Rightarrow v_n = 54.745 \mu A$$

$$i_s = \frac{0.15 - 54.745 \cdot 10^{-6}}{60k} = 2.4991 \mu A$$

Thus;

$$R_s = \frac{0.15}{2.4991 \cdot 10^{-6}} = 60.022 k\Omega$$