

EEEN 202
Electrical and Electronic Circuits II

MIDTERM EXAM, Spring 2014-2015

Duration: 100 minutes

Problem 1 (25 points)

There is no energy stored in the circuit in Figure P1 at the time the source is energized.

- Find the s-domain expression for $V_o(s)$. (10 points)
- Use the s-domain expression derived in (a) to predict the initial- and final-values of $v_o(t)$. (5 points)
- Find the time domain expression for $v_o(t)$ for $t \geq 0$. (10 points)

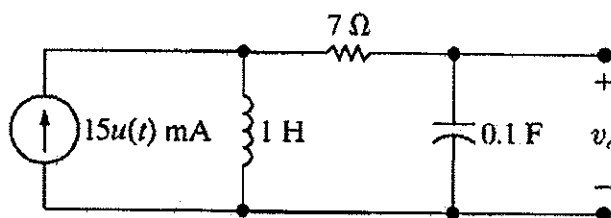


Figure P1

Problem 2) (25 points)

The op amp in the noninverting amplifier circuit of Figure P2 has an input resistance of $440\text{ k}\Omega$, an output resistance of $5\text{ k}\Omega$, and an open-loop gain of $100,000$. Assume that the amplifier is operating in its linear region.

- Calculate the voltage gain (v_o / v_g) of the amplifier. (15 points)
- Find the inverting and noninverting input voltages v_n and v_p in microvolts when $v_g = 1$ V. (10 points)

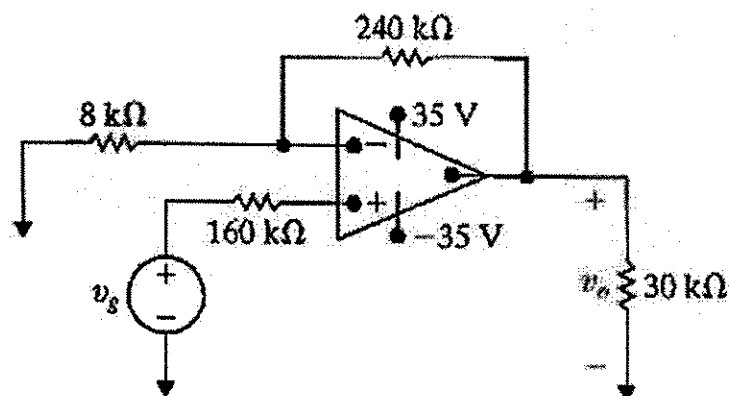


Figure P2

Problem 3) (25 points)

Consider the following circuit in Figure P3.

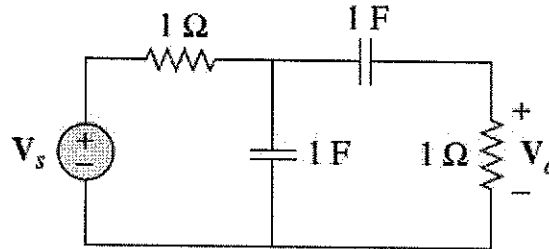


Figure P3

- Derive the transfer function of the filter, that is $\frac{V_o(s)}{V_s(s)}$. (10 points)
- Determine the type of the filter. Justify your answer. (5 points)
- Calculate the cutoff and center frequencies, bandwidth and quality factor of the filter. (10 points)

Problem 4) (25 points)


Design a passive bandreject filter with a quality factor of $\frac{2}{3}$ and a center frequency of 4 krad/sec using an 80nF capacitor.

- Draw your circuit by labeling the component values and output voltage. (10 points)
- Derive the transfer function of the bandreject filter. (10 points)
- For the passive bandreject filter designed in part (a), calculate the bandwidth and the two cut off frequencies. (5 points)


EEEN 202 Midterm Exam

- Solutions -

1) s-domain equivalent circuit:

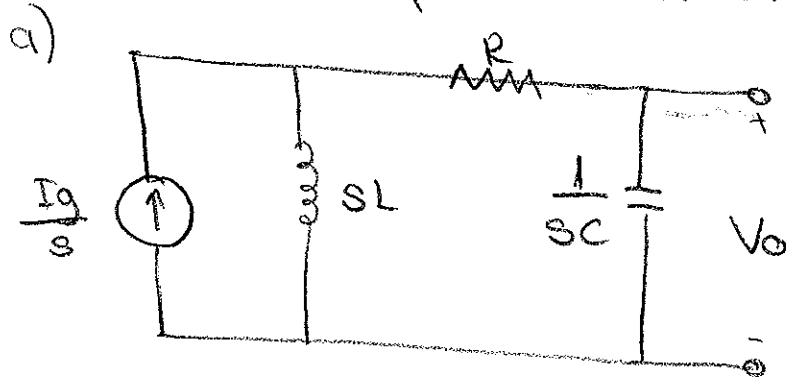

Applying source transformation:

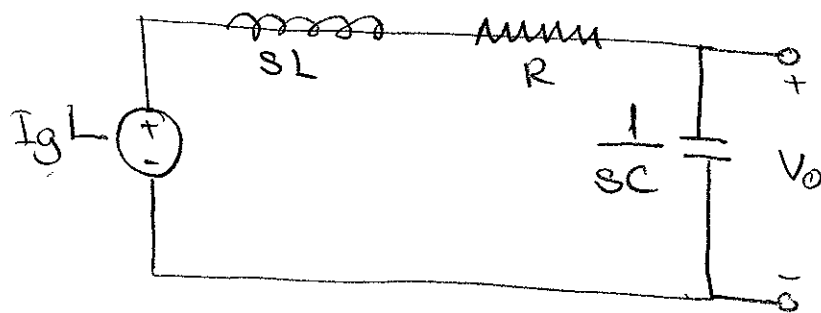

$$V_o = \frac{L I_g}{\left(sL + R + \frac{1}{sC}\right)} \times \frac{1}{sC} = \frac{L I_g}{\frac{LCs^2 + RCs + 1}{sC}} \times \frac{1}{sC}$$

$$= \frac{L I_g}{LCs^2 + RCs + 1} = \frac{I_g / C}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$= \frac{(0.015 / 0.1)}{s^2 + \left(\frac{7}{1}\right)s + \left(\frac{1}{1 \cdot 0.1}\right)} = \frac{0.15}{s^2 + 7s + 10} = \frac{0.15}{(s+2)(s+5)}$$

$$V_o(s) = \frac{0.15}{s^2 + 7s + 10}$$

b) Using initial-value theorem:

$$\lim_{t \rightarrow 0^+} v_o(t) = \lim_{s \rightarrow \infty} s V_o(s) = \lim_{s \rightarrow \infty} \frac{0.15s}{s^2 + 7s + 10} = 0$$

$$\boxed{v_o(0^+) = 0}$$

Using final-value theorem:

$$\lim_{t \rightarrow \infty} v_o(t) = \lim_{s \rightarrow 0} s V_o(s) = \lim_{s \rightarrow 0} \frac{0.15s}{s^2 + 7s + 10} = 0$$

$$\boxed{v_o(\infty) = 0}$$

$$c) V_o(s) = \frac{0.15}{(s+2)(s+5)} = \frac{K_1}{(s+2)} + \frac{K_2}{(s+5)}$$

$$K_1 = (s+2) V_o(s) \Big|_{s=-2} = \frac{0.15}{(s+5)} \Big|_{s=-2} = \frac{0.15}{3} = 0.05$$


$$K_2 = (s+5) V_o(s) \Big|_{s=-5} = \frac{0.15}{(s+2)} \Big|_{s=-5} = \frac{0.15}{-3} = -0.05$$

$$V_o(s) = \frac{0.05}{s+2} - \frac{0.05}{s+5} =$$

$$\boxed{v_o(t) = [0.05 e^{-2t} - 0.05 e^{-5t}] u(t) \text{ V}}$$

2)

a)

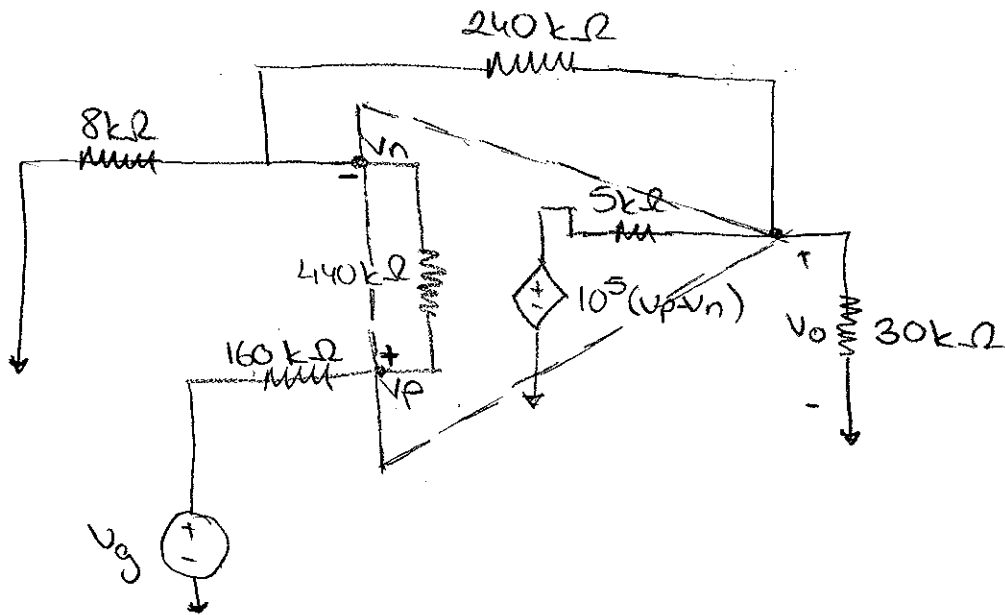

Applying KCL at non-inverting input terminal:

$$\frac{V_p - V_g}{160 \times 10^3} + \frac{V_p - V_n}{440 \times 10^3} = 0$$

$$\frac{11V_p - 11V_g + 4V_p - 4V_n}{1760 \times 10^3} = 0 \Rightarrow 15V_p - 4V_n - 11V_g = 0 \quad (I)$$

Applying KCL at inverting input terminal:

$$\frac{V_n}{8 \times 10^3} + \frac{V_n - V_o}{240 \times 10^3} + \frac{V_n - V_p}{440 \times 10^3} = 0$$

$$\frac{330V_n + 11V_n - 11V_o + 6V_n - 6V_p}{2640 \times 10^3} = 0 \Rightarrow -6V_p + 347V_n - 11V_o = 0 \quad (II)$$

Applying KCL at output terminal:

$$\frac{V_o - V_n}{240 \times 10^3} + \frac{V_o}{30 \times 10^3} + \frac{V_o - 10^5(V_p - V_n)}{5 \times 10^3} = 0$$

$$\frac{V_o - V_n + 8V_o + 48V_o - 48 \cdot 10^5(V_p - V_n)}{240 \times 10^3} = 0 \Rightarrow -48 \cdot 10^5 V_p + 48 \cdot 10^5 V_n + 57 V_o = 0 \quad (\text{III})$$

Using (I) and (II):

$$15 V_p - 4 V_n - 11 V_g = 0$$

$$6 V_p + 347 V_n - 11 V_o = 0$$

\Rightarrow

$$30 V_p - 8 V_n - 22 V_g = 0$$

$$-30 V_p + 1735 V_n - 55 V_o = 0$$

$$1727 V_n - 22 V_g - 55 V_o = 0$$

$$\Rightarrow 157 V_n - 2 V_g - 5 V_o = 0 \quad (\text{IV})$$

From (IV): $V_n = \frac{2 V_g + 5 V_o}{157} \quad (\text{V})$

From (I): $15 V_p - 4 V_n - 11 V_g = 15 V_p - \frac{8 V_g + 20 V_o}{157} - 11 V_g = 0$

$$\Rightarrow V_p = \frac{1735 V_g + 20 V_o}{157 \cdot 15}$$

Using (V) and (VI) in (III):

$$-48 \cdot 10^5 \left(\frac{1735 V_g + 20 V_o}{157 \cdot 15} \right) + 48 \cdot 10^5 \left(\frac{30 V_g + 75 V_o}{15 \cdot 157} \right) + 57 V_o = 0$$

$$\Rightarrow (-960 \times 10^5 + 3600 \times 10^5 + 134235) V_o = (83280 \cdot 10^5 - 1440 \times 10^5) V_g$$

$$(2640 \times 10^5 + 134235) V_o = 81840 \times 10^5 V_g$$

$$264134235 V_o = 8184000000 V_g$$


$$\frac{V_o}{V_g} = \frac{8184000000}{264134235} = 30.98 \Rightarrow \boxed{\frac{V_o}{V_g} = 30.98}$$

$$b) V_o = 30.98 \cdot V_g = 30.98 \text{ V}$$

$$V_n = \frac{2 V_g + 5 V_o}{157} = \frac{2 + 154.9}{157} = 0.99936 \text{ V} \Rightarrow \boxed{V_n = 999.36 \text{ mV}}$$

$$V_p = \frac{1735 V_g + 20 V_o}{157.15} = \frac{1735 + 619.6}{2355} = 0.99983 \text{ V} \Rightarrow \boxed{V_p = 999.83 \text{ mV}}$$

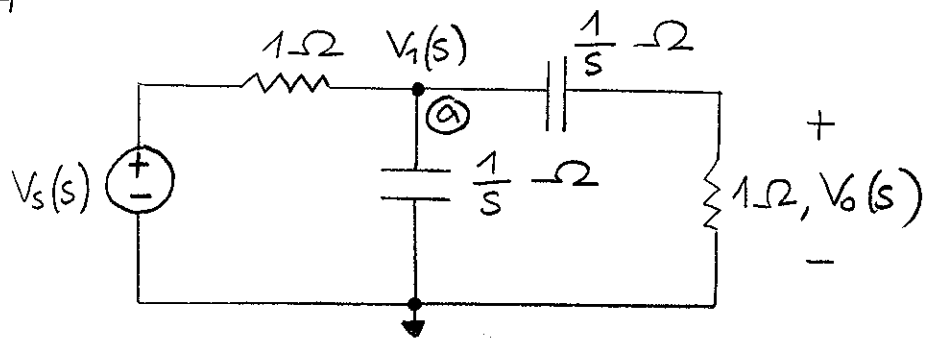Problem 3) We shall first draw the s-domain equivalent circuit



2. We consider KCL at node (a) :

$$\frac{V_1(s) - V_s(s)}{1} + \frac{V_1(s)}{1/s} + \frac{V_1(s)}{(1/s) + 1} = 0$$

$$\Rightarrow V_1(s) - V_s(s) + s V_1(s) + \frac{s V_1(s)}{1+s} = 0$$

$$\Rightarrow \left(1 + s + \frac{s}{1+s}\right) V_1(s) = V_s(s)$$

(05)

$$\Rightarrow \frac{(1+s)^2 + s}{1+s} V_1(s) = V_s(s)$$

$$\Rightarrow V_1(s) = \frac{s+1}{s^2 + 3s + 1} V_s(s)$$

and we also have from voltage division

$$V_0(s) = \frac{1}{(1/s) + 1} V_1(s)$$

$$= \frac{s}{s+1} V_1(s)$$

(03)

Hence ;

$$V_o(s) = \frac{s}{\cancel{s+1}} \frac{\cancel{s+1}}{s^2+3s+1} V_s(s)$$

$$\Rightarrow \frac{V_o(s)}{V_s(s)} = \frac{s}{s^2+3s+1} \triangleq H(s) \quad (02)$$

2. We consider

$$H(j\omega) = \frac{j\omega}{(j\omega)^2+3j\omega+1} = \frac{j\omega}{1-\omega^2+j3\omega} \quad (01)$$

and

$$|H(j\omega)| = \frac{\omega}{\sqrt{(1-\omega^2)^2+9\omega^2}}$$

-we find that

$$|H(j\omega)|_{\omega=0} = 0$$

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = \lim_{\omega \rightarrow \infty} \frac{1}{\sqrt{9 + \left(\frac{1-\omega^2}{\omega}\right)^2}}$$

$$= \lim_{\omega \rightarrow \infty} \frac{1}{\sqrt{9 + \left(\frac{1}{\omega} - \omega\right)^2}}$$

$$= \lim_{\omega \rightarrow \infty} \frac{1}{\sqrt{9 + \omega^2}}$$

$$= 0$$

Therefore;

- the type of the filter is justified to be band-pass, because the magnitude of the transfer function for both low and high frequencies approach zero (02)

Moreover;

- we also find that

$$|H(j\omega)| = \frac{1}{3} \frac{3\omega}{\sqrt{(1-\omega^2)^2 + (3\omega)^2}}$$
$$= \frac{1}{3} \frac{1}{\sqrt{1 + \left(\frac{1-\omega^2}{3\omega}\right)^2}}$$

has its maximum value when $\left(\frac{1-\omega^2}{3\omega}\right)^2 = 0$

$$\Rightarrow \omega = 1 \text{ rad/sec} \triangleq \omega_0 \text{ (center/corner frequency)}$$

and

$$H_{\max} \triangleq H(j\omega_0)$$
$$= H(j)$$
$$= \frac{1}{3}$$

c. We shall consider

$$H(s) = \frac{1}{3} \frac{3s}{s^2 + 3s + 1}$$
$$\triangleq \frac{1}{3} \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$\Rightarrow \beta = 3 \text{ rad/sec (bandwidth)} \quad (02)$$

$$\omega_0^2 = 1 \Rightarrow \omega_0 = 1 \text{ rad/sec} \quad (02)$$

and

$$|H(j\omega_c)| = \frac{1}{3} \frac{1}{\sqrt{1 + \left(\frac{1 - \omega_c^2}{3\omega_c}\right)^2}}$$

$$= \frac{1}{\sqrt{2}} \cdot \frac{1}{3}$$

$$\Rightarrow \left(\frac{1 - \omega_c^2}{3\omega_c}\right)^2 = 1 \Rightarrow 1 - \omega_c^2 = \pm 3\omega_c$$

$$\Rightarrow \omega_c^2 \pm 3\omega_c + 1 = 0$$

$$(02) \quad \omega_{c1} = \frac{-3 + \sqrt{9 + 4 \cdot 1}}{2}, \quad \omega_{c2} = \frac{-3 + \sqrt{9 + 4 \cdot 1}}{2} \quad (02)$$

$$= 0.3028 \text{ rad/sec}$$

$$= 3.3028 \text{ rad/sec}$$

and

$$Q = \frac{\omega_0}{\beta} = \frac{1}{3} \quad (02)$$

Problem 4) We have

$$Q = \frac{\omega_0}{\beta} = \frac{2}{3}, \quad \omega_0 = 4 \text{ k rad/sec}$$

$$\Rightarrow \frac{4 \cdot 10^3}{\beta} = \frac{2}{3} \Rightarrow \beta = 6 \cdot 10^3 \text{ rad/sec}$$

2.


$$\omega_0 = \sqrt{\frac{1}{LC}} \Rightarrow 4 \cdot 10^3 = \sqrt{\frac{1}{L \cdot 80 \cdot 10^{-9}}}$$

$$\Rightarrow 4 \cdot 10^3 = \frac{10^4}{\sqrt{8L}} \Rightarrow 8L = \frac{1}{16}$$

$$\Rightarrow L = 7.8125 \text{ mH} \quad (04)$$

$$\beta = \frac{R}{L} \Rightarrow 6 \cdot 10^3 = \frac{R}{(1/128)}$$
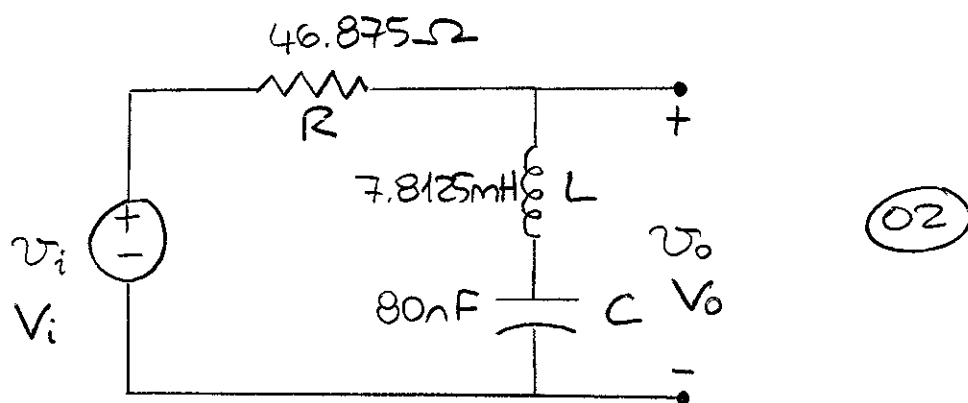
$$\Rightarrow R = 46.875 \Omega \quad (04)$$



2. Considering the s-domain equivalent circuit allows to obtain

$$\frac{V_o(s)}{V_i(s)} = \frac{sL + (1/sC)}{R + sL + (1/sC)}$$

$$= \frac{LCs^2 + 1}{LCs^2 + RCs + 1}$$

$$= \frac{s^2 + (1/LC)}{s^2 + (R/L)s + (1/LC)}$$

$$= \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

$$= \frac{s^2 + 16 \cdot 10^6}{s^2 + 6 \cdot 10^3 s + 16 \cdot 10^6} \quad (10)$$

$$\triangleq H(s)$$

c. $\beta = \frac{\omega_0}{Q} = \frac{4 \cdot 10^3}{2/3}$

$$= 6 \text{ krad/sec} \quad (01)$$

$$\omega_{c1} = \frac{-6 \cdot 10^3 + \sqrt{(6 \cdot 10^3)^2 + 4 \cdot 4 \cdot 10^3}}{2}$$

$$= \frac{-6 \cdot 10^3 + \sqrt{52} \cdot 10^3}{2}$$

$$= 605.5513 \text{ rad/sec} \quad (02)$$

$$\omega_{c2} = \frac{6 \cdot 10^3 + \sqrt{52} \cdot 10^3}{2}$$

$$= 6605.5513 \text{ rad/sec} \quad (02)$$