

Problem 1) Let

$$F(\omega) = \hat{\sim} \{f(t)\}$$

a. Show that

$$\hat{\sim} \left\{ \frac{df(t)}{dt} \right\} = j\omega F(\omega)$$

b. What is the restriction on $f(t)$ if the result given in (a) is valid?

c. Show that

$$\hat{\sim} \left\{ \frac{d^n f(t)}{dt^n} \right\} = (j\omega)^n F(\omega)$$

Solution. We use the defining integral and integrate by parts as follows

$$\hat{\sim} \left\{ \frac{df(t)}{dt} \right\} = \int_{-\infty}^{\infty} \frac{df(t)}{dt} e^{-j\omega t} dt$$

- let $u = e^{-j\omega t}$, $dv = \frac{df(t)}{dt} dt \Rightarrow v = f(t)$, $du = -$

$$du = -j\omega e^{-j\omega t} dt$$

- then

$$\hat{\sim} \left\{ \frac{df(t)}{dt} \right\} = e^{-j\omega t} f(t) \Big|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} f(t) (-j\omega e^{-j\omega t}) dt$$

$$= \lim_{t \rightarrow \infty} e^{-j\omega t} f(t) - \lim_{t \rightarrow -\infty} e^{-j\omega t} f(t) + j\omega \underbrace{\int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt}_{\hat{\sim} \{f(t)\}}$$

- assuming that

$$\lim_{t \rightarrow \infty} f(t) = \lim_{t \rightarrow -\infty} f(t) = 0$$

we obtain

$$\tilde{\mathcal{F}}\left\{\frac{df(t)}{dt}\right\} = 0 - 0 + j\omega F(\omega) \\ = j\omega F(\omega)$$

b. The restriction on $f(t)$ is that Fourier transform of $f(t)$ exists, that $f(t)$ must be absolutely integrable on an infinite interval.

c. Note that

$$\tilde{\mathcal{F}}\left\{\frac{d^n f(t)}{dt^n}\right\} = \frac{d^{n-1} f(t)}{dt^{n-1}} e^{-j\omega t} \Big|_{-\infty}^{\infty} - \int_{-\infty}^{\infty} \frac{d^{n-1} f(t)}{dt^{n-1}} (-j\omega) e^{-j\omega t} dt$$

$n=1$:

$$\tilde{\mathcal{F}}\left\{\frac{df(t)}{dt}\right\} = j\omega \tilde{\mathcal{F}}\{f(t)\}$$

$n=2$:


$$\tilde{\mathcal{F}}\left\{\frac{d^2 f(t)}{dt^2}\right\} = j\omega \tilde{\mathcal{F}}\left\{\frac{df(t)}{dt}\right\} \\ = (j\omega)(j\omega) \tilde{\mathcal{F}}\{f(t)\}$$

\vdots

n is arbitrary :

$$\tilde{\mathcal{F}}\left\{\frac{d^n f(t)}{dt^n}\right\} = (j\omega)^n \tilde{\mathcal{F}}\{f(t)\}$$

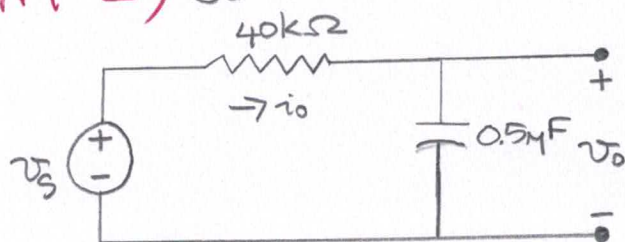Problem 2) Consider the following circuit



a. Use the Fourier transform method to find $v_o(t)$ if

$$v_g = 20 \operatorname{sgn}(t) \text{ V.}$$

b. Does your solution make sense in terms of known circuit behavior? Explain.

Solution. We have

$$\begin{aligned} \mathcal{F}\{20 \operatorname{sgn}(t)\} &= 20 \frac{2}{j\omega} \\ &= \frac{40}{j\omega} \triangleq V_g \end{aligned}$$

$$V_o = I_o \left(40000 + \frac{1}{j\omega \cdot 0.5 \cdot 10^{-6}} \right) = V_g \quad \text{"phasor-domain"}$$

$$\Rightarrow I_o \left(40000 - j \frac{2 \cdot 10^6}{\omega} \right) = \frac{40}{j\omega}$$

$$\Rightarrow I_o (j40000\omega + 2 \cdot 10^6) = 40$$

$$\Rightarrow I_o (5 \cdot 10^4 + j1000\omega) = 1$$

$$\Rightarrow I_o = \frac{1}{5 \cdot 10^4 + j1000\omega} = \frac{10^{-3}}{j\omega + 50}$$

Hence;

$$\mathcal{F}^{-1}\left\{ \frac{10^{-3}}{j\omega + 50} \right\} \triangleq i_o(t) = 10^{-3} e^{-50t}$$

Moreover;

$$\frac{V_o(s)}{V_g(s)} \triangleq H(s) = \frac{1/sC}{R + \frac{1}{sC}} = \frac{1}{1 + sRC} = \frac{1}{1 + s40 \cdot 10^3 \cdot 0.5 \cdot 10^{-6}}$$

$$= \frac{1}{1 + 0.02s}$$

$$\Rightarrow H(\omega) = H(s) \Big|_{s=j\omega} = \frac{1}{1 + 0.02j\omega}$$

$$= \frac{50}{j\omega + 50}$$

then

$$V_o(\omega) = H(\omega) V_s(\omega)$$

$$= \frac{50}{j\omega + 50} \cdot \frac{40}{j\omega} = \frac{C_1}{j\omega} + \frac{C_2}{j\omega + 50}$$

$$\Rightarrow C_1 = \frac{2000}{j\omega + 50} \Big|_{j\omega=0} = 40$$

$$\Rightarrow C_2 = \frac{2000}{j\omega} \Big|_{j\omega=-50} = -40$$

$$\Rightarrow V_o(\omega) = \frac{40}{j\omega} - \frac{40}{j\omega + 50}$$

$$\Rightarrow \mathcal{F}^{-1}\{V_o(\omega)\} = 20s\delta(t) - 40e^{-50t}u(t) \text{ V}$$

b. We have it behaves as a low-pass filter

$$v_o(0^-) = -20 - 0 = -20 \text{ V}$$

$$v_o(0^+) = 20 - 40 = -20 \text{ V}$$

\Rightarrow the capacitor is charged to -20 V when $t < 0$ and shows NO instantaneous change, that is, $v_o(0^+) = v_o(0^-)$

$$v_o(\infty) = 20 - 0 = 20 \text{ V}$$


\Rightarrow the capacitor behaves as a short circuit as $t \rightarrow \infty$

thus $v_o(\infty) = v_g = 20 \text{ V}$

finally, the time constant, $RC = 40 \cdot 10^3 \cdot 0.5 \cdot 10^{-6} = 0.02 \text{ s}$

$\hookrightarrow v_o(t)$ is of exponential form with a time constant of $1/50 = 0.02 \text{ s}$

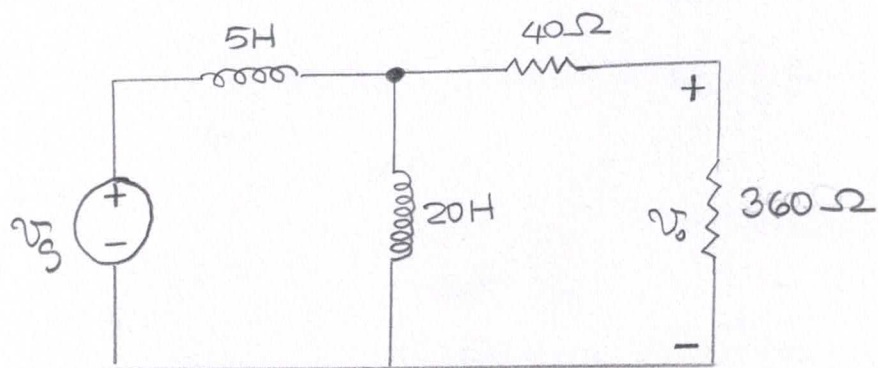Problem 3) Consider the following circuit shown as




a. Use the Fourier transform method to find v_o if

$v_g = 125 \cos 75t \text{ V}$

b. Check the answer obtained in (a) by finding the steady-state expression for v_o using phasor domain analysis.

Solution.

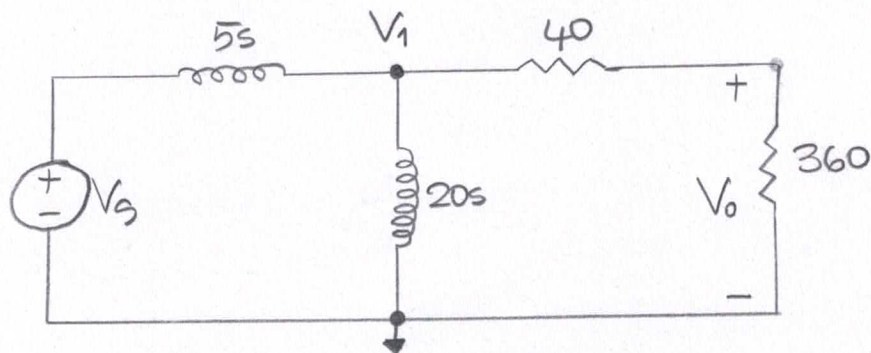a. We consider the s-domain equivalent circuit



we consider the node-voltage equations:

$$\frac{V_1 - V_g}{5s} + \frac{V_1}{20s} + \frac{V_1}{40} = 0 \Rightarrow (s+100)V_1 = 80V_g = 0$$

$$\Rightarrow V_1 = \frac{80}{s+100} V_g$$

and

$$V_o = \frac{360}{40+360} V_1 = \frac{360}{400} \frac{280}{s+100} V_s$$

$$\Rightarrow \frac{V_o}{V_s} \triangleq H(s) = \frac{72}{s+100}$$

then

$$H(\omega) = H(s) \Big|_{s=j\omega} = \frac{72}{j\omega+100}$$

$$V_g(\omega) = \mathcal{F}\{125 \cos 75t\} = 125\pi [\delta(\omega+75) + \delta(\omega-75)]$$

$$\Rightarrow V_o(\omega) = H(\omega) V_g(\omega)$$

$$= \frac{72}{j\omega+100} 125\pi [\delta(\omega+75) + \delta(\omega-75)]$$

$$= 90\pi \left[\frac{\delta(\omega+75)}{j\omega+100} + \frac{\delta(\omega-75)}{j\omega+100} \right]$$

Thus ;

$$v_o(t) = \mathcal{F}^{-1}\{V_o(\omega)\} = \frac{1}{2\pi} \int_{-\infty}^{\infty} 90\pi \left[\frac{\delta(\omega+75)}{j\omega+100} + \frac{\delta(\omega-75)}{j\omega+100} \right] e^{j\omega t} d\omega$$


$$= 45 \left(\frac{e^{-75t}}{100-j75} + \frac{e^{75t}}{100+j75} \right)$$

$$= \frac{9}{25} \left(\frac{e^{-75t}}{125 e^{-j36.87^\circ}} + \frac{e^{75t}}{125 e^{j36.87^\circ}} \right)$$

$$= \frac{9}{25} \left[e^{-j(75t-36.87^\circ)} + e^{j(75t-36.87^\circ)} \right]$$

$$= 0.72 \cos(75t - 36.87^\circ) \text{ V}$$

b. We now employ phasor domain analysis

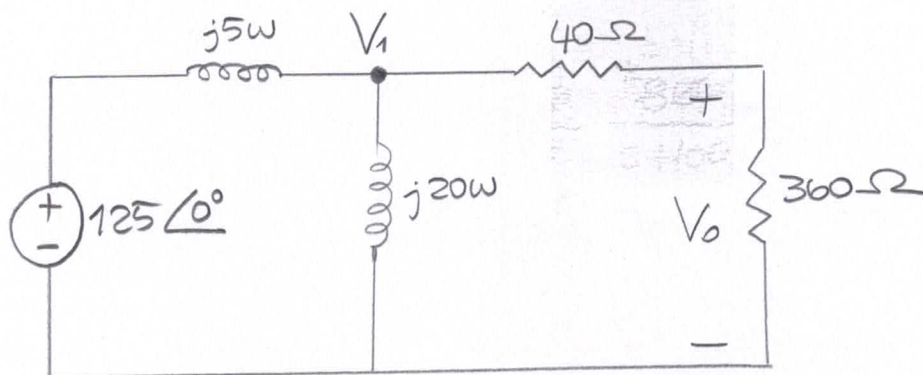

where $\omega = 75 \text{ rad/s}$

-we write the node-voltage equation as follows

$$\frac{V_1 - 125}{j5\omega} + \frac{V_1}{j20\omega} + \frac{V_1}{400} = 0$$

(80) (20) (100)

$$\Rightarrow (j\omega + 100)V_1 = 10^4 \Rightarrow V_1 = \frac{10^4}{j\omega + 100}$$

and

$$V_0 = \frac{360}{40 + 360} V_1 = \frac{360}{400} \frac{10^4}{j\omega + 100} = \frac{9000}{j\omega + 100}$$

-letting $\omega = 75 \text{ rad/s}$ gives

$$V_0 = \frac{9000}{j75 + 100} = \frac{9000}{125 e^{j36.87^\circ}} = 72 \angle -36.87^\circ$$

$$\Rightarrow v_0(t) = 72 \cos(75t - 36.87^\circ) \text{ V}$$

Problem 4) It is given that

$$F(\omega) = e^{\omega} u(-\omega) + e^{-\omega} u(\omega)$$

a. Find $f(t)$.

b. Find the 1-Ω energy associated with $f(t)$ via time-domain

PS 10.7

c. Repeat part (b) using frequency-domain integration

d. Find the value of ω_1 if $f(t)$ has 90% of the energy in the frequency band $0 \leq \omega \leq \omega_1$.

Solution.

a.

$$\begin{aligned} f(t) &= \mathcal{F}^{-1}\{F(\omega)\} \\ &= \frac{1}{2\pi} \int_{-\infty}^{\infty} [e^{\omega} u(-\omega) + e^{-\omega} u(\omega)] e^{j\omega t} d\omega \\ &= \frac{1}{2\pi} \left(\int_{-\infty}^0 e^{\omega} e^{j\omega t} d\omega + \int_0^{\infty} e^{-\omega} e^{j\omega t} d\omega \right) \\ &= \frac{1}{2\pi} \left[\int_{-\infty}^0 e^{(1+jt)\omega} d\omega + \int_0^{\infty} e^{\omega(-1+jt)} d\omega \right] \\ &= \frac{1}{2\pi} \left[\left. \frac{e^{(1+jt)\omega}}{1+jt} \right|_{-\infty}^0 + \left. \frac{e^{\omega(-1+jt)}}{-1+jt} \right|_0^{\infty} \right] \\ &= \frac{1}{2\pi} \left(\frac{1}{1+jt} - 0 + 0 - \frac{1}{-1+jt} \right) \\ &= \frac{1}{2\pi} \frac{-1+jt-1-jt}{(1+jt)(-1+jt)} \\ &= \frac{1}{2\pi} \frac{-2}{-t^2+1} \\ &= \frac{1}{\pi(t^2+1)} \end{aligned}$$

b.

$$\begin{aligned}
 W_{1-\Omega} &= 1 \cdot \int_{-\infty}^{\infty} f^2(t) dt \\
 &= \frac{1}{\pi^2} \int_{-\infty}^{\infty} \frac{1}{(t^2+1)^2} dt \\
 &= \frac{2}{\pi^2} \int_0^{\infty} \frac{1}{(t^2+1)^2} dt \\
 &= \frac{2}{\pi^2} \cdot \frac{1}{2} \left(\frac{t}{t^2+1} + t^{-1} \right) \Big|_0^{\infty} \\
 &= \frac{1}{\pi^2} \left(0 + \frac{\pi}{2} - 0 - 0 \right) \\
 &= \frac{1}{2\pi} \mathcal{J}
 \end{aligned}$$

c.

$$\begin{aligned}
 W_{1-\Omega} &= \frac{1}{2\pi} \int_{-\infty}^{\infty} |F(w)|^2 dw \\
 &= \frac{1}{2\pi} \int_{-\infty}^{\infty} [e^w u(-w) + e^{-w} u(w)]^2 dw \\
 &= \frac{1}{2\pi} \int_{-\infty}^{\infty} [e^{2w} u^2(-w) + 2u(-w)u(w) + e^{-2w} u^2(w)] dw \\
 &= \frac{1}{2\pi} \left(\int_{-\infty}^0 e^{2w} dw + \int_0^{\infty} e^{-2w} dw \right) \\
 &= \frac{1}{2\pi} \left(\frac{1}{2} e^{2w} \Big|_{-\infty}^0 + \frac{1}{-2} e^{-2w} \Big|_0^{\infty} \right) \\
 &= \frac{1}{2\pi} \left(\frac{1}{2} \cdot 1 - \frac{1}{2} \cdot 0 - \frac{1}{2} \cdot 0 + \frac{1}{2} \cdot 1 \right) \\
 &= \frac{1}{2\pi} \mathcal{J}
 \end{aligned}$$

d. We have

$$2. \frac{1}{2\pi} \int_{-\omega_1}^{\omega_1} |F(\omega)|^2 d\omega = 0.9 \cdot \frac{1}{2\pi}$$

$$\Rightarrow \frac{1}{2\pi} \int_{-\omega_1}^{\omega_1} [e^{z\omega} u^2(-\omega) + 2u(-\omega)u(\omega) + e^{-z\omega} u^2(\omega)] d\omega = 0.9 \frac{1}{2\pi}$$

$$\Rightarrow \int_{-\omega_1}^0 e^{z\omega} d\omega + \int_0^{\omega_1} e^{-z\omega} d\omega = 0.9$$


$$\Rightarrow \frac{1}{z} e^{z\omega} \Big|_{-\omega_1}^0 + \frac{1}{-z} e^{-z\omega} \Big|_0^{\omega_1} = 0.9$$

$$\Rightarrow \frac{1}{z} (1 - e^{-z\omega_1}) - \frac{1}{z} (e^{-z\omega_1} - 1) = 0.9$$

$$\Rightarrow 1 - e^{-z\omega_1} = 0.9 \Rightarrow e^{-z\omega_1} = 0.1$$

$$\Rightarrow -z\omega_1 = \ln 0.1 \Rightarrow \omega_1 = \frac{\ln 0.1}{-2} = 1.1513 \text{ rad/s}$$

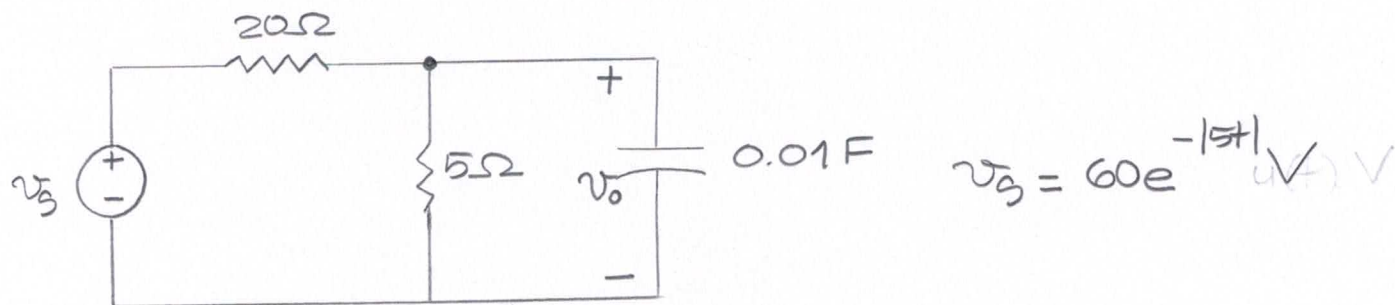Problem 5) Consider the following circuit



a. Find $v_o(t)$.

b. Sketch $|V_g(\omega)|$ for $-10 \leq \omega \leq 10 \text{ rad/s}$.

c. Sketch $|V_o(\omega)|$ for $-10 \leq \omega \leq 10 \text{ rad/s}$.


d. Calculate the 1- Ω energy content of v_g .

e. Calculate the 1- Ω energy content of v_o .

f. What percentage of the 1- Ω energy content in v_g is in the frequency range $0 \leq \omega \leq 10 \text{ rad/s}$?

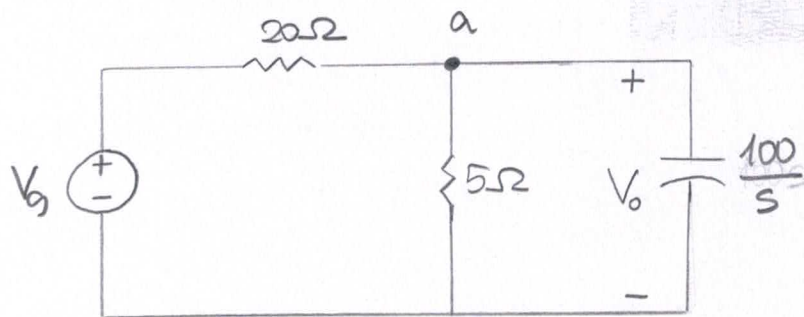g. Repeat (f) for V_o .

Solution. We shall first draw the s-domain equivalent circuit as follows



-writing node-voltage equation at node a : gives

$$\frac{V_o - V_g}{20} + \frac{V_o}{5} + \frac{sV_o}{100} = 0$$

(5) (20) (1)

$$\Rightarrow (s+25)V_o - 5V_g = 0 \Rightarrow \frac{V_o}{V_g} \triangleq H(s) = \frac{5}{s+25}$$

a. We have

$$v_g(t) = v_g^+ + v_g^-$$

where

$$v_g^+ = 60e^{-5t}, t > 0$$

$$v_g^- = 60e^{5t}, t < 0$$

then

$$\mathcal{L}\{v_g\} = \mathcal{L}\{60e^{-5t}\}|_{s=j\omega} + \mathcal{L}\{60e^{5t}\}|_{s=-j\omega}$$

$$= \frac{60}{j\omega+5} + \frac{60}{-j\omega+5}$$

$$= \frac{600}{(j\omega+5)(-j\omega+5)}$$

Hence;

$$V_o(\omega) = H(\omega) V_s(\omega)$$

$$= H(s) \Big|_{s=j\omega} V_s(\omega)$$

$$= \frac{5}{j\omega+25} \frac{600}{(j\omega+5)(-j\omega+5)}$$

$$= \frac{C_1}{j\omega+5} + \frac{C_2}{-j\omega+5} + \frac{C_3}{j\omega+25}$$

$$\Rightarrow C_1 = \frac{3000}{(j\omega+25)(-j\omega+5)} \Big|_{j\omega=-5} = \frac{3000}{25 \cdot 10} = 12$$

$$\Rightarrow C_2 = \frac{3000}{(j\omega+25)(j\omega+5)} \Big|_{j\omega=5} = \frac{3000}{30 \cdot 10} = 10$$


$$\Rightarrow C_3 = \frac{3000}{(j\omega+5)(-j\omega+5)} \Big|_{j\omega=-25} = \frac{3000}{(-25) \cdot 20} = -6$$

Thus;

$$\begin{aligned} \mathcal{L}^{-1}\{V_o(\omega)\} &\triangleq v_o(t) = \mathcal{L}^{-1}\left\{\frac{12}{j\omega+5} + \frac{10}{-j\omega+5} - \frac{6}{j\omega+25}\right\} \\ &= (12e^{-5t} - 6e^{-25t})u(t) - 10e^{5t}u(-t) \text{ V} \end{aligned}$$


b. We have

$$|V_s(\omega)| = \left| \frac{600}{(j\omega+5)(-j\omega+5)} \right| = \frac{600}{\sqrt{\omega^2+25} \cdot \sqrt{\omega^2+25}} = \frac{600}{\omega^2+25}$$

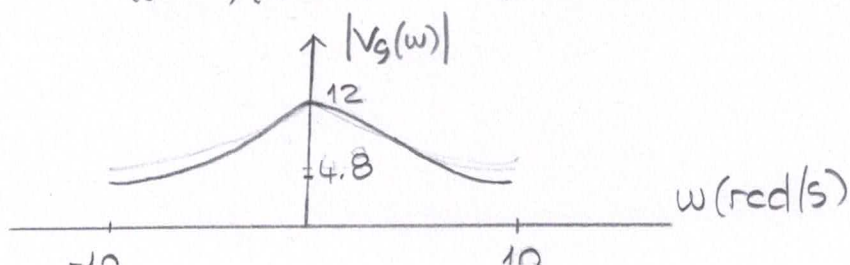

c. We calculate

$$\begin{aligned}
 |V_o(\omega)| &= \left| \frac{3000}{(j\omega+5)(-j\omega+5)(j\omega+25)} \right| \\
 &= \frac{3000}{\sqrt{\omega^2+25} \cdot \sqrt{\omega^2+25} \cdot \sqrt{\omega^2+625}} \\
 &= \frac{3000}{\omega^2+25 \sqrt{\omega^2+625}}
 \end{aligned}$$

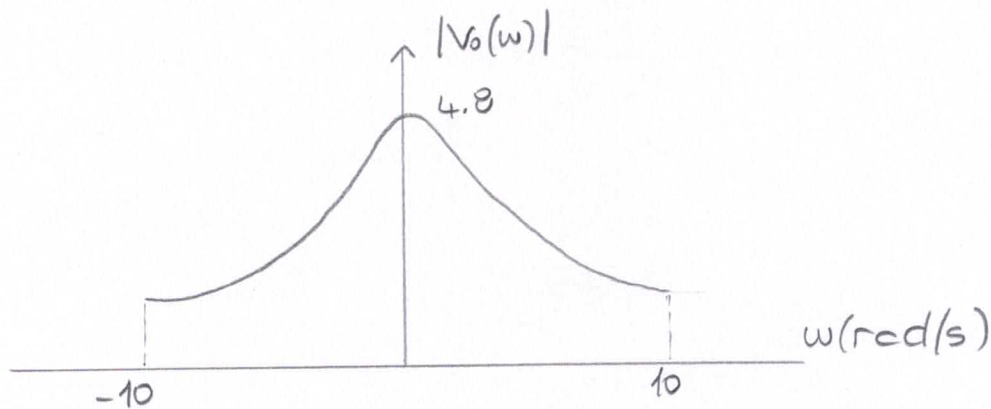

d.

$$\begin{aligned}
 W_s &= \frac{1}{2\pi} \int_{-\infty}^{\infty} |V_s(\omega)|^2 d\omega \\
 &= \frac{1}{2\pi} \int_{-\infty}^{\infty} \frac{36 \cdot 10^4}{(\omega^2+25)^2} d\omega \\
 &= \frac{36 \cdot 10^4}{2\pi} \cdot 2 \int_0^{\infty} \frac{1}{\omega^2+5^2} d\omega \\
 &= \frac{18 \cdot 10^4}{\pi} \cdot \frac{1}{5^2} \left(\frac{\omega}{\omega^2+25} + \frac{1}{5} \tan^{-1} \frac{\omega}{5} \right) \Bigg|_0^{\infty} \\
 &= \frac{7200}{\pi} \left(0 + \frac{1}{5} \frac{\pi}{2} - 0 - 0 \right) \\
 &= 720 \text{ J}
 \end{aligned}$$

e.

$$W_0 = \int_{-\infty}^{\infty} v_0^2(t) dt$$

$$= \int_{-\infty}^{\infty} \left[(15e^{-5t} - 5e^{-25t})u(t) - 10e^{5t}u(-t) \right]^2 dt$$

$$= \int_{-\infty}^{\infty} \left[(15e^{-5t} - 5e^{-25t})^2 u^2(t) - 20(15 - 5e^{-20t})u(t)u(-t) + 100e^{10t}u^2(-t) \right] dt$$

$$= \int_0^{\infty} (225e^{-10t} - 150e^{-30t} + 25e^{-50t}) dt + \int_{-\infty}^0 100e^{10t} dt$$

$$= \left(-22.5e^{-10t} + 5e^{-30t} - 0.5e^{-5t} \right) \Big|_0^{\infty} + 10e^{10t} \Big|_{-\infty}^0$$

$$= (0 + 22.5 + 0 - 5 - 0 + 0.5) + 10 - 0$$

$$= 28 \text{ J}$$

f.

$$W'_G = \frac{1}{2\pi} \int_{-10}^{10} |V_3(\omega)|^2 d\omega =$$

$$= \frac{1}{2\pi} \int_{-10}^{10} \frac{36 \cdot 10^4}{(\omega^2 + 5^2)^2} d\omega$$

$$= \frac{36 \cdot 10^4}{2\pi} \cdot 2 \int_0^{10} \frac{1}{(\omega^2 + 5^2)^2} d\omega$$

$$= \frac{36 \cdot 10^4}{2\pi} \cdot 2 \left(\frac{1}{2 \cdot 5^2} \left(\frac{\omega}{\omega^2 + 5^2} + \frac{1}{5} \tan^{-1} \frac{\omega}{5} \right) \right) \Big|_0^{10}$$

$$= \frac{7200}{\pi} \left(\frac{10}{125} + \frac{1}{5} \tan^{-1} 2 - 0 - 0 \right)$$

$$= \frac{7200}{\pi} \left(0.08 + \frac{1}{5} \cdot 1.0171 \right)$$

$$= 690.8038 \text{ J}$$

Hence;

$$\frac{690.8038}{720} \times 100 = \% 95.9450$$

9. We calculate

$$W_0' = \frac{1}{2\pi} \int_{-10}^{10} |V_0(\omega)|^2 d\omega$$

$$= \frac{1}{2\pi} \int_{-10}^{10} \frac{9 \cdot 10^6}{(\omega^2 + 25)^2 (\omega^2 + 625)} d\omega$$

Note that;

$$\frac{9 \cdot 10^6}{(\omega^2 + 25)^2 (\omega^2 + 625)} = \frac{15000}{(\omega^2 + 25)^2} - \frac{25}{\omega^2 + 25} + \frac{25}{\omega^2 + 625}$$

Hence;

$$W_0' = \frac{1}{2\pi} \cdot 2 \int_0^{10} \left[\frac{15000}{(\omega^2 + 25)^2} - \frac{1}{1 + (\omega/5)^2} + \frac{1/25}{1 + (\omega/25)^2} \right] d\omega$$

$$= \frac{1}{\pi} \left[\frac{1}{2 \cdot 25} \cdot 300 \left(\frac{\omega}{\omega^2 + 25} + \frac{1}{5} \tan^{-1} \frac{\omega}{5} \right) - 5 \tan^{-1} \frac{\omega}{5} + \tan^{-1} \frac{\omega}{25} \right]_0^{10}$$

$$= \frac{1}{\pi} \left[300 \left(\frac{10}{125} + \frac{1}{5} \cdot 1.0171 \right) - 5 \cdot 1.0171 + 0.3805 - 0 + 0 - 0 \right]$$

$$= 27.1435 \text{ J}$$

As a result;

$$\frac{27.1435}{28} \times 100 = \% 96.9409$$