

- Problem 1) a.** Write the transfer function for a 4<sup>th</sup>-order Butterworth low-pass filter (prototype).
- b.** Write the transfer function for the scaled filter with a cutoff frequency of 1000 Hz.
- c.** Calculate the gain in decibels at 4000 Hz.

**Solution:**

a. We find the roots of the polynomial

$$1 + (-s)^{2.4} = 0$$

$$\Rightarrow s^8 = -1 \quad j(\pi + 2\pi n) \\ = e$$

Hence;

$$s = e^{j\left(\frac{\pi + 2\pi n}{8}\right)}, \quad n = 0, 1, \dots, 7$$

$$s_0 = e^{j\pi/8} = 0.9239 + j0.3827 \quad \text{RHP}$$

$$s_1 = e^{j3\pi/8} = 0.3827 + j0.9239 \quad \text{RHP}$$

$$s_2 = e^{j5\pi/8} = -0.3827 + j0.9239 \quad \text{LHP}$$

$$s_3 = e^{j7\pi/8} = -0.9239 + j0.3827 \quad \text{LHP}$$

$$s_4 = e^{j9\pi/8} = -0.9239 - j0.3827 \quad \text{LHP}$$

$$s_5 = e^{j11\pi/8} = -0.3827 - j0.9239 \quad \text{LHP}$$

$$s_6 = e^{j13\pi/8} = 0.3827 - j0.9239 \quad \text{RHP}$$

$$s_7 = e^{j15\pi/8} = 0.9239 - j0.3827 \quad \text{RHP}$$

use these poles to build  
H(s)

- we first calculate

$$(s + 0.3827 - j0.9239)(s + 0.3827 + j0.9239)$$

$$= s^2 + 0.7654 + 1.0001$$

- then we calculate

$$(s+0.5239-j0.3827)(s+0.5239+j0.3827)$$

$$= s^2 + 1.8478s + 1.0001$$

Therefore ;

$$H(s) = \frac{1}{(s^2 + 0.7654s + 1.0001)(s^2 + 1.8478s + 1.0001)}$$

Q. We have

$$\omega_c = 2\pi \cdot 1000 \Rightarrow k_f = 2000\pi$$

then we replace s by  $s/2000\pi$  in  $H(s)$  to get a magnitude and frequency scaled transfer fn.

as

$$H'(s) = \frac{1}{\left[\left(\frac{s}{2000\pi}\right)^2 + 0.7654\left(\frac{s}{2000\pi}\right) + 1.0001\right]\left[\left(\frac{s}{2000\pi}\right)^2 + 1.8478\left(\frac{s}{2000\pi}\right) + 1.0001\right]}$$

$$= \frac{(4 \cdot 10^6 \pi^2)^2}{(s^2 + 4809.2s + 4 \cdot 10^6 \pi^2)(s^2 + 11610s + 4 \cdot 10^6 \pi^2)}$$

Q.

$$H'(j8000\pi) = \frac{16}{(-60+j12.24)(-60+j29.568)}, \quad \omega = 2\pi \cdot 4000 = 8000\pi$$

$$|H'(j8000\pi)| = \frac{16}{61.24 \cdot 66.89} = 3.91 \cdot 10^{-3}$$


Hence ;

$$20 \log_{10} |H'(j8000\pi)| = -48.16 \text{ dB}$$

**Problem 2) a.** Using  $2k\Omega$  resistors and ideal opamps, design a 4<sup>th</sup>-order low-pass Butterworth filter with a cutoff frequency of 1000 Hz. The gain in the passband is one.

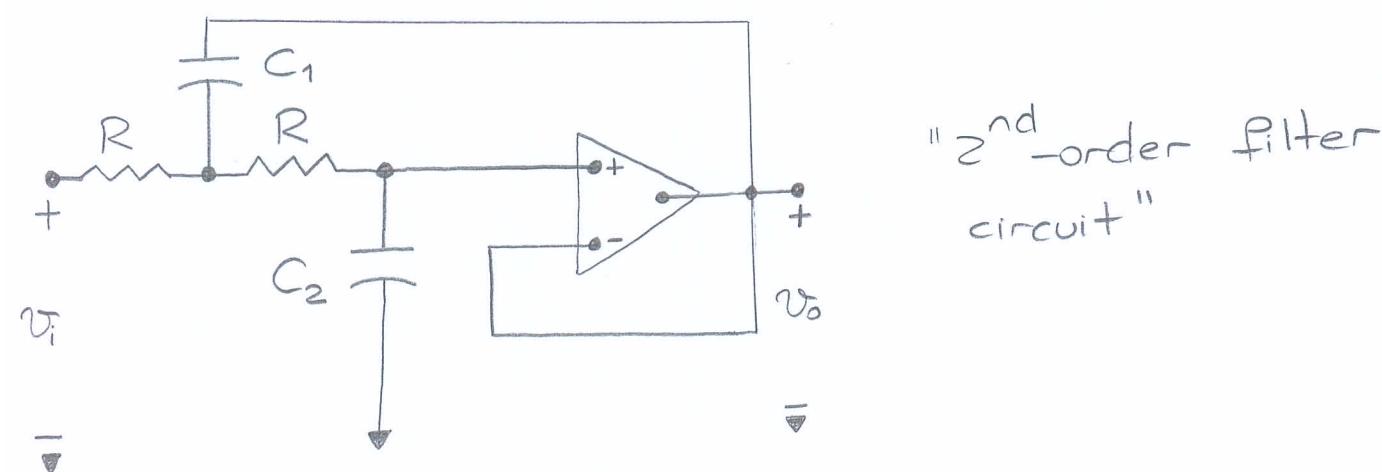b. Construct the circuit diagram and label all component values.

**Solution.** The prototype 4<sup>th</sup>-order low-pass Butterworth filter is a cascade of two 2<sup>nd</sup>-order filters:



- we shall easily derive that

$$\frac{V_0}{V_i} = H(s) = \frac{\frac{1}{R^2 C_1 C_2}}{s^2 + \frac{2}{R C_1} s + \frac{1}{R^2 C_1 C_2}}$$

- for a prototype filter, we set  $R = 1\Omega$

1<sup>st</sup> stage :  $s^2 + 0.765s + 1$

$$\frac{1}{C_1 C_2} = 1, \quad \frac{2}{C_1} = 0.765 \Rightarrow C_1 = 2.6144 \text{ F}$$

$$\Rightarrow C_2 = \frac{1}{2.6144} = 0.3825 \text{ F}$$

$$2^{\text{nd}} \text{ stage : } s^2 + 1.848s + 1$$

$$\frac{1}{C_3 C_4} = 1, \quad \frac{2}{C_3} = 1.848 \Rightarrow C_3 = 1.0823$$

$$\Rightarrow C_4 = \frac{1}{1.0823} = 0.9240$$

- we have  $k_f = 2000\pi$ ,  $k_m = 2000$


$$C_1' = \frac{2.6144}{2000\pi \cdot 2000} = 208 \text{ nF}$$

$$C_2' = \frac{0.3825}{2000\pi \cdot 2000} = 30.4 \text{ nF}$$

$$C_3' = \frac{1.0823}{2000\pi \cdot 2000} = 86.1 \text{ nF}$$

$$C_4' = \frac{0.9240}{2000\pi \cdot 2000} = 73.5 \text{ nF}$$

D.

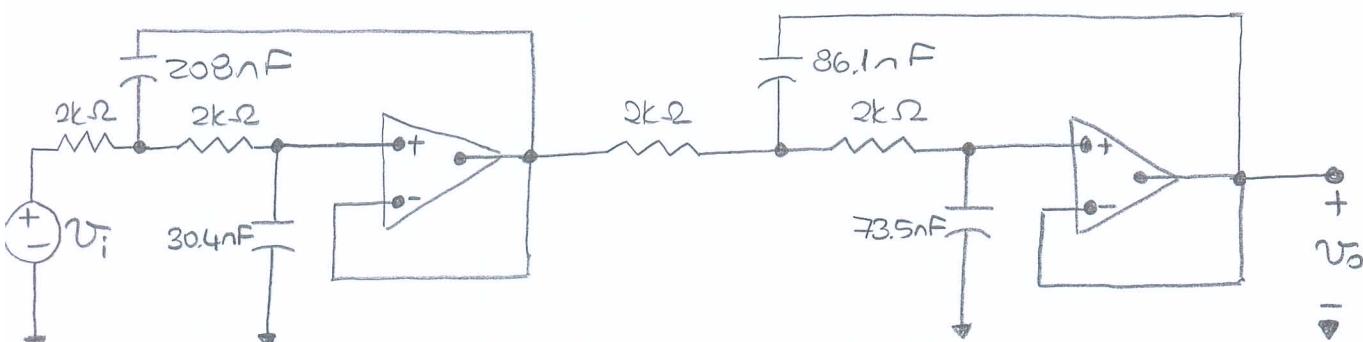

4<sup>th</sup>-order low-pass Butterworth filter

Problem 3)a. Using  $25\text{nF}$  capacitors and ideal op amps, design a high-pass unity-gain Butterworth filter with a cutoff frequency of  $5\text{kHz}$  and a gain of at least  $-25\text{dB}$  at  $1\text{kHz}$ .

b. Draw a circuit diagram of the filter and label all component values.

Solution.

c.  $\omega_c = 2\pi \cdot 5000 = 10000\pi \Rightarrow k_f = 10000\pi$

- we first determine the order of the filter:

$$|H(j\omega)| = \frac{(\omega/\omega_c)^n}{\sqrt{1 + (\omega/\omega_c)^{2n}}}$$

$$-25\text{ dB} = 20 \log_{10} |H(j2000\pi)|$$

$$\Rightarrow |H(j2000\pi)| = 10^{-1.25} = 0.0562$$

$$\Rightarrow \frac{(2000\pi/1000\pi)^n}{\sqrt{1 + (2000\pi/10000\pi)^{2n}}} = 0.0562$$


$$\Rightarrow 1 + (0.2)^{2n} = 316.2278 \cdot (0.2)^{2n}$$

$$\Rightarrow (0.2)^{2n} = 0.0032 \Rightarrow 2n = \frac{\log 0.0032}{\log 0.2}$$

$$\Rightarrow n = 1.7874$$

we choose the upper closest integer for  $n$   
 $\Rightarrow$  a 2nd order high-pass Butterworth filter  
is required

- we receive

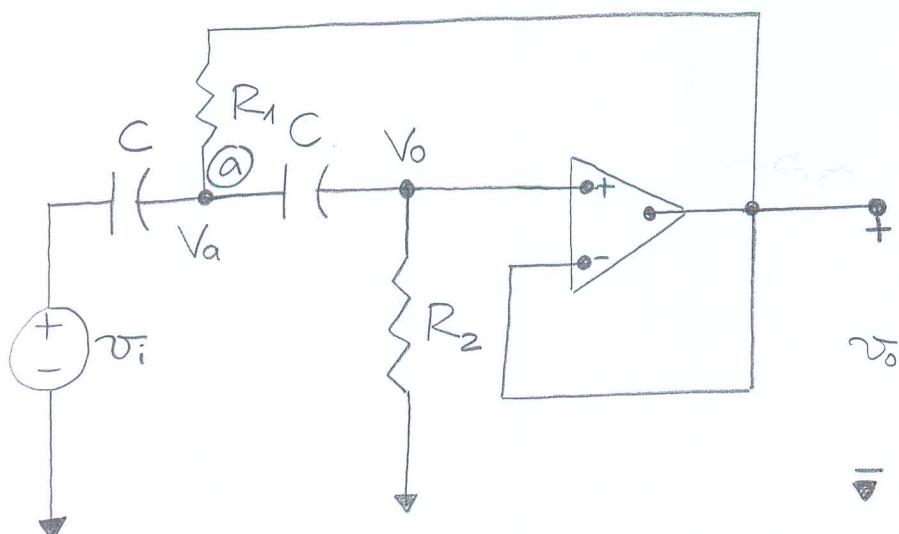

$$\frac{V_o}{V_i} = H(s) = \frac{1}{s^2 + \sqrt{2}s + 1}$$

"2<sup>nd</sup>-order high-pass Butterworth filter transfer fn."

KCL at non-inverting input of the op amp:

$$\frac{V_o}{R_2} + \frac{V_o - V_a}{(1/sC)} = 0 \Rightarrow \left(\frac{1}{R_2} + sC\right)V_o = sC V_a$$

$$\Rightarrow V_a = \frac{1 + sR_2 C}{sR_2 C}$$

KCL at node C:

$$\frac{V_a - V_i}{(1/sC)} + \frac{V_c - V_o}{(1/sC)} + \frac{V_a - V_o}{R_1} = 0$$

$$\Rightarrow \left(2sC + \frac{1}{R_1}\right)V_a - sC V_i - \left(sC + \frac{1}{R_1}\right)V_o = 0$$

$$\Rightarrow (2sR_1C + 1)V_a - sR_1C V_i - (sR_1C + 1)V_o = 0$$

$$\Rightarrow (2sR_1C + 1) \frac{(1 + sR_2 C)}{sR_2 C} V_o - sR_1C V_i - (sR_1C + 1)V_o = 0$$

$$\Rightarrow \left[ \frac{(2sR_1C+1)(sR_2C+1)}{sR_2C} - (sR_1C+1) \right] V_o = sR_1C V_i$$

$$\Rightarrow [(2sR_1C+1)(sR_2C+1) - sR_2C(sR_1C+1)] V_o = sR_2C \cdot sR_1C \cdot V_i$$

$$\Rightarrow (s^2 R_1 R_2 C^2 + 2sR_1C + 1) V_o = s^2 R_1 R_2 C^2 V_i$$

$$\Rightarrow \frac{V_o}{V_i} \triangleq H(s) = \frac{(1/R_1 R_2 C^2) s^2}{s^2 + \frac{2}{R_2 C} s + \frac{1}{R_1 R_2 C^2}}$$

- let us choose  $C = 1 F$ , then

$$\frac{2}{R_2} = \sqrt{2} \Rightarrow R_2 = \sqrt{2} \Omega$$

$$\frac{1}{R_1 R_2} = 1 \Rightarrow R_1 = \frac{1}{\sqrt{2}} = \frac{\sqrt{2}}{2} \Omega$$


- for the magnitude scaling factor, we have

$$25 \cdot 10^{-9} = \frac{1}{k_m \cdot 10^4 \pi} \Rightarrow k_m = 1273.2$$


Therefore;

$$R_1 = \frac{\sqrt{2}}{2} \cdot 1273.2 = 900.3163 \Omega$$

$$R_2 = \sqrt{2} \cdot 1273.2 = 1800.6326 \Omega$$

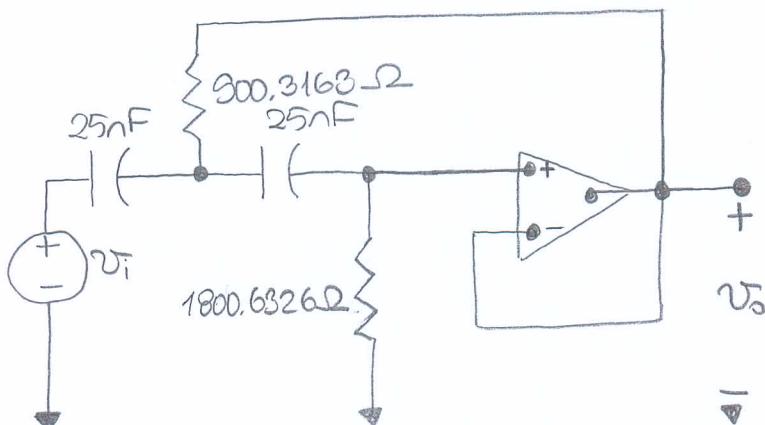

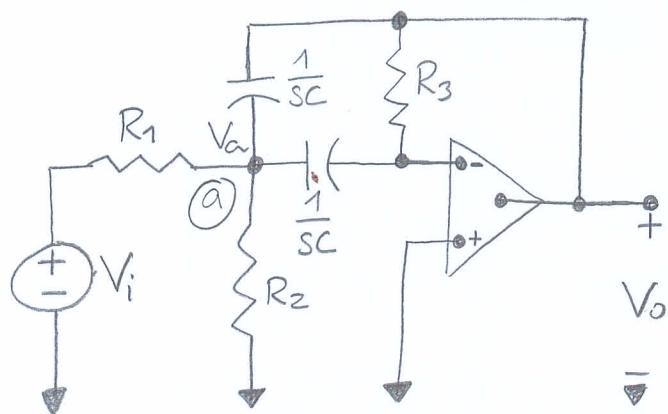Problem 4) Consider the following active high-Q bandpass filter



- a. Use  $300\text{pF}$  capacitors to design a bandpass filter with a quality factor of 20, a center frequency of  $8\text{kHz}$ , and a passband gain of  $40\text{dB}$ .
- b. Draw the circuit diagram of the filter and label all component values.

**Solution.** Let us first derive the transfer function of the above filter:

KCL at inverting input of the op amp :

$$\frac{0-V_a}{(1/\text{sC})} + \frac{0-V_o}{R_3} = 0 \Rightarrow V_a = -\frac{1}{sR_3C}V_o$$

KCL at node a :

$$\frac{V_a-V_i}{R_1} + \frac{V_a}{R_2} + \frac{V_a-V_o}{(1/\text{sC})} + \frac{V_o}{(1/\text{sC})} = 0$$

$$\Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} + 2\text{sC}\right)V_a - \frac{1}{R_1}V_i - \text{sC}V_o = 0$$

$$\Rightarrow (R_2 + R_1 + 2sR_1R_2C)V_a - R_2V_i - sR_1R_2CV_o = 0$$

$$\Rightarrow \left[ -\frac{(R_1 + R_2 + 2sR_1R_2C)}{sR_3C} - sR_1R_2C \right] V_o = R_2V_i$$

$$\Rightarrow -(s^2R_1R_2R_3C^2 + 2R_1R_2Cs + R_1 + R_2)V_o = sR_2R_3C V_i$$

$$\Rightarrow \frac{V_o}{V_i} \triangleq H(s) = -\frac{sR_2R_3C}{s^2R_1R_2R_3C^2 + 2R_1R_2Cs + R_1 + R_2}$$

$$-\frac{(1/R_1C)s}{s^2 + \frac{2}{R_3C}s + \frac{R_1 + R_2}{R_1R_2R_3C^2}}$$

$$= -\frac{R_3}{2R_1} \frac{\left(\frac{2}{R_3C}\right)s}{s^2 + \frac{2}{R_3C}s + \frac{R_1 + R_2}{R_1R_2R_3C^2}}$$

$$= -K \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

where

$$K = \frac{R_3}{2R_1}, \quad \beta = \frac{2}{R_3C}, \quad \omega_0^2 = \frac{R_1 + R_2}{R_1R_2R_3C^2}$$

$$\varphi = \frac{\omega_0}{\beta} \Rightarrow \varphi = \frac{\pi \cdot 800}{\beta} \Rightarrow \beta = 800\pi$$

$$\Rightarrow R_3 = \frac{2}{\beta C} = \frac{2}{800\pi \cdot 300 \cdot 10^{-12}} = 2652.6 \text{ k}\Omega$$

$$40 \text{ dB} = 20 \log_{10} |H(j\omega_0)|$$

$$\Rightarrow |H(j\omega_0)| = 100 = \frac{R_3}{2R_1} \Rightarrow R_1 = 13.263 \text{ k}\Omega$$

and

$$(2\pi \cdot 8000)^2 = \frac{1}{R_{eq} \cdot 2652.6 \cdot 10^3 \cdot (300 \cdot 10^{-12})^2}$$

$$\Rightarrow R_{eq} = 1.6579 \cdot 10^3 \Omega = \frac{13.263 \cdot 10^3 R_2}{13.263 \cdot 10^3 + R_2}$$


$$\Rightarrow 1.6579 \cdot 13.263 \cdot 10^3 = 11.6051 R_2$$

$$\Rightarrow R_2 = 1.8947 \text{ k}\Omega$$

Note that;

-we could have used frequency scaling  
and magnitude scaling to find component values

b.

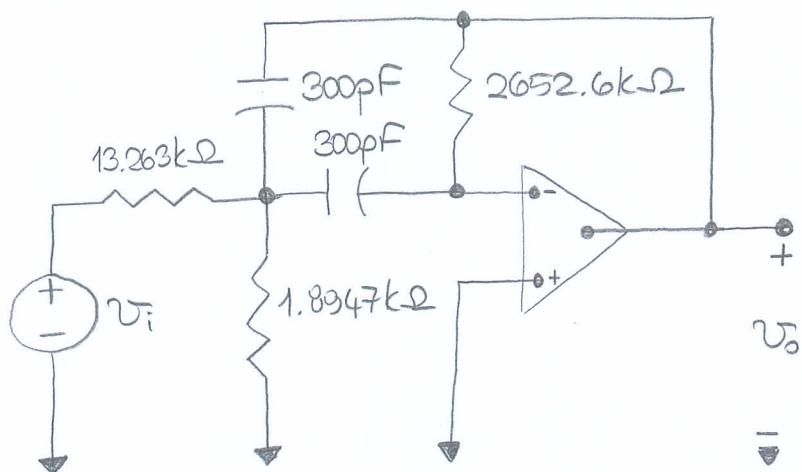

Problem 5)c. Design a broadband Butterworth bandpass filter with a lower cutoff frequency of 1000 Hz and an upper cutoff frequency of 8000 Hz. The passband gain of the filter is 10 dB. The gain should be down at least 20 dB at 400 Hz and 20 kHz. Use 50 nF capacitors in the high-pass circuit and 5 kΩ resistors in the low-pass circuit.  
d. Draw the circuit and label all component values. PS 6.10

**Solution. a.** We consider the cascade of Butterworth low-pass and high-pass filters

Low-pass filter:  $\omega_c = 2\pi \cdot 8000 \text{ rad/s}$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_c)^{2n}}}$$

$$-20 \text{ dB} = 20 \log \frac{1}{\sqrt{1 + (2\pi \cdot 20 \cdot 10^3 / 2\pi \cdot 8000)^{2n}}}$$

$$\Rightarrow -20 = -20 \log [1 + (2.5)^{2n}]$$

$$\Rightarrow 100 = 1 + (2.5)^{2n} \Rightarrow (2.5)^{2n} = 99$$

$$\Rightarrow 2n \log 2.5 = \log 99 \Rightarrow n = \frac{\log 99}{2 \log 2.5} = 2.5075$$

Hence;

- the order is 3

$$H_{LPP}(s) = \frac{1}{(s+1)(s^2 + s + 1)}$$

$$\frac{1}{c_1 c_2} = 1, \quad \frac{2}{c_1} = 1 \Rightarrow c_1 = 2, \quad c_2 = \frac{1}{2}, \quad R_1 = R_2 = 1$$

$$k_p = 2\pi \cdot 8000 = 16000\pi, \quad k_m = 5000$$

2<sup>nd</sup> order factor

- then we get

$$c_1 = \frac{2}{16000\pi \cdot 5000} = 7.9577 \text{ nF}, \quad R_1 = R_2 = 5k\Omega$$

$$c_2 = \frac{1/2}{16000\pi \cdot 5000} = 1.9894 \text{ nF}$$

- and for the 1<sup>st</sup> order factor

$$R = 5k\Omega, \quad C = \frac{1}{5000 \cdot 16000\pi} = 3.9789 \text{ nF}$$

High-pass Filter:  $\omega_c = 2\pi \cdot 1000$

$$|H(j\omega)| = \frac{(\omega/\omega_c)^n}{\sqrt{1 + (\omega/\omega_c)^{2n}}}$$

$$\cancel{-20dB} = 20 \log \frac{(2\pi \cdot 400 / 2\pi \cdot 1000)^n}{\sqrt{1 + (2\pi \cdot 400 / 2\pi \cdot 1000)^{2n}}}$$

$$\Rightarrow -20 = \log \frac{0.4^n}{\sqrt{1 + (0.4)^{2n}}}$$

$$\Rightarrow 0.1 = \frac{0.4^n}{\sqrt{1 + 0.4^{2n}}} \Rightarrow 0.01 = \frac{0.4^{2n}}{1 + 0.4^{2n}}$$

$$\Rightarrow 0.99 \cdot 0.4^{2n} = 0.01 \Rightarrow 0.4^{2n} = \frac{1}{99}$$

$$\Rightarrow 2n = \frac{\log(1/99)}{\log(0.4)} \Rightarrow n = 2.5075$$

Hence;

-the order is 3

$$H_{HPF}(s) = \frac{1}{(s+1)(s^2+s+1)}$$

1<sup>st</sup>-order factor:  $R=1\Omega$ ,  $C=1\text{F}$  (prototype version)

$$k_f = 2\pi \cdot 1000 = 2000\pi, 50 \cdot 10^{-9} = \frac{1}{2000\pi \cdot k_m}$$

$$\Rightarrow k_m = 3183.1$$

$$R = 3183.1 \cdot 1 = 3183.1 \text{ k}\Omega$$

2<sup>nd</sup>-order factor:  $R_2 = 0.5\Omega$ ,  $R_1 = 2\Omega$ ,  $C = 1\text{F}$  (prototype)

$$R_1 = 3183.1 \cdot 2 = 6366.2 \text{ k}\Omega$$


$$R_2 = 3183.1 \cdot 0.5 = 1591.5 \text{ k}\Omega$$

- and for the passband gain, we have


$$20 \text{ dB} = 20 \log_{10} K \Rightarrow K = 10 = \frac{R_f}{R_i}$$

- choosing  $R_i = 5\text{k}\Omega$ ,  $R_f = 50\text{k}\Omega$


O.

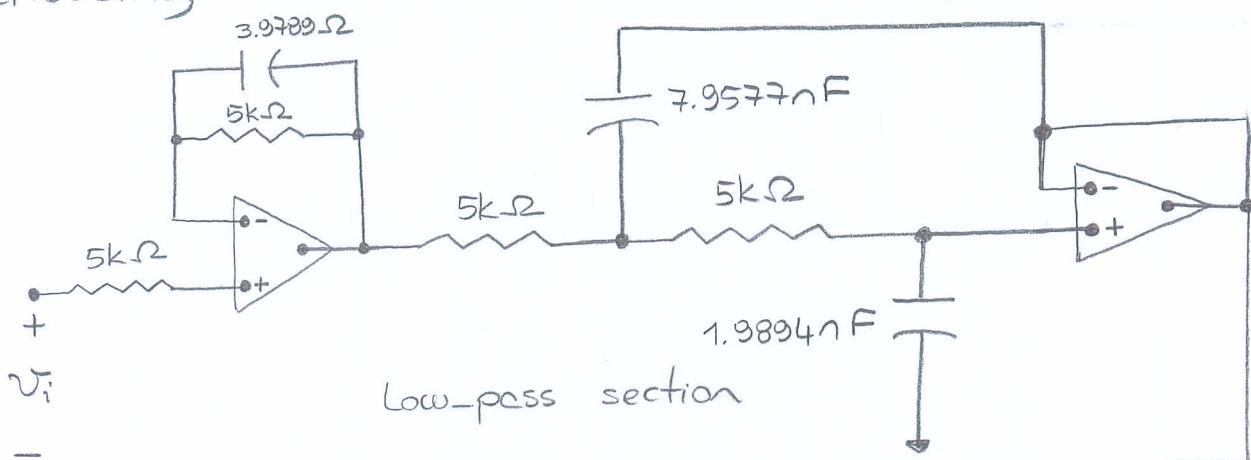

Low-pass section

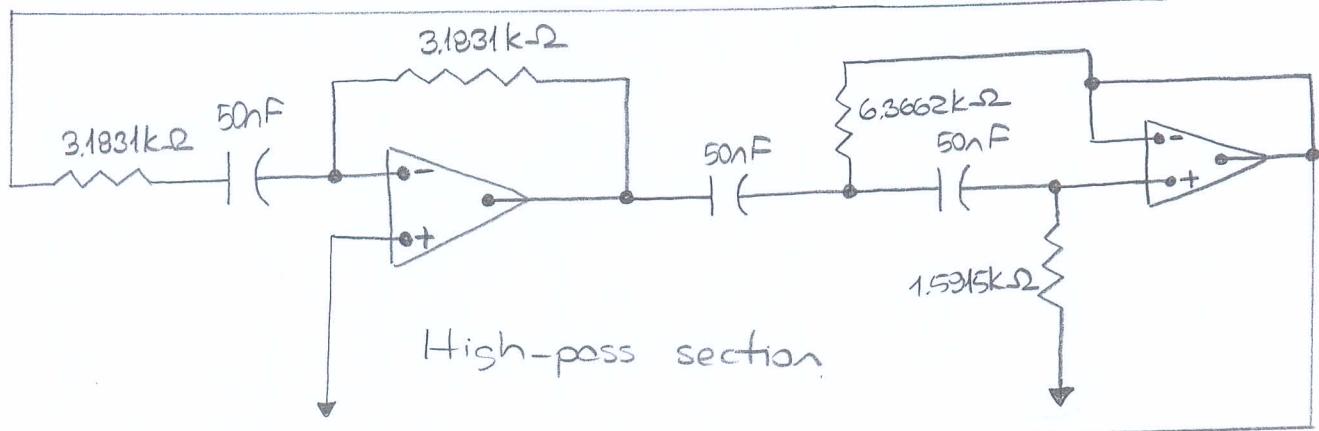

High-pass section

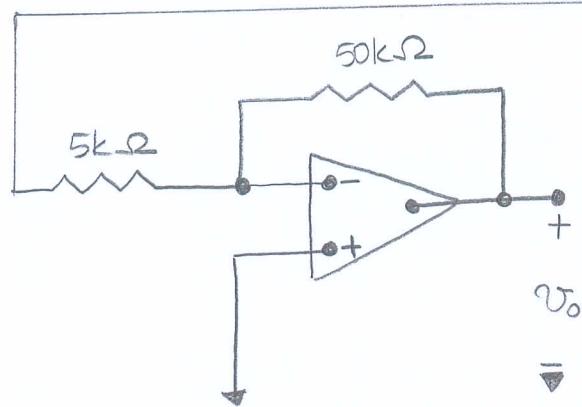

Gain-amplifier section

Problem 6) Using the "twin-T notch filter" circuit diagram,

a. design a narrow-band bandreject filter having a center frequency of 4kHz, and a quality factor of 15. Base the design on C=150nF.

b. draw the circuit diagram of the filter and label all component values on the diagram.

c. what is the scaled transfer function of the filter?

**Solution.** Note that we have

$$H(s) = \frac{s^2 + (1/R^2 C^2)}{s^2 + \frac{4(1-\sigma)}{RC} s + \frac{1}{R^2 C^2}}$$

$$\triangleq \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

where

$$\omega_0^2 = \frac{1}{R^2 C^2}, \quad \beta = \frac{4(1-\sigma)}{RC}$$

a.

Hence;

-we start with prototype version, i.e.  $R=1\Omega$ ,  $C=1F$

$$k_f = 2\pi \cdot 4000 = 8000\pi, \quad 150 \cdot 10^{-9} = \frac{1}{8000\pi \cdot k_m}$$

$$\Rightarrow k_m = 265.2582$$

$$\Rightarrow R = 265.82 \cdot 1 = 265.82 \Omega$$

-we also have


$$\frac{4(1-\sigma)}{RC} = \beta \quad \Rightarrow \quad 4(1-\sigma) = \frac{\beta}{\omega_0} = \frac{1}{Q}$$

$\sim (1/\omega_0)$

$$\Rightarrow 1-\sigma = \frac{1}{4Q} \Rightarrow \sigma = 1 - \frac{1}{4Q} = 1 - \frac{1}{4 \cdot 15} = \frac{59}{60}$$

$$\Rightarrow \sigma = 0.9833$$

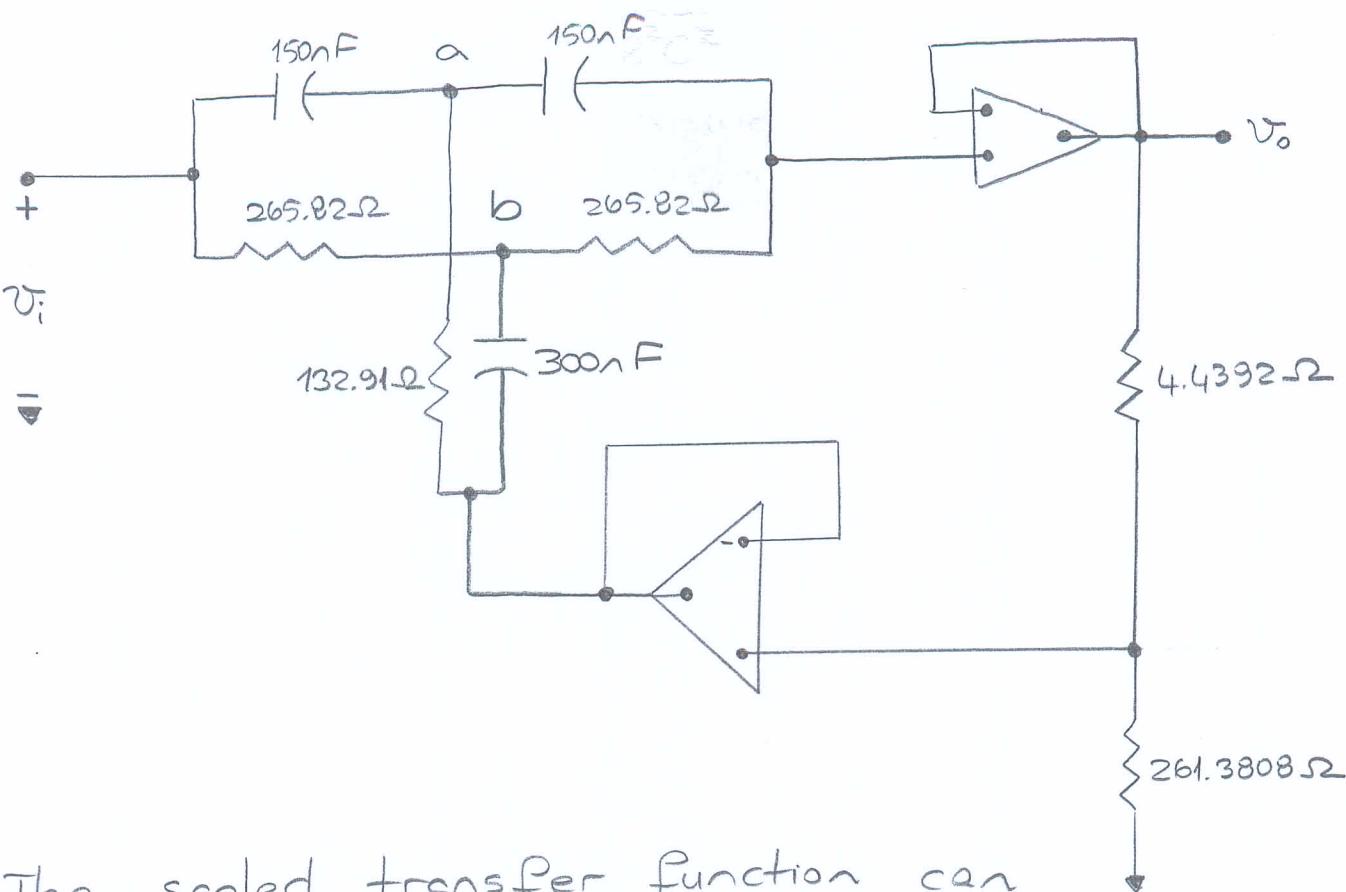b. We shall draw the circuit diagram of the filter as follows:



C. The scaled transfer function can be written as

$$\omega_0 = 2.5133 \cdot 10^4 \text{ rad/s}$$

$$\beta = \frac{\omega_0}{\Omega} = \frac{2.5133 \cdot 10^4}{15} = 1.6755 \cdot 10^3$$

$$H(s) = \frac{s^2 + 6.3165 \cdot 10^8}{s^2 + 1.6755 \cdot 10^3 s + 6.3165 \cdot 10^8}$$