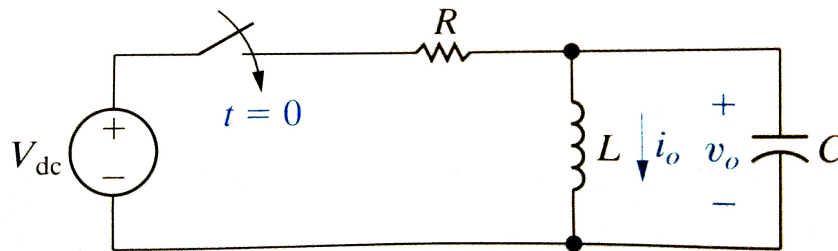


EEEN 202 Electrical and Electronic Circuits II
Homework 01**Due: 15-March-2019**
Friday 17:00**Problem 1)****Figure P1**

The switch in Figure P1 has been open for a long time. At $t = 0$, the switch is closed.

- Derive the integro-differential equation that governs the behavior of the voltage v_o for $t \geq 0$.
- Show that

$$V_o(s) = \frac{\frac{V_{dc}}{RC}}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)}$$

- Show that

$$I_o(s) = \frac{\frac{V_{dc}}{RLC}}{s \left[s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right) \right]}$$

Problem 2)

Find $f(t)$ for each of the following equations.

-


$$F(s) = \frac{10s^2 + 512s + 7186}{s^2 + 48s + 625}$$

-

$$F(s) = \frac{(s + 5)^2}{s(s + 1)^2}$$


-

$$F(s) = \frac{s^3 + 5s^2 - 50s - 100}{s^2 + 13s + 40}$$

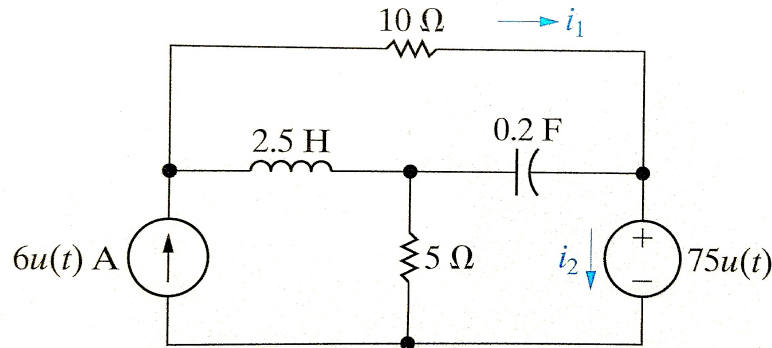Problem 3)**Figure P3**

There is no energy stored in the Figure P4. At the time sources are energized;

- Find $I_1(s)$ and $I_2(s)$.
- Use the initial-value and final-value theorems to check the initial values of $i_1(t)$ and $i_2(t)$.
- Find $i_1(t)$ and $i_2(t)$ for $t > 0$.

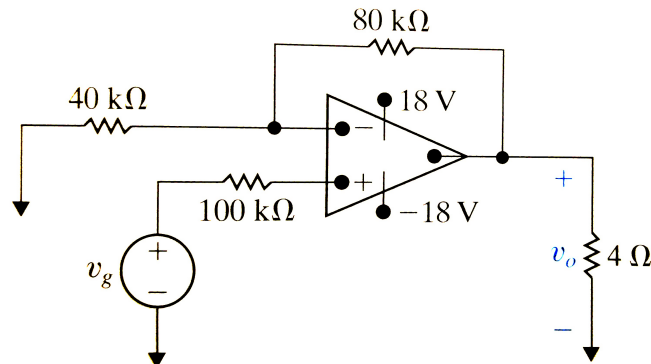Problem 4)**Figure P4**

The op amp in the noninverting amplifier circuit of Fig. P4 has an input resistance of $500\text{ k}\Omega$, an output resistance of $1\text{ k}\Omega$, and an open loop gain of 10,000. Assume that the op amp is operating in the linear region.

- Calculate the voltage gain (v_o/v_g).
- Find the inverting and non-inverting input voltages v_n and v_p (in millivolts) if $v_g = 1\text{ V}$.
- Calculate the difference ($v_p - v_n$) in microvolts when $v_g = 1\text{ V}$.
- Find the current drain in picoamperes on the signal source v_g when $v_g = 1\text{ V}$.
- Repeat (a)-(d) assuming ideal op-amp