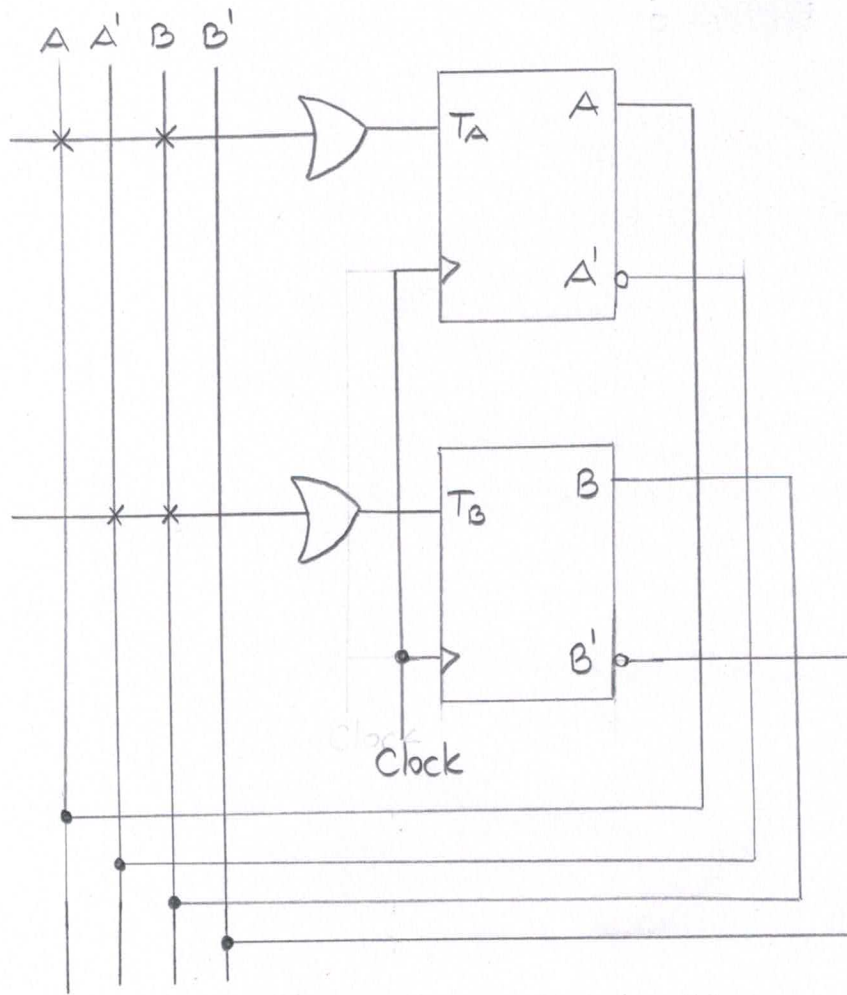


Problem 1) Derive the state table and the state diagram of the sequential circuit shown as follows:



Explain the function that the circuit performs.

Solution. We have

$$T_A = A + B$$

$$T_B = A' + B$$

Hence;

$$\begin{aligned} A(t+1) &= A \oplus T_A \\ &= A \oplus (A + B) \\ &= A \oplus A + A \oplus B \\ &= 0 + A \oplus B \\ &= A \oplus B \end{aligned}$$

$$B(t+1) = B \oplus T_B$$

$$= B \oplus (A' + B)$$

$$= B \oplus A' + B \oplus B$$


$$= B \oplus A' + 0$$

$$= B \oplus A'$$

AB	
00	01
01	10
10	10
11	01

$A(t+1), B(t+1)$

"state table"

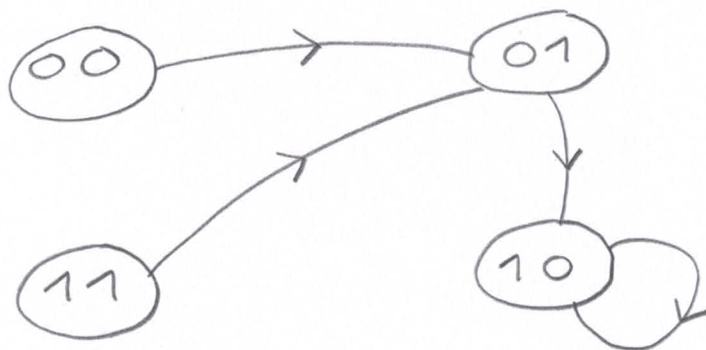

- the circuit is a counter with a repeated sequence of $0 \rightarrow 1 \rightarrow 2 \rightarrow 2 \rightarrow 2 \dots$ and $3 \rightarrow 1 \rightarrow 2 \rightarrow 2 \dots$

Problem 2) A sequential circuit has two JK flip-flops A and B, two inputs x and y, and one output z. The flip-flop input equations and circuit output equation are


$$J_A = Bx + B'y' \quad K_A = B'xy'$$

$$J_B = A'x \quad K_B = A + xy'$$

$$z = Ax'y' + Bx'y'$$

- Draw the logic diagram for the circuit.
- Tabulate the state table.
- Derive the state equations for A and B.

Solution.

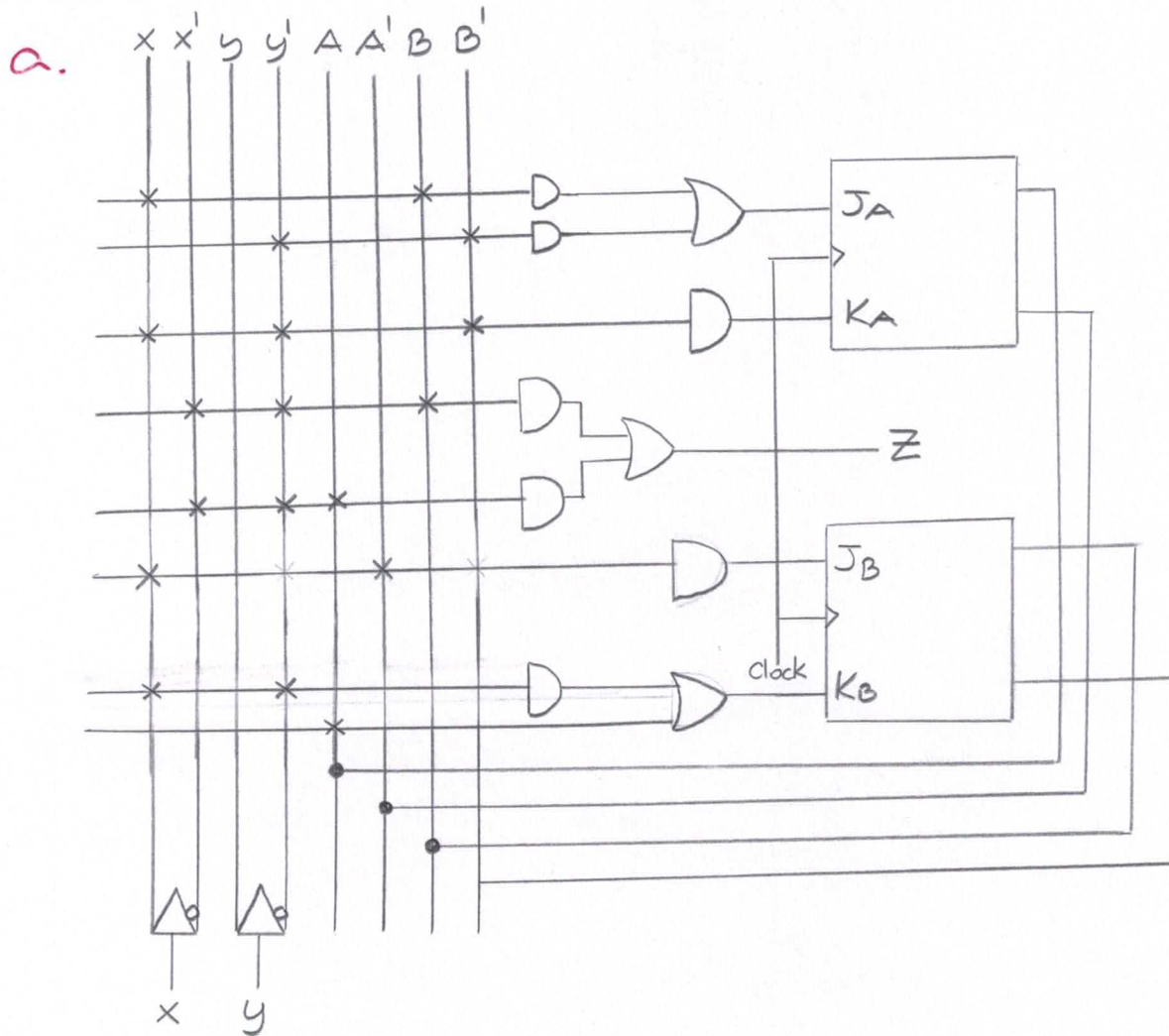

b. We obtain

$$A(t+1) = J_A A' + K_A A$$

$$= (Bx + B'y')A' + (B'xy')A$$

$$= xA'B + y'A'B' + AB + x'A + yA$$

AB	00	01	11	10
xy				
00	1		1	1
01			1	1
11		1	1	1
10	1	1	1	

$$A(t+1) = x'A + yA + xB + y'A'B'$$

$$B(t+1) = J_B B + K_B B$$

$$= A'x B' + (A + xy')' B$$

$$= x A' B' + A' (x' + y) B$$

$$= x A' B' + x' A' B + y A' B$$

x \ y		00	01	11	10
		00	01	11	10
0	0	10, 1	01, 0	10, 0	10, 0
0	1	00, 1	01, 0	10, 0	10, 0
1	1	01, 1	11, 0	10, 0	10, 0
1	0	11, 0	10, 0	10, 0	00, 0

$$A(t+1), B(t+1), Z$$


c. We have already derived in part b as

$$A(t+1) = x'A + yA + xB + y'A'B'$$

$$B(t+1) = xA'B' + x'A'B + yA'B$$

Problem 3) Derive the state diagram of a sequential circuit system with one input X and one output Z such that $Z=1$ if and only if the binary bit pattern of 10011 is recognized or detected throughout the input sequence.

Solution.

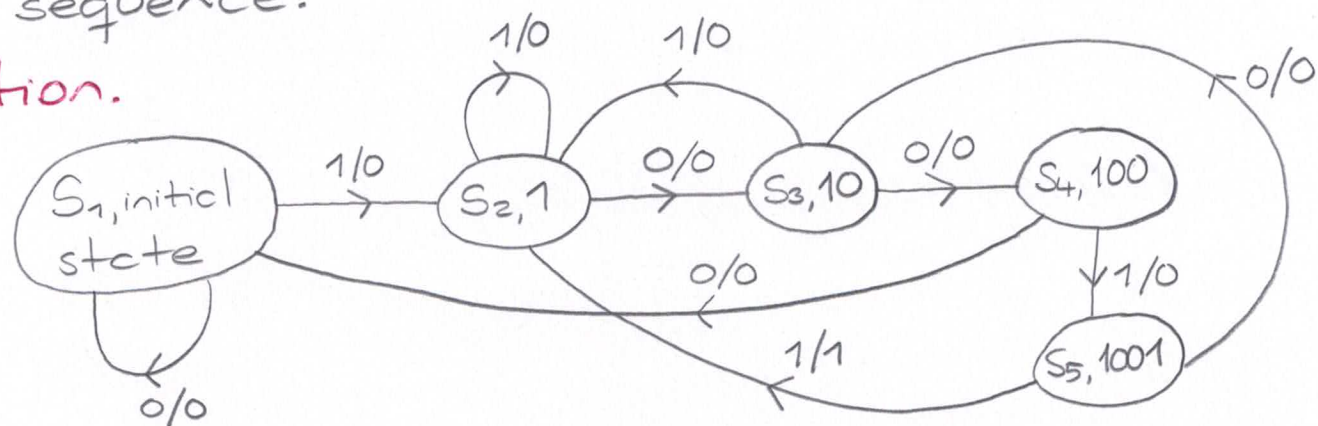

Problem 4) Design a sequential circuit with two D type flip-flops A and B and one input x.

a. When $x = 0$, the state of the circuit remains the same. When $x = 1$, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats.

b. When $x = 0$, the state of the circuit remains the same. When $x = 1$, the circuit goes through the state transitions from 00 to 11, to 01, to 10, back to 00, and repeats.

Solution.

a.

AB \ x	0	1
00	00	01
01	01	11
11	11	10
10	10	00


$A(t+1), B(t+1)$

x \ AB	00	01	11	10
0			1	1
1		1	1	

$$A(t+1) = D_A = x'A + xB$$

x \ AB	00	01	11	10
0		1	1	
1	1	1		

$$B(t+1) = D_B = x'B + xA'$$

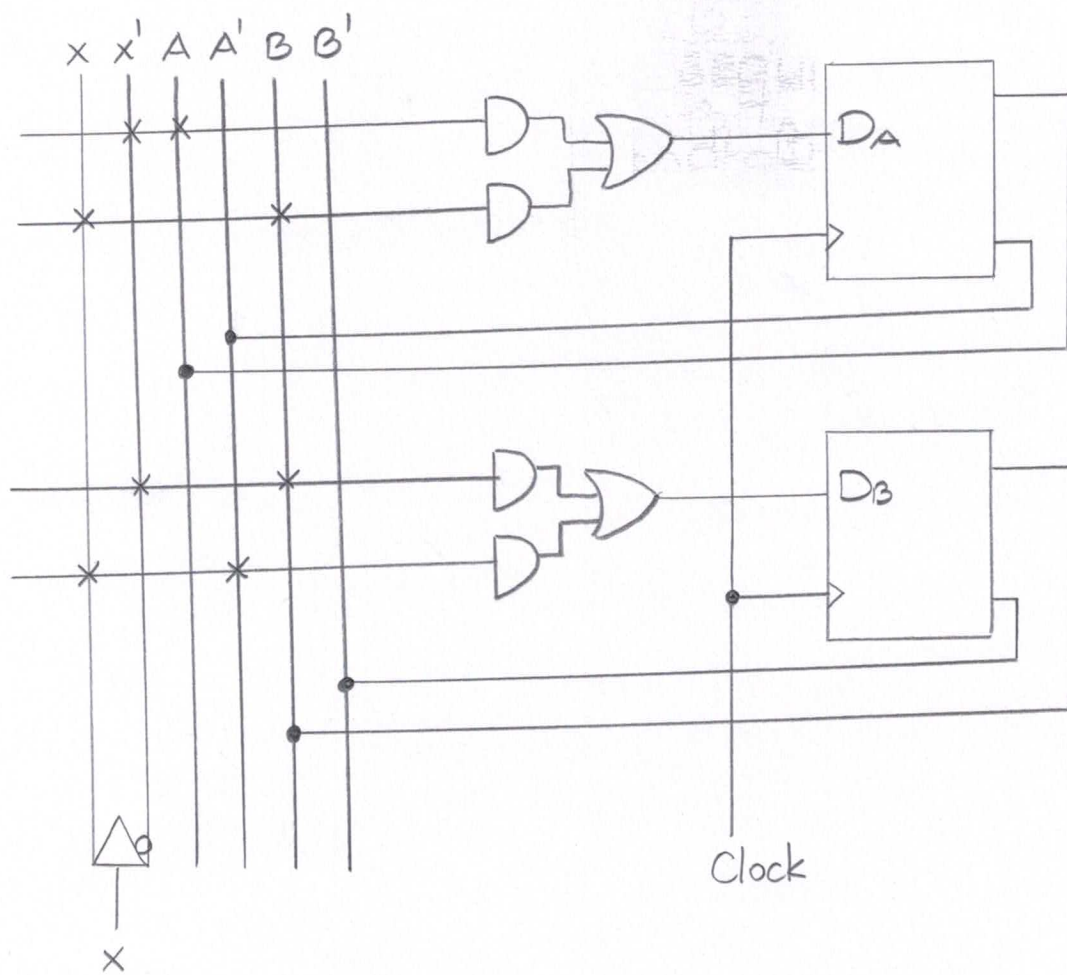

b.

AB \ x	0	1
00	00	11
01	01	10
11	11	01
10	10	00

$A(t+1), B(t+1)$

x \ AB	00	01	11	10
0			1	1
1	1	1		

$$A(t+1) = D_A = x'A + xA' = x \oplus A$$

x \ AB	00	01	11	10
0		1	1	
1	1		1	

$$B(t+1) = D_B = x'B + AB + xA'B'$$

