


### Selected Problems III

**Problem 1)** Use a 25mH inductor to design a low-pass, RL, passive filter with a cutoff frequency of 2.5kHz.

1. Specify the value of the resistor.

2. A load having a resistance of 750Ω is connected across the output terminals of the filter. What is the corner, or cutoff, frequency of the loaded filter in Hertz?

Solution. We have

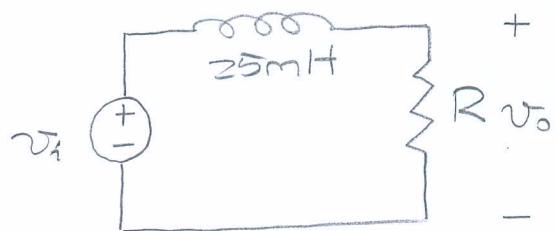


$$\frac{V_o(s)}{V_i(s)} = H(s) = \frac{R}{sL + R} = \frac{R/L}{s + R/L}$$

2.

$$\Rightarrow \omega_c = \frac{R}{L} \Rightarrow 2\pi(2.5 \cdot 10^3) = \frac{R}{25 \cdot 10^{-3}}$$

$$\Rightarrow R = 392.6991 \Omega$$

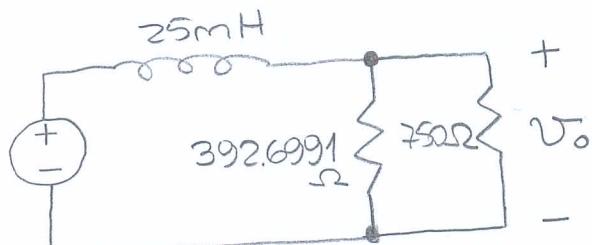


$$R_{\text{eq}} = \frac{392.6991 \cdot 750}{392.6991 + 750} \\ = 257.7444 \Omega$$

$$\omega_c = \frac{257.7444}{25 \cdot 10^{-3}} = 10,3098 \cdot 10^3 \text{ rad/s}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{10,3098}{2\pi} \cdot 10^3 = 1,6409 \text{ kHz OR } 1640.9 \text{ Hz}$$

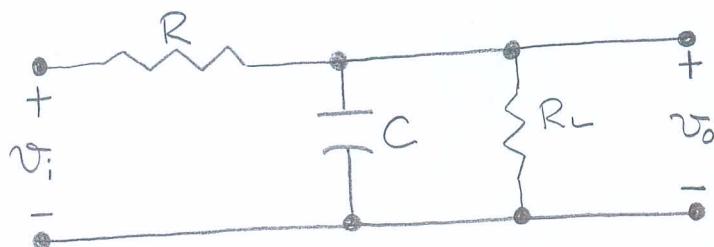**Problem 2)** A loaded low-pass filter circuit is shown as



- a. Derive the expression for the voltage transfer function  $V_o/V_i$ .
- b. At what frequency will the magnitude of  $H(j\omega)$  be maximum?
- c. What is the maximum value of the magnitude of  $H(j\omega)$ ?
- d. At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?

Solution.

$$2. \frac{1}{sc} \parallel R_L \Rightarrow Z_{eq} = \frac{(1/sc) R_L}{\frac{1}{sc} + R_L} = \frac{R_L}{1+sR_L C}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{R_L}{1+sR_L C}}{R + \frac{R_L}{1+sR_L C}} = \frac{R_L}{sRR_L C + R + R_L}$$

$$= \frac{1/RC}{s + \frac{R + R_L}{RR_L C}}$$

$$3. |H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + \left(\frac{R+R_L}{RR_L C}\right)^2}} = \frac{R_L / R + R_L}{\sqrt{1 + \left[\frac{\omega}{(R+R_L)/RR_L C}\right]^2}}$$


$\Rightarrow |H(j\omega)|$  is maximum when  $\omega = 0$

$$2. |H(j0)| = \frac{1/RC}{R+R_L/RR_L C} = \frac{R_L}{R+R_L} \triangleq H_{max}$$

$$4. |H(j\omega_c)| = \frac{1}{\sqrt{1 + \left[\frac{\omega_c}{(R+R_L)/RR_L C}\right]^2}} \quad H_{max} = \frac{1}{\sqrt{2}} H_{max}$$

$$\Rightarrow \omega_c = \frac{R+R_L}{RR_L C}$$

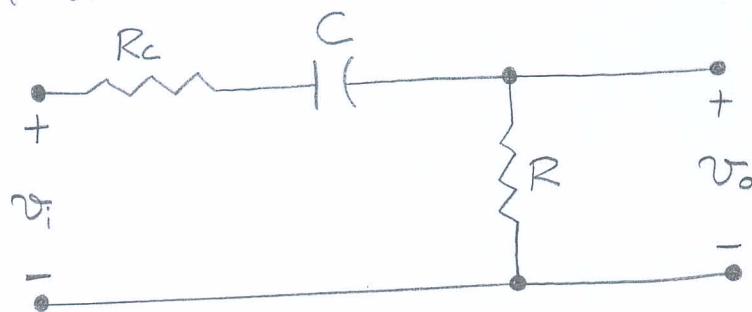Problem 3) Consider a modified high-pass filter circuit shown as



1. Derive the expression for  $H(s)$  where  $H(s) = \frac{V_o}{V_i}$ .
2. At what frequency will the magnitude of  $H(j\omega)$  be maximum?
3. What is the maximum value of the magnitude of  $H(j\omega)$ ?
4. At what frequency will the magnitude of  $H(j\omega)$  equal its maximum value divided by  $\sqrt{2}$ ?

Solution. We have

a.

$$H(s) = \frac{V_o}{V_i} = \frac{R}{R_c + \frac{1}{sC} + R} = \frac{sRC}{s(R+R_c)C + 1}$$

$$= \frac{R}{R+R_c} \frac{s}{s + \frac{1}{(R+R_c)C}}$$

b.

$$H(j\omega) = \frac{R}{R+R_c} \frac{j\omega}{j\omega + \frac{1}{(R+R_c)C}}$$

$$|H(j\omega)| = \frac{R}{R+R_c} \frac{\omega}{\sqrt{\omega^2 + \frac{1}{(R+R_c)^2 C^2}}} = \frac{R}{R+R_c} \frac{1}{\sqrt{1 + \frac{1/(R+R_c)^2 C^2}{\omega^2}}}$$

when  $\omega \rightarrow \infty$ ,  $|H(j\omega)| \rightarrow H_{max}$

$$H_{max} = \lim_{\omega \rightarrow \infty} |H(j\omega)| = \lim_{\omega \rightarrow \infty} \frac{R}{R+R_c} \cdot \frac{1}{\sqrt{1 + \frac{1/(R+R_c)^2 C^2}{\omega^2}}} \\ = \frac{R}{R+R_c}$$

i. We have


$$|H(j\omega)| = \underbrace{\frac{R}{R+R_c}}_{H_{max}} \cdot \frac{1}{\sqrt{1 + \frac{1/(R+R_c)^2 C^2}{\omega_c^2}}} = \frac{1}{\sqrt{2}} \cdot \frac{R}{\underbrace{R+R_c}_{H_{max}}}$$

$$\Rightarrow \frac{1/(R+R_c)^2 C^2}{\omega_c^2} = 1 \Rightarrow \omega_c = \frac{1}{(R+R_c)C}$$

**Problem 4)** Using a 25mH inductor, design a high-pass, RL, passive filter with a cutoff frequency of 160 kHz/s.


- a. Specify the value of the resistance.
- b. Assume the filter is connected to a pure resistive load. The cutoff frequency is not to drop below 150 kHz/s. What is the smallest load resistor that can be connected across the output terminals of the filter?

**Solution.** We have

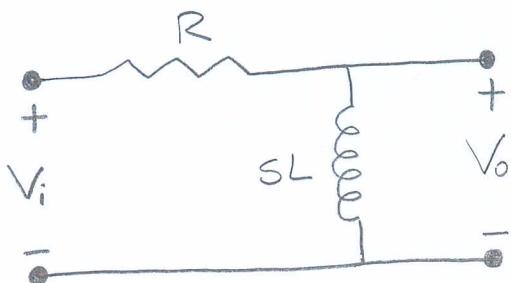

$$H(s) = \frac{V_o}{V_i} = \frac{sL}{sL + R} \\ = \frac{s}{s + (R/L)}$$
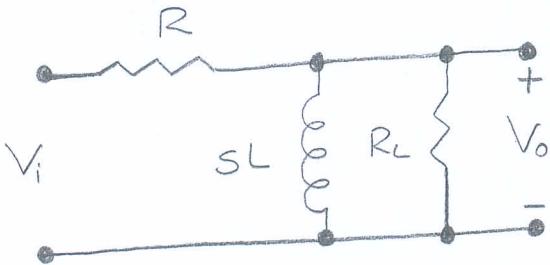
$$1. \frac{R}{L} = \frac{R}{25 \cdot 10^3} = 160 \cdot 10^3 \Rightarrow R = 4 \text{ k}\Omega$$



$$H(s) = \frac{V_o}{V_i} = \frac{\frac{(sL)RL}{sL+RL}}{R + \frac{(sL)RL}{sL+RL}} = \frac{sRL}{s(R+RL)L+RR_L}$$

$$= \frac{R_L}{R+R_L} \frac{s}{s + \frac{RR_L}{(R+R_L)L}}$$

$$H(j\omega) = \frac{R_L}{R+R_L} \frac{j\omega}{j\omega + \frac{RR_L}{(R+R_L)L}}$$

$$|H(j\omega)| = \frac{R_L}{R+R_L} \frac{\omega}{\sqrt{\omega^2 + \left[ \frac{RR_L}{(R+R_L)L} \right]^2}}$$

$$= \frac{R_L}{R+R_L} \frac{1}{\sqrt{1 + \left[ \frac{RR_L}{\omega(R+R_L)L} \right]^2}}$$

Hence;

$$H_{max} = \frac{R_L}{R+R_L} \quad \text{and} \quad \omega_c = \frac{RR_L}{(R+R_L)L}$$

$$\frac{4 \cdot 10^3 \cdot R_L}{(4 \cdot 10^3 + R_L) \cdot 25 \cdot 10^3} \geq 150 \cdot 10^3$$


$$\Rightarrow 4R_L \geq 15 \cdot 10^3 + 3.75 R_L$$

$$\Rightarrow 0.25 R_L \geq 15 \cdot 10^3 \Rightarrow R_L \geq 60 k\Omega$$

Thus;

$$[R_L]_{\min} = 60 k\Omega$$

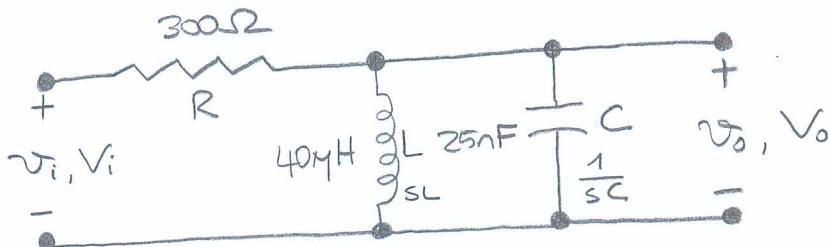Problem 5) Consider the following bandpass filter shown as



Find  $\omega_0$ ,  $Q$ ,  $\omega_{c1}$ ,  $\omega_{c2}$ , and  $\beta$ .

Solution. We have

$$H(s) = \frac{V_o}{V_i} = \frac{\frac{SL(1/sC)}{SL+(1/sC)}}{R + \frac{SL(1/sC)}{SL+(1/sC)}} = \frac{L/C}{R(SL + \frac{1}{sC}) + \frac{L}{C}}$$

$$= \frac{sL}{s^2RLC + R + sL} = \frac{s(1/RC)}{s^2 + s(1/RC) + (1/LC)} \triangleq \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

Therefore;

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{40 \cdot 10^{-6} \cdot 25 \cdot 10^{-9}} = 10^{12} \Rightarrow \omega_0 = 10^6 \text{ rad/s}$$

$$\beta = \frac{1}{RC} = \frac{1}{300 \cdot 25 \cdot 10^{-9}} = 133.3333 \text{ krad/s}$$

$$Q = \frac{\omega_0}{\beta} = \frac{10^6}{133.3333 \cdot 10^3} = 7.5$$

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$= 935.55 \text{ krad/s}$$


$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$= 1068.5 \text{ krad/s}$$

**Problem 6)** Design a series RLC bandpass filter with a quality factor of 5 and a center frequency of 20 krad/s using a 0.05 nF capacitor

2. Draw your circuit by labeling the component values and output voltage.
3. Calculate  $\beta$ ,  $\omega_{c1}$  and  $\omega_{c2}$ .

**Solution:**

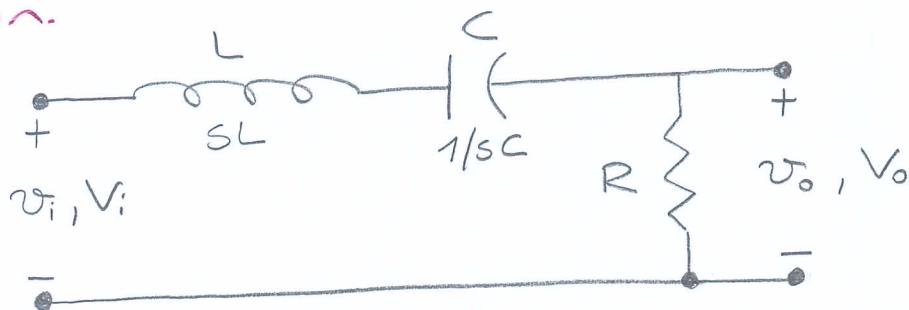

$$Q = \frac{\omega_0}{\beta} \Rightarrow 5 = \frac{20 \cdot 10^3}{\beta} \Rightarrow \beta = 4 \cdot 10^3 \text{ rad/s}$$

$$H(s) = \frac{V_o}{V_i} = \frac{R}{sL + \frac{1}{sC} + R} = \frac{sRC}{s^2LC + 1 + sRC} = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}$$


$$\triangle = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \Rightarrow (20 \cdot 10^3)^2 = \frac{1}{L \cdot 0.05 \cdot 10^{-6}}$$

$$\Rightarrow L = \frac{1}{0.05 \cdot 400} = 50 \text{ mH}$$

and
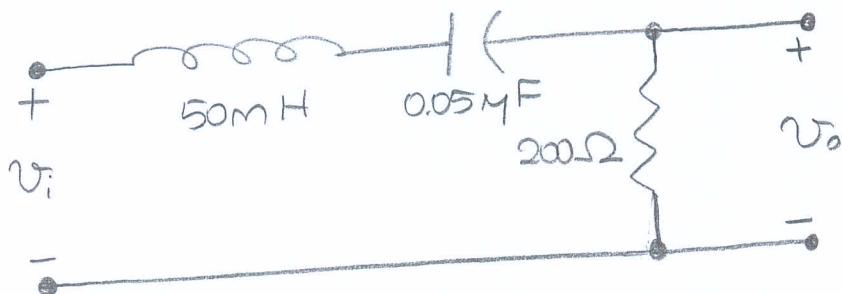
$$\beta = \frac{R}{L} \Rightarrow 4 \cdot 10^3 = \frac{R}{50 \cdot 10^{-3}} \Rightarrow R = 200 \Omega$$



b.  $\beta = 4 \cdot 10^3$


$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\approx 18.1 \text{ krad/s}$$

$$\omega_{c2} \approx \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$= 22.1 \text{ krad/s}$$

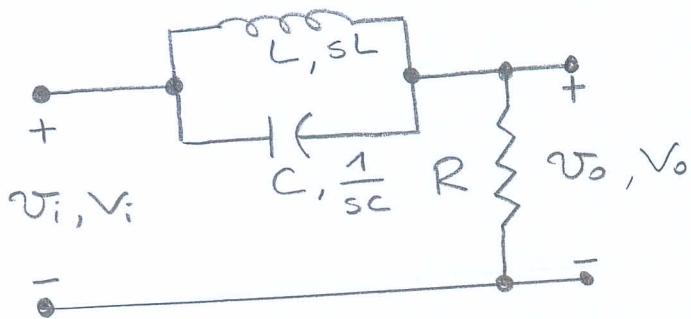Problem 7) Consider the following RLC circuit



- a. Show that the circuit is a bandreject filter via a qualitative analysis.
- b. Support the qualitative analysis by finding the voltage transfer function of the filter.
- c. Derive an expression for the center frequency  $\omega_0$ .
- d. Derive the expressions for  $\omega_{c1}$  and  $\omega_{c2}$ .
- e. What is the expression for the bandwidth of the filter?
- f. What is the expression for the quality factor of the filter?

Solution.

- c. When  $\omega=0$ , inductor is short-circuit and capacitor is open-circuit
  - (i) that is, the output voltage is same as the input voltage both in magnitude and phase
- When  $\omega \rightarrow \infty$ , inductor is open-circuit and capacitor is short-circuit
  - (ii) therefore, the output voltage is again same as the input voltage both in magnitude and phase
- For  $0 < \omega < \infty$ , there will be some voltage drop across L and C
  - (iii) thus reducing the output voltage from the input voltage

At the resonant frequency of the parallel combination of L and C, the equivalent impedance is infinite, hence

(b) the output voltage is zero when  $\omega = \omega_0$

- At frequencies lower or greater than  $\omega_0$ , the output voltage will be less than the input voltage

∴ The circuit behaves like a band reject filter.

c. We have

$$\begin{aligned}
 H(s) &= \frac{V_o}{V_i} = \frac{R}{\frac{sL(\frac{1}{sc})}{sL + \frac{1}{sc}} + R} = \frac{R}{\frac{sL}{s^2LC+1} + R} \\
 &= \frac{R(s^2LC+1)}{s^2LCR+R+sL} = \frac{s^2 + (1/LC)}{s^2 + (1/RC)s + (1/LC)} \\
 &\triangleq \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}
 \end{aligned}$$

Band-reject filter characteristics

c. It follows that

$$H(j\omega) = \frac{-\omega^2 + \omega_0^2}{-\omega^2 + j\beta\omega + \omega_0^2} = 0 \quad \text{when } \omega = \omega_0, \omega_0^2 = \frac{1}{LC}, \omega_0 = \sqrt{\frac{1}{LC}}$$

$$d. H(j\omega) = \frac{-\omega^2 + \omega_0^2}{-\omega^2 + j\beta\omega + \omega_0^2}, |H(j\omega)| = \frac{\omega_0^2 - \omega^2}{\sqrt{\beta^2\omega^2 + (\omega_0^2 - \omega^2)^2}}$$

$$\Rightarrow |H(j\omega)| = \frac{1}{\sqrt{1 + \frac{\beta^2 \omega^2}{(\omega_0^2 - \omega^2)^2}}}$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{1 + \frac{\beta^2 \omega_c^2}{(\omega_0^2 - \omega_c^2)^2}}} = \frac{1}{\sqrt{2}} \cdot 1$$

$\overbrace{1}^1$

$$\Rightarrow \frac{\beta^2 \omega_c^2}{(\omega_0^2 - \omega_c^2)^2} = 1 \Rightarrow \frac{\beta \omega_c}{\omega_0^2 - \omega_c^2} = \pm 1$$

$$\Rightarrow \mp \omega_c^2 - \beta \omega_c \pm \omega_0^2 = 0 \quad \text{OR} \quad \omega_c^2 \mp \beta \omega_c \mp \omega_0^2 = 0$$

Hence;


$$\omega_{c1} = \frac{-\beta + \sqrt{\beta^2 + 4\omega_0^2}}{2} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\omega_{c2} = \frac{\beta + \sqrt{\beta^2 + 4\omega_0^2}}{2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

e.  $\omega_{c2} - \omega_{c1} = \beta = \frac{1}{RC}$

f.  $\varphi = \frac{\omega_0}{\beta} = \frac{\sqrt{1/LC}}{1/RC} = \sqrt{\frac{R^2 C^2}{L}} = R \sqrt{\frac{C}{L}}$

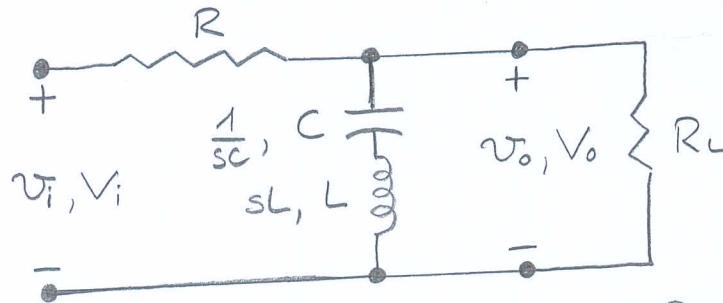Problem 8) Consider a loaded bandreject filter circuit shown as



- a. Find the voltage transfer function  $\frac{V_o}{V_i}$ .
- b. What is the expression for the center frequency?
- c. What is the expression for the bandwidth?
- d. What is the expression for the quality factor?
- e. Evaluate  $H(j\omega_0)$ ,  $H(j0)$ ,  $H(j\infty)$ .
- f. What are the expressions for the corner frequencies,  $\omega_1$  and  $\omega_{c2}$ ?

Solution. We have

$$H(s) = \frac{V_o}{V_i} = \frac{Z_{eq}}{R + Z_{eq}} \quad \text{where } Z_{eq} = \frac{\left(\frac{1}{sc} + sL\right) R_L}{\frac{1}{sc} + sL + R_L}$$

$$\Rightarrow Z_{eq} = \frac{(1 + s^2 LC) R_L}{1 + s^2 LC + s R_L C}$$

Therefore;

$$H(s) = \frac{R_L + s^2 R_L L C / 1 + s^2 L C + s R_L C}{R + \frac{R_L + s^2 R_L L C}{1 + s^2 L C + s R_L C}}$$

$$= \frac{R_L + s^2 R_L L C}{R + R_L + s^2 (R + R_L) L C + s R R_L C}$$

$$= \frac{\frac{R_L C}{(R+R_L)LC}}{\frac{s^2 + (1/LC)}{s^2 + \frac{RR_L}{R+R_L} s + \frac{1}{LC}}} \triangleq \frac{\frac{R_L}{R+R_L}}{\frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}}$$

Bandreject  
filter  
characteristic  
PS 3.12

where

$$\omega_0^2 = \frac{1}{LC}, \quad \beta = \frac{RR_L}{(R+R_L)L}$$

2.  $\omega_0 = \sqrt{\frac{1}{LC}}$

3.  $\beta = \frac{RR_L}{(R+R_L)L}$

4.  $\phi = \frac{\omega_0}{\beta} = \frac{\sqrt{1/LC}}{\frac{RR_L}{(R+R_L)L}} = \frac{R+R_L}{RR_L} \sqrt{\frac{L}{C}}$

5.  $H(j\omega_0) = \frac{R_L}{R+R_L} \frac{-\omega_0^2 + \omega_0^2}{-\omega_0^2 + j\beta\omega_0 + \omega_0^2} = 0$

$$H(j0) = \frac{R_L}{R+R_L} \frac{0+\omega_0^2}{0+0+\omega_0^2} = \frac{R_L}{R+R_L}$$

$$H(j\infty) = \lim_{\omega \rightarrow \infty} \frac{-\omega^2 + \omega_0^2}{-\omega^2 + j\beta\omega + \omega_0^2} \left( \frac{R_L}{R+R_L} \right)$$

$$= \frac{R_L}{R+R_L} \lim_{\omega \rightarrow \infty} \frac{-1 + \left(\frac{\omega_0}{\omega}\right)^2}{-1 + j\beta \frac{1}{\omega} + \left(\frac{\omega_0}{\omega}\right)^2}$$

$$= \frac{R_L}{R+R_L} \frac{-1}{-1}$$

$$= \frac{R_L}{R+R_L}$$

$$|H(j\omega_c)| = \frac{R_L}{R+R_L} \frac{-\alpha_c^2 + \omega_0^2}{\sqrt{(\omega_0^2 - \omega_c^2)^2 + \beta^2 \omega_c^2}} = \frac{R_L}{R+R_L} \frac{1}{\sqrt{1 + \frac{\beta^2 \omega_c^2}{(\omega_0^2 - \omega_c^2)^2}}}$$

$$= \frac{1}{\sqrt{2}} \cdot \frac{R_L}{R+R_L}$$


$$\Rightarrow \frac{\beta^2 \omega_c^2}{(\omega_0^2 - \omega_c^2)^2} = 1 \Rightarrow \frac{\beta \omega_c}{\omega_0^2 - \omega_c^2} = \pm 1$$

- yielding two positive roots as

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

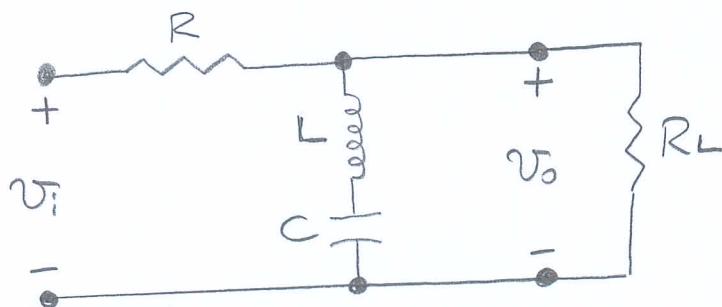Problem 9) Reconsider the loaded bandreject filter



$$R_L = 36 k\Omega$$

$$\omega_0 = 1 \text{ M rad/s}$$

$$C = 400 \text{ pF}$$

At very low and very high frequencies, the amplitude of the sinusoidal output voltage should be at least 96% of the amplitude of the sinusoidal input voltage.

- a. Specify the numerical values of R and L.  
 b. What is the quality factor of the circuit?

Solution. We have

$$|H(j0)| = |H(j\infty)| = \frac{36 \cdot 10^3}{R + 36 \cdot 10^3} = \frac{96}{100}$$

$$\Rightarrow 0.96R + 0.96 \cdot 36 \cdot 10^3 = 36 \cdot 10^3$$

$$\Rightarrow \frac{0.96}{2} R = 0.04 \cdot \frac{36}{2} \cdot 10^3$$

$$\Rightarrow R = 1.5 \text{ k}\Omega$$

$$10^6 = \sqrt{\frac{1}{L \cdot 400 \cdot 10^{-12}}} \Rightarrow 10^{12} = \frac{1}{L \cdot 400 \cdot 10^{-12}}$$

$$\Rightarrow L = \frac{1}{400} = 2.5 \text{ mH}$$

2. Referring to Problem 8, we have

$$\beta = \frac{RR_L}{(R+R_L)L} = \frac{15\text{k} \cdot 36\text{k}}{(15\text{k}+36\text{k}) \cdot 2.5 \cdot 10^{-3}} = 576 \text{ k rad/s}$$

$$\alpha = \frac{\omega_0}{\beta} = \frac{10^6}{576 \cdot 10^3} = 1.7361$$