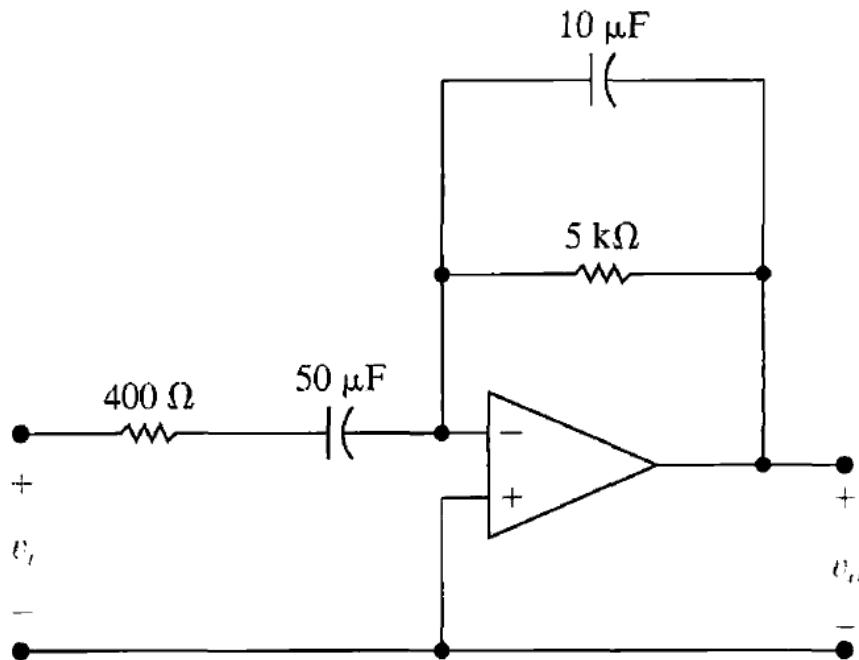


**EEEN 202 Electrical and Electronic Circuits II**  
**Homework 03****Due: 10-May-2019**  
**Friday 17:00****Problem 1)**

Consider the filter shown in Figure P1.

- Show that the circuit behaves as a band-pass filter. (Hint: Find the transfer for this circuit and show that it has the same form as the transfer function for a band-pass filter.)
- Find the center frequency, bandwidth and gain for this band-pass filter.
- Find the cutoff frequencies and the quality factor for this band-pass filter.

**Figure P1****Problem 2)**

- Using  $1\ \text{k}\Omega$  resistors and ideal op amps, design a low-pass unity-gain Butterworth filter that has a cutoff frequency of  $8\ \text{kHz}$  and is down at least  $48\ \text{dB}$  at  $32\ \text{kHz}$ .
- Draw a circuit diagram of the filter and label all the components.

**Problem 3)**

The periodic voltage source in the circuit shown in Figure P3 (a) has the waveform shown in Figure P3 (b).

- Derive the expression for  $C_n$ .
- Find the values of the complex coefficients  $C_0$ ,  $C_{-1}$ ,  $C_1$ ,  $C_{-2}$ ,  $C_2$ ,  $C_{-3}$ ,  $C_3$ ,  $C_{-4}$ , and  $C_4$  for the input voltage  $v_g$ , if  $V_m = 54$  V and  $T = 10\pi$   $\mu$ s.
- Repeat **b)** for  $v_o$ .
- Use the complex coefficients found in **c)** to estimate the average power delivered to the 250 k $\Omega$  resistor.


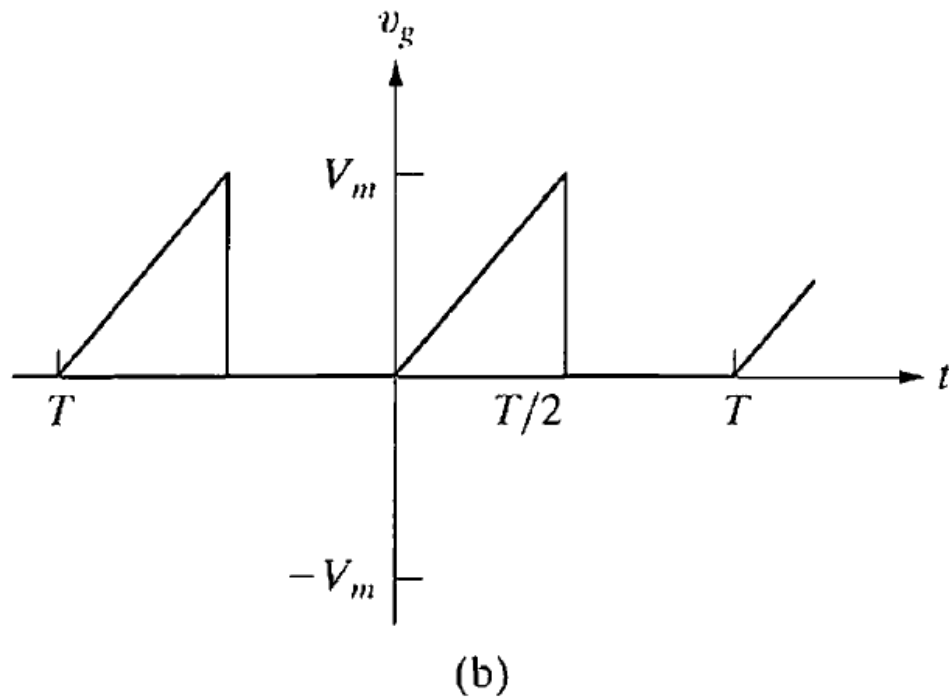
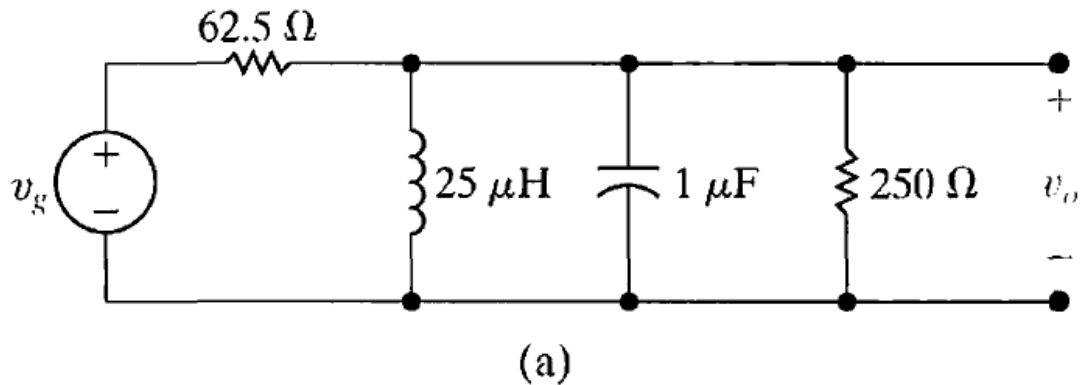


Figure P3

**Problem 4)**

Find the Fourier series of the periodic functions shown in Figure P4 (a) and (b).

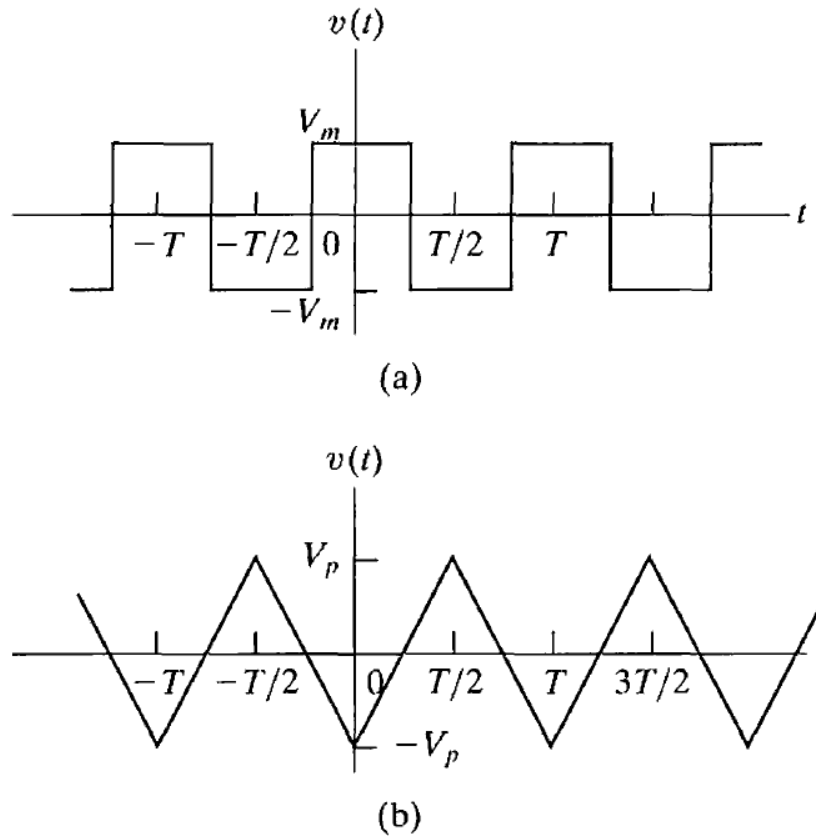

**Figure P4**

**Problem 5)**

The voltage and current at the terminals of a network are

$$v = 15 + 400 \cos 500t + 100 \sin 1500t \text{ V,}$$

$$i = 2 + 5 \sin (500t + 60^\circ) + 3 \cos (1500t - 15^\circ) \text{ A.}$$

The current is in the direction of the voltage drop across the terminals.

- What is the average power at the terminals?
- What is the rms value of the voltage?
- What is the rms value of the current?