

## The Laplace transform in circuit analysis

- Laplace transform has two attractive characteristics :
  1. It transforms a set of linear constant-coefficient differential equations  
↳ into a set of linear polynomial equations.
  2. It automatically introduces into the polynomial equations  
↳ the initial values of the current and voltage variables.
- We will show how we can skip writing time-domain integro-differential equations  
↳ and transforming them into the s-domain.

## Circuit elements in the s-domain

- We first write the time-domain equation  
↳ that relates the terminal voltage to the terminal current.
- Next we take the Laplace transform of the time-domain equation.

### a resistor in the s-domain


- From Ohm's law, we have
$$\vartheta = Ri$$
- because  $R$  is constant, the Laplace transform becomes

$$V = RI$$

where

$$V = \mathcal{L}\{\vartheta\} , \quad I = \mathcal{L}\{i\}$$

Hence ;

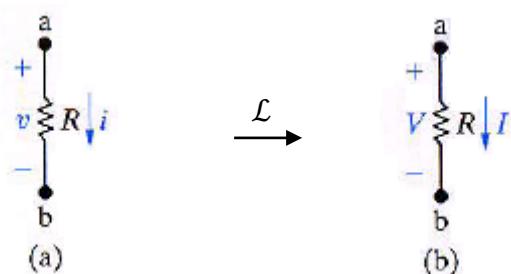

### an inductor in the s-domain




- We have

$$\vartheta = L \frac{di}{dt}$$

- and the Laplace transform of  $\vartheta$  gives

$$\begin{aligned} V &= L[sI - i(0^-)] \\ &= sLI - LI_0 \quad , \quad I_0 : i(0^-) \end{aligned}$$

Hence ;

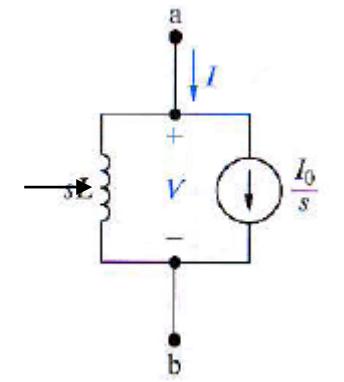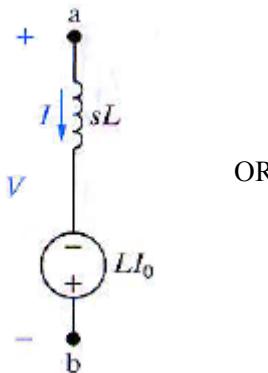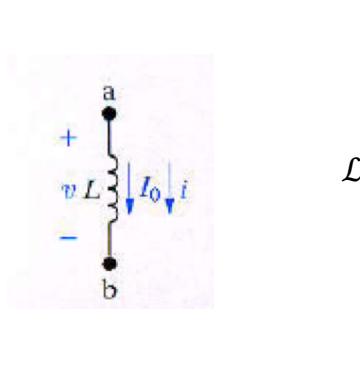

### a capacitor in the s-domain


- We have

$$i = C \frac{d\vartheta}{dt}$$

- Transforming into s-domain gives

$$\begin{aligned} I &= C[sV - \vartheta(0^-)] \\ &= sCV - CV_0 \quad , \quad V_0 : \vartheta(0^-) \end{aligned}$$

Thus ;

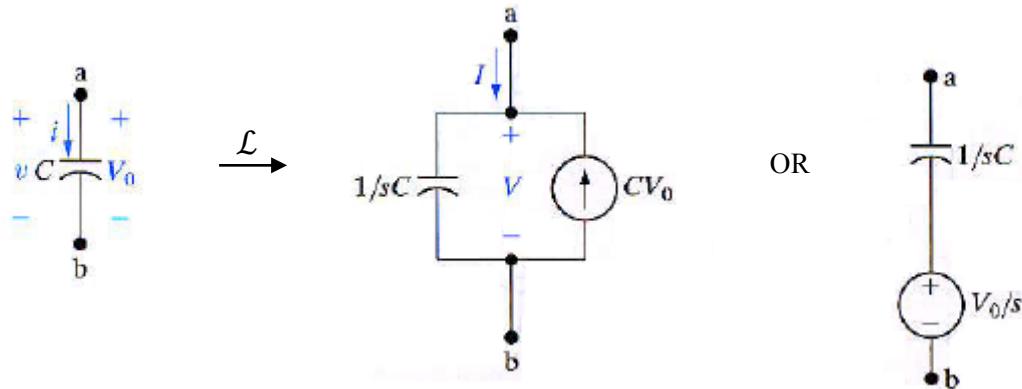


### Circuit analysis in the s-domain

- We shall now illustrate how to use the Laplace transform

→ to determine the transient behavior of linear lumped-parameter circuits.

### The natural response of an RC circuit

- We consider an RC circuit

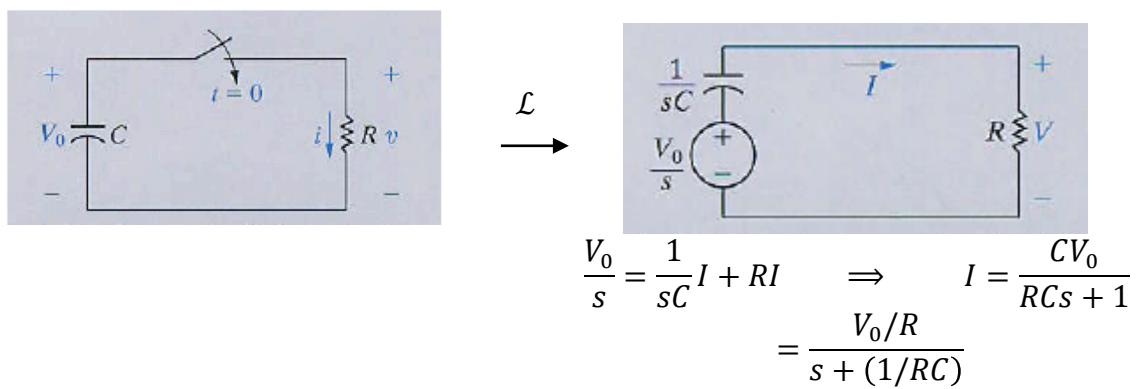

- Using inverse Laplace transform yields


$$i(t) = \frac{V_0}{R} e^{-t/RC} u(t)$$

- and applying Ohm's law gives


$$\vartheta(t) = Ri(t) = V_0 e^{-t/RC} u(t)$$
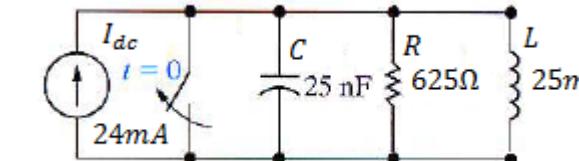
## The step response of a parallel RLC circuit

- We now analyze the parallel RLC circuit as follows



$\downarrow \mathcal{L}$

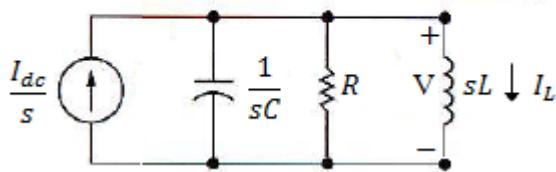

$$I_L = \frac{V}{sL}$$

$$\frac{V}{sC} + \frac{V}{R} + \frac{V}{sL} = \frac{I_{dc}}{s}$$

$$\rightarrow \left( sC + \frac{1}{R} + \frac{1}{sL} \right) V = \frac{I_{dc}}{s}$$

$$\rightarrow V = \frac{I_{dc}/C}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

- and

$$I_L = \frac{I_{dc}/LC}{s \left[ s^2 + \left( \frac{1}{RC} \right) s + \left( \frac{1}{LC} \right) \right]}$$

$$= \frac{384 \cdot 10^5}{s(s^2 + 64000s + 16 \cdot 10^8)} = \frac{384 \cdot 10^5}{(s + 32000 - j24000)(s + 32000 + j24000)}$$

$$= \frac{C_1}{s} + \frac{C_2}{s + 32000 - j24000} + \frac{C_2^*}{s + 32000 + j24000}$$

$$\rightarrow C_1 = \frac{384 \cdot 10^5}{16 \cdot 10^8} = 24 \cdot 10^{-3}$$

$$C_2 = \frac{384 \cdot 10^5}{s(s + 32000 + j24000)} \Big|_{s = -32000 + j24000}$$

$$= \frac{384 \cdot 10^5}{(-32000 + j24000)j48000}$$

$$= 20 \cdot 10^{-3} \angle 126.87^\circ$$

Hence;

$$i_L(t) = [24 \cdot 10^{-3} + 40 \cdot 10^{-3} e^{-32000t} \cos(24000t + 126.87^\circ)] u(t)$$

### **The transient response of a parallel RLC circuit**

- We now replace the dc current source with a sinusoidal current source

$$i_g = I_m \cos \omega t \text{ A}$$

- The s-domain expression for the source current is

$$I_g = \frac{s I_m}{s^2 + \omega^2}$$

- The voltage across the parallel elements is

$$V = \frac{\left(\frac{I_g}{C}\right)s}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)} = \frac{\left(\frac{I_m}{C}\right)s^2}{(s^2 + \omega^2)[s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)]}$$

from which

$$\begin{aligned} I_L &= \frac{V}{sL} = \frac{\left(\frac{I_m}{C}\right)s}{(s^2 + \omega^2)[s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)]} \\ &= \frac{384 \cdot 10^5 s}{(s - j\omega)(s + j\omega)(s + \alpha - j\beta)(s + \alpha + j\beta)} \end{aligned}$$

where

$$\omega = 40000, \quad \alpha = 32000, \quad \text{and } \beta = 24000$$

- Then we expand

$$I_L = \frac{C_1}{s - j40000} + \frac{C_1^*}{s + j40000} + \frac{C_2}{s + 32000 - j24000} + \frac{C_2^*}{s + 32000 + j24000}$$

$$\rightarrow C_1 = \frac{384 \cdot 10^5 s}{(s + j40000)(s + 32000 - j24000)(s + 32000 + j24000)} \Big|_{s=j40000}$$

$$= 7.5 \cdot 10^{-3} \angle -90^\circ$$

$$\rightarrow C_2 = \frac{384 \cdot 10^5 s}{(s - j40000)(s + j40000)(s + 32000 + j24000)} \Big|_{s=-32000 + j24000}$$

$$= 12.5 \cdot 10^{-3} \angle 90^\circ$$

$$\rightarrow i_L(t) = [15 \cos(40000t - 90^\circ) + 25e^{-32000t} \cos(24000t + 90^\circ)]u(t) \text{ mA}$$


$$= [15 \sin 40000t - 25e^{-32000t} \sin 24000t]u(t) \text{ mA}$$

- Thus, the steady-state current is


$$i_{Lss} = 15 \sin 40000t \text{ mA} \quad (i_{Lss} = \lim_{t \rightarrow \infty} i_L(t))$$
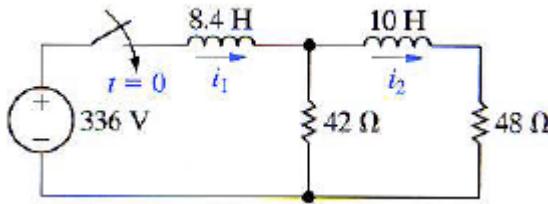
### The step response of a multiple mesh circuit

- Let us consider the following circuit example



$\downarrow \mathcal{L}$

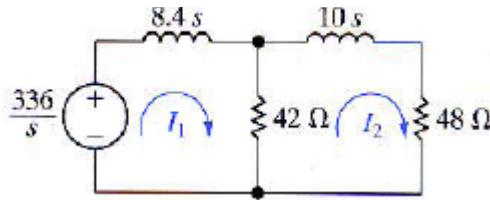

$$\frac{336}{s} = 8.4sI_1 + 42(I_1 - I_2) \Rightarrow (8.4s + 42)I_1 - 42I_2 = \frac{336}{s}$$

$$42(I_2 - I_1) + 10sI_2 + 48I_2 = 0 \Rightarrow -42I_1 + (10s + 90)I_2 = 0$$

Hence ;

$$I_1 = \frac{10s + 90}{42} I_2 \quad \Rightarrow \quad \left[ \frac{(8.4s + 42)(10s + 90)}{42} - 42 \right] I_2 = \frac{336}{s}$$

$$I_2 = \frac{168}{s(s + 2)(s + 12)} \quad , \quad I_1 = \frac{40(s + 9)}{s(s + 9)(s + 12)}$$


- Using partial-fraction expansion gives

$$I_1 = \frac{15}{s} - \frac{14}{s + 2} - \frac{1}{s + 12} \quad , \quad I_2 = \frac{7}{s} - \frac{8.4}{s + 2} + \frac{1.4}{s + 12}$$


→  $i_1(t) = (15 - 14e^{-2t} - e^{-12t})u(t)A \quad , \quad i_2 = (7 - 8.4e^{-2t} + 1.4e^{-12t})u(t)A$
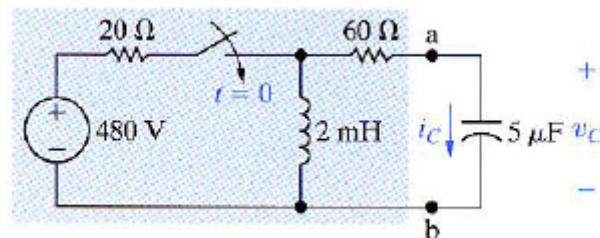
### The use of Thevenin's equivalent

- We now consider how to use Thevenin's equivalent in the s-domain for the circuit shown as



- with the s-domain equivalent circuit

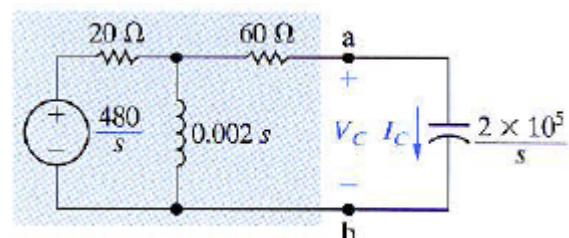

- the Thevenin voltage is the open-circuit voltage across terminals a,b.

$$V_{Th} = \frac{\left(\frac{480}{s}\right) 0.002s}{20 + 0.002s} = \frac{480}{s + 10^4}$$

- and the Thevenin impedance is calculated as

$$Z_{Th} = 60 + \frac{20.0.002s}{20 + 0.002s} = \frac{80(s + 7500)}{s + 10^4}$$

Hence ;

$$\begin{aligned} I_C &= \frac{V_{Th}}{Z_{Th} + \frac{2.10^5}{s}} = \frac{\frac{480}{s} + 10^4}{\left[ \frac{80(s + 7500)}{s + 10^4} \right] + \frac{2.10^5}{s}} \\ &= \frac{6s}{s^2 + 10000s + 25.10^6} = \frac{6s}{(s + 5000)^2} \\ &= -\frac{30000}{(s + 5000)^2} + \frac{6}{s + 5000} \end{aligned}$$

→  $i_C(t) = (-30000te^{-5000t} + 6e^{-5000t})u(t)A$

Note that ;

$$i_C(0) = \lim_{t \rightarrow 0} i(t) = 6 A$$

- which can also be found from the circuit as

$$i_C(0) = \frac{480}{20 + 60} = 6 A$$

- and in a similar manner, we also obtain

$$V_C(t) = 2.10^5 \int_{0^-}^t (6 - 30000\tau)e^{-5000\tau} d\tau$$

OR

$$V_C = \frac{6s}{(s + 5000)^2} \frac{2.10^5}{s} = \frac{12.10^5}{(s + 5000)^2}$$

→  $V_C(t) = \mathcal{L}^{-1}\{V_C\}$

$$= 12.10^5 e^{-5000t} u(t) V$$

## The transfer function

- Defined as the s-domain ratio of the Laplace transform of the output (response)

↳ to the Laplace transform of the input (source)

- To compute transfer function of a circuit

↳ we assume ZERO initial conditions


$$H(s) = \frac{Y(s)}{X(s)}$$

where

$Y(s)$  : LT of output signal  $\longrightarrow$  depends on how it is defined

$X(s)$  : LT of input signal

e.g. Consider

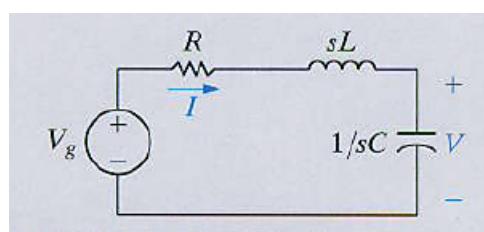

$$\begin{aligned} H(s) &= \frac{I}{V_g} = \frac{1}{R + sL + \frac{1}{sC}} \\ &= \frac{sC}{s^2LC + sRC + 1} \end{aligned}$$

- If the voltage across the capacitor is defined as the output signal, then

$$H(s) = \frac{V}{V_g} = \frac{1/sC}{R + sL + \frac{1}{sC}} = \frac{1}{s^2LC + sRC + 1}$$

Note that ;

- For linear lumped-parameter circuits,  $H(s)$  is always a rational function of  $s$
- The poles of  $H(s)$  must always lie in the LHP of  $s$

↳ if the response to a bounded source is to be bounded.

## The transfer function in partial fraction expansions

- We shall write the circuit output as the product of the transfer function and the driving function

$$Y(s) = H(s)X(s)$$

- Expanding the right-hand side into a sum of partial fractions

 produces a term for each pole of  $H(s)$  and  $X(s)$

- The terms generated by the poles of  $H(s)$

 give rise to the transient component of the total response

- And the terms generated by the poles  $X(s)$

 lead to the steady-state component of the response.

### **The transfer function and the steady-state sinusoidal response**

- Once we have computed a circuit's transfer function

 we NO LONGER need a separate phasor analysis to determine the steady-state response.

- We use transfer function to relate the steady-state response

 to the excitation source.

- Assume that

$$\begin{aligned} x(t) &= A \cos(\omega t + \phi) \\ &= A \cos \omega t \cos \phi - A \sin \omega t \sin \phi \end{aligned}$$

$$\Rightarrow \mathcal{L}\{x(t)\} \triangleq X(s) = \frac{(A \cos \phi)s}{s^2 + \omega^2} - \frac{(A \sin \phi)\omega}{s^2 + \omega^2}$$

$$= \frac{A(s \cos \phi - \omega \sin \phi)}{s^2 + \omega^2}$$

$$\begin{aligned} \Rightarrow Y(s) &= H(s)X(s) = H(s) \frac{A(s \cos \phi - \omega \sin \phi)}{s^2 + \omega^2} \\ &= \frac{c_1}{s - j\omega} + \frac{c_1^*}{s + j\omega} + \sum \text{Terms generated by the poles of } H(s) \end{aligned}$$

$$\Rightarrow c_1 = \frac{H(s)A(s \cos \phi - \omega \sin \phi)}{s + j\omega} \Big|_{s=j\omega}$$

$$= \frac{H(j\omega)A(j\omega \cos \phi - \omega \sin \phi)}{j2\omega}$$

$$= \frac{H(j\omega)A(\cos \phi + j \sin \phi)}{2} = \frac{1}{2} H(j\omega) A e^{j\phi}$$

Hence ;

$$c_1 = \frac{A}{2} |H(j\omega)| e^{j[\theta(\omega) + \phi]}$$


where

$$H(j\omega) = |H(j\omega)| e^{j\theta(\omega)}$$

- and we obtain

$$y_{ss}(t) = A |H(j\omega)| \cos[\omega t + \theta(\omega) + \phi]$$

**e.g.** Consider the following circuit

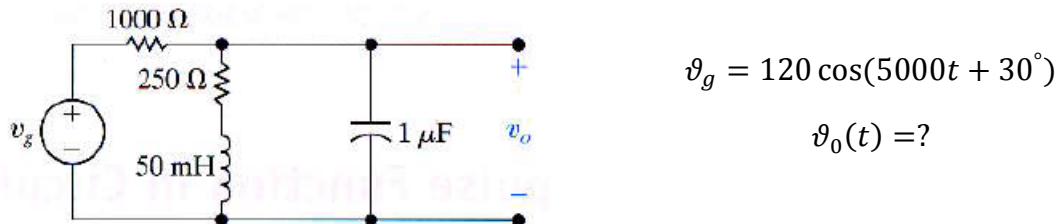

**Solution.**

$$(250 + 0.05s) // \frac{10^6}{s} \Rightarrow \frac{\frac{(250 + 0.05s)10^6}{s}}{250 + 0.05s + \frac{10^6}{s}} = \frac{25 \cdot 10^7 + 5 \cdot 10^4 s}{0.05s^2 + 250s + 10^6}$$

$$\frac{V_0(s)}{V_g(s)} = \frac{\frac{25.10^7 + 5.10^4 s}{0.05s^2 + 250s + 10^6}}{\frac{25.10^7 + 5.10^4 s}{0.05s^2 + 250s + 10^6} + 1000} = \frac{25.10^7 + 5.10^4 s}{50s^2 + 30.10^4 s + 125.10^7}$$

$$= \frac{5.10^6 + 10^3 s}{s^2 + 6.10^3 s + 25.10^6} = \frac{1000(s + 5000)}{s^2 + 6000s + 25.10^6} = H(s)$$

• and

$$H(j5000) = \frac{1000(j5000 + 5000)}{-25.20^6 + j30.10^6 + 25.10^6} = \frac{10^6(j+1)5}{j30.10^6} = \frac{1-j}{6} = \frac{\sqrt{2}}{6} \angle -45^\circ$$

$$\Rightarrow V_0(t) = 120 \frac{\sqrt{2}}{6} \cos(5000t + 30^\circ - 45^\circ) = 20\sqrt{2} \cos(5000t - 15^\circ) \text{ V}$$