

Name: Tugberk GÖÇÜ  
Std. Id: 115200084


19.04.2020

### Homework 1

- The following ring distributor is fed from point A with a 230 V supply. The resistances are given for go and return conductors.
  - Determine the voltage at each load point.
  - If the points A and D are linked through an inter-connector of resistance  $0.05 \Omega$ , determine the new voltage at each load point.


P.S. Do not multiply the resistances by 2, you can use the values directly. Row# indicates your row number in the class list which is given in Appendix.

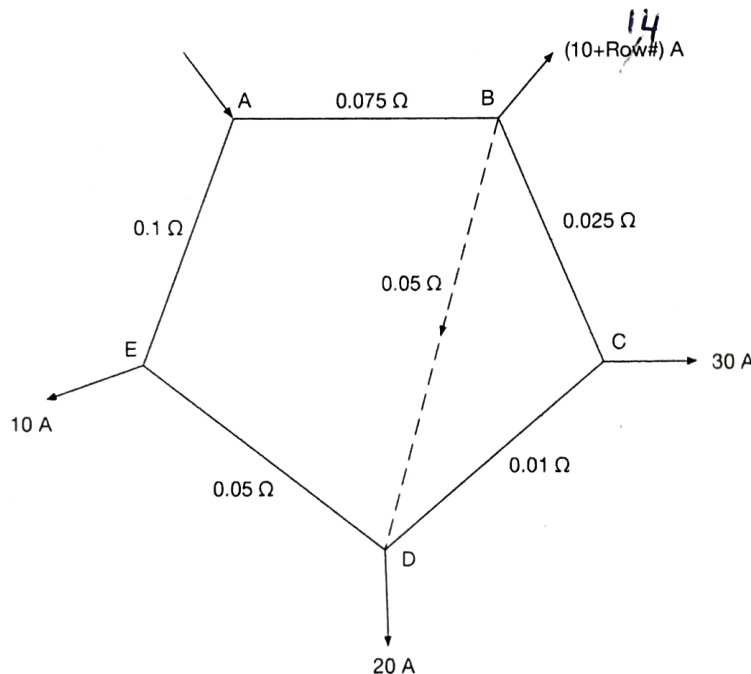Hint You can apply the Thevenin's Theorem for solving b)




- A single phase distributor is shown below. At the far end, the voltage  $V_B = (230 + \text{Row\#})$  V and the current is 100 A at a p.f. of 0.8 leading. Notice that phase angle  $\phi_2$  is between  $V_M$  and  $I_1$ .
  - Find the current at point M,  $I_1$ , and power factor,  $\cos(\phi_2)$  by specifying the lagging or leading.
  - Draw the phasor diagram

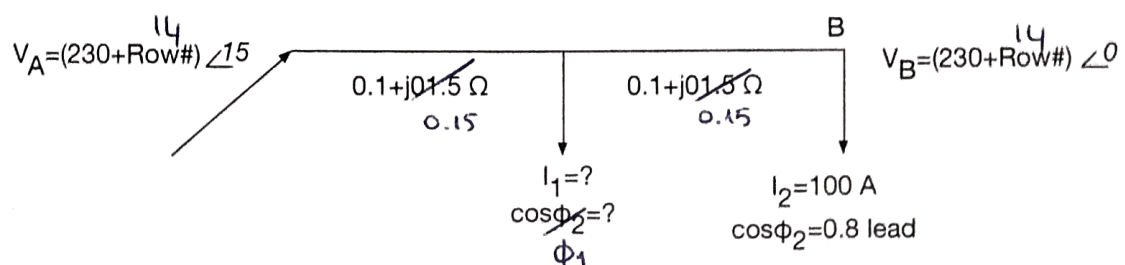P.S. Here, Row# indicates again your row number in the class list which is given in Appendix.



1)

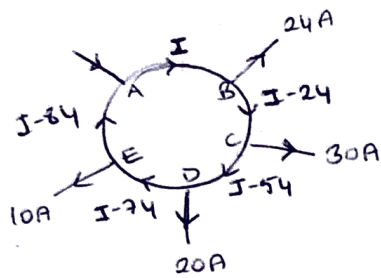

$$R_{AB} = 0.075 \Omega$$

$$R_{BC} = 0.025 \Omega$$

$$R_{CD} = 0.01 \Omega$$

$$R_{DE} = 0.05 \Omega$$

$$R_{EA} = 0.1 \Omega$$

a) Kirchhoff's voltage law:


$$I_{AB} \cdot R_{AB} + I_{BC} \cdot R_{BC} + I_{CD} \cdot R_{CD} + I_{DE} \cdot R_{DE} + I_{EA} \cdot R_{EA} = 0$$

$$0.075 \cdot I + 0.025 \cdot (I - 24) + (0.01) \cdot (I - 54) + 0.05 \cdot (I - 74) + 0.1 \cdot (I - 84) = 0$$

$$I(0.075 + 0.025 + 0.01 + 0.05 + 0.1) + (-0.6) + (-0.54) + (-3.7) + (-8.4) = 0$$

$$0.26 I = 13.24$$

$$I \approx 50.92$$

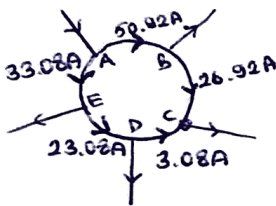

$$I_{AB} = 50.92 \text{ A}$$

$$I_{BC} = 26.92 \text{ A}$$

$$I_{CD} = 3.08 \text{ A}$$

$$I_{DE} = 23.08 \text{ A}$$

$$I_{EA} = 33.08 \text{ A}$$

Point C is the minimum voltage potential point.

$$V_A = 230 \text{ V}$$

$$V_A = V_B + I_{AB} \cdot R_{AB}$$

$$230 = V_B + (50.92) \cdot (0.075)$$

$$V_B = 230 - 3.819$$

$$= 226.18 \text{ V}$$

$$V_C = V_B - I_{BC} \cdot R_{BC}$$

$$= 226.18 - (26.92) \cdot (0.025)$$

$$= 225.507 \text{ V}$$

$$V_D = V_C + I_{CD} \cdot R_{CD}$$

$$= 225.507 + (3.08) \cdot (0.01)$$

$$= 225.5378 \text{ V}$$

$$V_E = V_D + I_{DE} \cdot R_{DE}$$

$$= 225.5378 + (23.08) \cdot (0.05)$$

$$= 226.6918 \text{ V}$$

$$V_A = V_E + I_{EA} \cdot R_{EA}$$

$$= 226.6918 + 33.08 \cdot (0.1)$$

$$= 230 \text{ V}$$

Answers for a)

$$V_A = 230 \text{ Volt}$$

$$V_B = 226.18 \text{ Volt}$$

$$V_C = 225.507 \text{ Volt}$$

$$V_D = 225.5378 \text{ Volt}$$

$$V_E = 226.6918 \text{ Volt}$$

b) Voltage Drop Along BCD =  $(26.92) \times (0.025) + (-3.08) \times (0.01)$   
 $= 0.673 + (-0.0308)$   
 $= 0.6422 \text{ V}$

This is equal to Thevenin's open circuited voltage  $E_0$ ;


$$E_0 = 0.6422 \text{ V}$$

$$R_0 = \frac{\overbrace{(0.075 + 0.1 + 0.05)}^{0.225} \cdot \overbrace{(0.025 + 0.01)}^{0.035}}{(0.075 + 0.1 + 0.05) + (0.025 + 0.01)}$$

$$= 0.03 \Omega$$

Current in inter-connector,  $I_{BD} = \frac{E_0}{R_0 + R_{BD}} = \frac{0.6422}{0.03 + 0.05} = 8.0275$

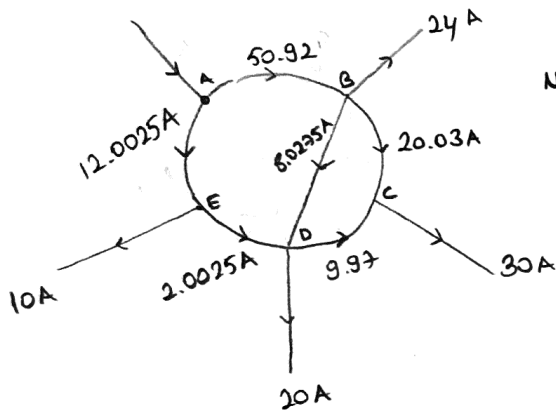Voltage Drop in inter-connector,  $V_{BD} = I_{BD} \cdot R_{BD} = 8.0275 \times 0.05$   
 $= 0.401375 \text{ V}$



New Current in  $I_{BC}$ ;

$$I_{BC} \cdot (0.025) + (I_{BD} - I_{BD}) \cdot 0.01 - (0.05 \times 8.0275) = 0$$

$$I_{BC} \cdot (0.035) - 0.3 - 0.401375 = 0$$

$$I_{BC} = 20.03 \text{ A}$$

$$V_A = 230 \text{ V}$$

$$V_B = V_A - V_{AB} = 230 - (50.92 \times 0.025)$$

$$= 226.181 \text{ V}$$

$$V_C = V_B - V_{BC} = 226.181 - (20.03 \times 0.025)$$

$$= 225.68 \text{ V}$$


$$V_D = V_C + V_{CD} = 225.68 + (9.97 \times 0.1)$$

$$= 226.667 \text{ V}$$

$$V_E = V_D + V_{DE} = 226.667 + (2.0025 \times 0.05)$$

$$= 226.767 \text{ V}$$

2)

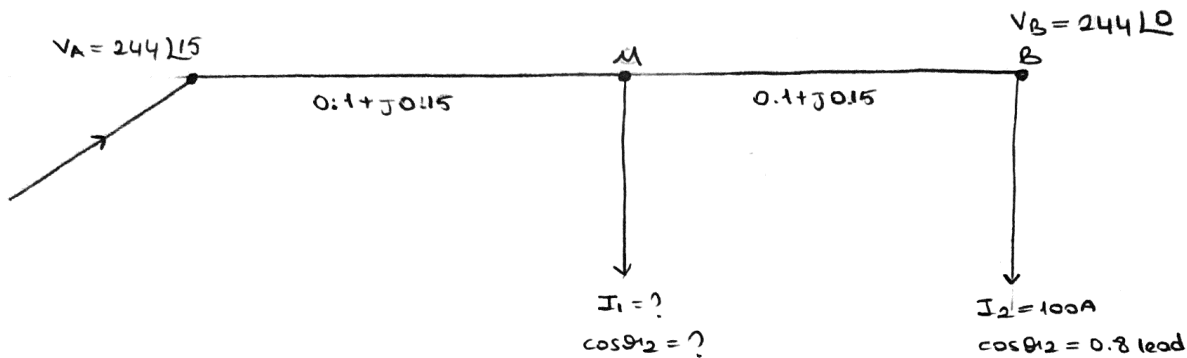

a) Total impedance of distributors =  $(0.1 + j0.15) + (0.1 + j0.15) = 0.2 + j0.3 \Omega$

Impedance of section AM,  $\bar{Z}_{AM} = 0.1 + j0.15 \Omega$

" " " MB,  $\bar{Z}_{MB} = 0.1 + j0.15 \Omega$

$$\bar{V}_A = 244 \angle 15^\circ \text{ V} = 235.7 + j63.2 \text{ V}$$

$$\bar{V}_B = 244 \angle 0^\circ \text{ V} = 244 + j0 \text{ V}$$

$$\text{Load current at point B, } \bar{I}_2 = 100 (0.8 + j0.6) = 100 \angle 36.87^\circ$$

$\cos \phi_2 \quad \sin \phi_2$

$$\text{Current in section MB, } \bar{I}_{MB} = \bar{I}_2 = 80 + j60 \text{ A}$$

$$\text{Drop in section MB, } \bar{V}_{MB} = \bar{I}_{MB} \cdot \bar{Z}_{MB} = (80 + j60) \times (0.1 + j0.15) = -1 + j18 \text{ V}$$

$$\begin{aligned} \text{Voltage at point M, } \bar{V}_M &= \bar{V}_B + \bar{V}_{MB} = (244 + j0) + (-1 + j18) \\ &= 243 + j18 \text{ V} \\ &= 243.7 \angle 4.236^\circ \end{aligned}$$

$$\text{Voltage at point A, } \bar{V}_A = \bar{V}_M + (0.1 + j0.15) \cdot \bar{I}_1$$

$$\text{Current in section AM, } \bar{I}_{AM} = \bar{I}_1 = \frac{\bar{V}_A - \bar{V}_M}{(0.1 + j0.15)} = \frac{(235.7 + j63.2) - (243 + j18)}{0.1 + j0.15}$$

$$\approx 186.15 + j132.77$$

$$\bar{I}_1 \approx 253.97 \angle 42.86^\circ \text{ positive}$$

$$\begin{aligned} \cos \phi_1 &= \cos (4.236 - 42.86) \\ &= 0.981 \text{ leading} \end{aligned}$$

Thus,  $\cos \phi_1 = 0.981$  leading  
 $\bar{I}_1 = 253.97 \angle 42.86^\circ$

b) Phasor Diagram:

