

Programmable Logic Devices (PLD)

- Programmable logic devices are AND-OR logic circuits

↳ which can be programmed by the user

- we consider three main types of PLDs:

1. Read Only Memory (ROM)
2. Programmable Logic Array (PLA)
3. Programmable Array Logic (PAL)

Read Only Memory (ROM)


- there exist various types of ROMs such as

PROM (Programmable ROM)

EPROM (Electrically PROM)

EEPROM (Electrically Erasable PROM)

 
- the general structure is given as follows




- the ROM circuit is a combinational circuit

↳ that implements m Boolean functions of n variables in sum of minterms form

 -the circuit is composed of an n -input decoder and m OR gates



-and equivalently represented as follows

 

Note that ;

- if the input sequence is $(x_1 \dots x_n)$, then the binary information of m bits, namely, $(f_1 \dots f_m)$ is stored at address $(x_1 \dots x_n)$

↳ justifying why it is referred as "Read Only Memory"


However;

- keep in mind that this is a combinational logic circuit.

↳ thus every combinational logic circuit can be interpreted as a ROM circuit

Programmable Logic Array (PLA)

- the general structure can be given by

 

- a typical PLA circuit involves 16 inputs, 48 AND gates, and 8 outputs

Note that;

- a PROM with 16 inputs has 2^{16} AND gates

↳ while PLA has only 48 AND gates

Hence;


- a PROM with 16 inputs and 8 outputs is capable of storing 2^{16} times 8 bits of binary information

- so does a PLA of the same size

↳ but with significantly less number of AND gates.

Programmable Array Logic (PAL)

- the general structure can be shown as

 

- since only the AND gates are programmable
↳ it is not as flexible as PLA

Note that;

- ROM, PLA and PAL devices can be mask programmable or field programmable

mask programming

- the customer provides a program table to the manufacturer

↳ which is used by the vendor to produce a custom-made PLD that has the internal logic specified by the customer

field programming

- it uses a field-programmable logic array

↳ which can be programmed by the user with a commercial hardware programming unit

Boolean functions and PLDs

- multiple number of Boolean functions can be implemented using ROM, PLA, or PAL
- simply because PLDs generate either entire minterms or several product terms

(\hookrightarrow) which are ORed and obtained as outputs

- we need to handle each PLD in a different way

Namely,

ROM: All minterms are available. ^{in form} Obtain the sum of minterms for each Boolean function.

PLA: AND terms are in limited number. Minimize the Boolean functions such that common product terms are obtained

PAL: Minimize the Boolean functions individually such that each function is implemented with at most a certain number of AND gates

example. Consider the following Boolean functions


$$f_1(x_1, x_2, x_3) = \sum m(1, 2, 3, 5)$$

$$f_2(x_1, x_2, x_3) = \sum m(1, 3, 6, 7)$$

$$f_3(x_1, x_2, x_3) = \sum m(0, 1, 6, 7)$$

Implement f_1, f_2, f_3 using an appropriate size ROM.

- we need to employ an 8×3 ROM

 

- we find that at the following addresses,

x_1	x_2	x_3	f_1	f_2	f_3
0	1	1	1	1	0

1	0	1	1	0	0
---	---	---	---	---	---

1	1	0	0	1	1
---	---	---	---	---	---

addresses information stored

the corresponding 3 bits of data are stored

example. Consider the following Boolean functions

$$f_1(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 6, 7, 8, 9, 12, 14, 15)$$

$$f_2(x_1, x_2, x_3, x_4) = \sum m(2, 3, 5, 11, 12, 13)$$

- we minimize both $\{f_1, f_1'\}$ and $\{f_2, f_2'\}$

$x_1x_2 \backslash x_3x_4$	00	01	11	10
00	1	1	0	1
01	0	0	1	1
11	1	0	1	1
10	1	1	0	0

$x_1x_2 \backslash x_3x_4$	00	01	11	10
00	0	0	1	1
01	0	1	0	0
11	1	1	0	0
10	0	0	1	0

$$f_1 = x_2x_3 + x_2'x_3' + x_1'x_3x_4' + x_1x_3'x_4'$$

$$f_2 = x_1'x_2'x_3 + x_2'x_3x_4 + x_1x_2x_3' + x_2x_3'x_4$$

$$f_1' = x_1'x_2x_3' + x_2x_3'x_4 + x_2'x_3x_4 + x_1x_2'x_3$$

$$f_2' = x_2'x_3' + x_2x_3 + x_1'x_2x_4' + x_1x_2'x_4'$$

- we can see that f_1 and f_2' have the greatest number of common terms

- the PLA implementation table is given by

Product terms	x_1	x_2	x_3	x_4	f_1	f_2'
1	-	1	1	-	1	1
2	-	0	0	-	1	1
3	0	-	1	0	1	-
4	1	-	0	0	1	-
5	0	1	-	0	-	1
6	1	0	-	0	-	1

-then the PLA has 4 inputs, 6 AND gates, and 2 outputs

