

EEEN 222 Digital System Design
Homework 03Due : 14-May-2016
Monday 17:00

Problem 1) Implement a full adder using a 3-to-8 line decoder and external gates if necessary.

Problem 2) Draw a PLA circuit to implement the functions

$$F_1(A, B, C) = (AC + AB + BC)'$$

$$F_2(A, B, C) = A'B + AC + A'BC'$$

Problem 3) The following is a truth table of a three-input, four output combinational circuit;

<i>x</i>	<i>y</i>	<i>z</i>	A	B	C	D
0	0	0	0	1	1	0
0	0	1	0	1	1	1
0	1	0	1	0	0	1
0	1	1	0	0	0	1
1	0	0	1	1	1	0
1	0	1	0	1	0	1
1	1	0	1	0	1	1
1	1	1	0	1	1	0

Tabulate PAL programming for the circuit and mark the fuse map.

Problem 4) A sequential circuit with two D flip-flops *A* and *B*, two inputs, *x* and *y*; and one output *z* is specified by the following next-state and output equations

$$A(t + 1) = xy' + xB$$

$$B(t + 1) = xA + xB'$$

$$z = A$$

- Draw the logic diagram of the circuit.
- List the state table for the sequential circuit.
- Draw the corresponding state diagram.

Problem 5) Design a sequential circuit that counts even numbers including 0, from 0 to 14. (Eg. 0,2,4,6,8,10,12,14,0,2,4...). Use JK flip flops.

- List the state table for the sequential circuit.
- Draw the corresponding state diagram.
- Draw the logic diagram of the circuit.