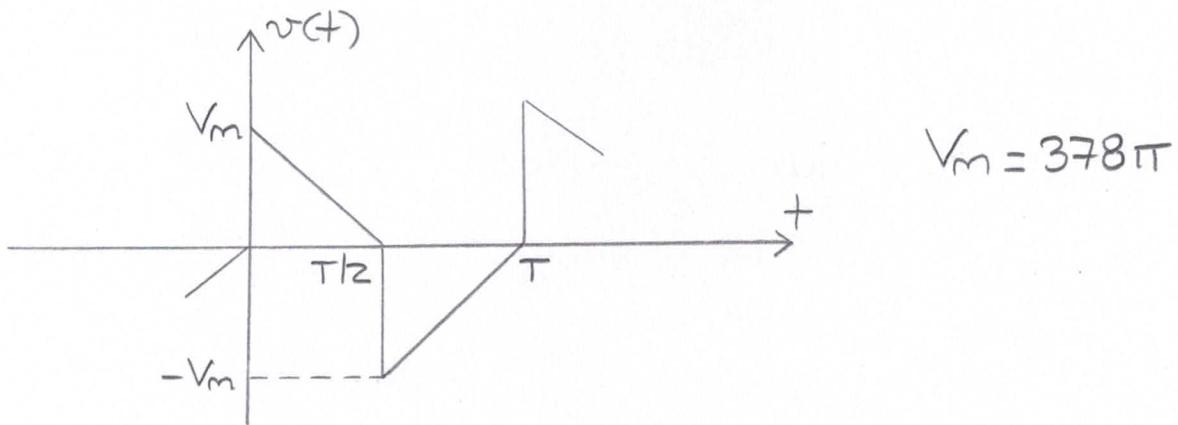


## Selected Problems - VIII

**Problem 1)** Consider the following periodic function shown as



- a. Derive the Fourier series in trigonometric form.
- b. Use the first five terms to estimate  $v(T/8)$ .

**Solution.**

- we shall express  $v(t)$  in closed form as

$$v(t) = \begin{cases} -\frac{2V_m}{T}t + V_m, & 0 \leq t < \frac{T}{2} \\ \frac{2V_m}{T}t - 2V_m, & \frac{T}{2} \leq t < T \end{cases}$$

- and the trigonometric Fourier series representation is given by

$$v(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

where

$$a_n - j b_n = \sqrt{a_n^2 + b_n^2} \angle -\theta_n = A_n \angle -\theta_n$$

- we calculate  $a_v$  as follows

$$\begin{aligned} a_v &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{T} \left[ \int_0^{T/2} \left( -\frac{2V_m}{T}t + V_m \right) dt + \int_{T/2}^T \left( \frac{2V_m}{T}t - 2V_m \right) dt \right] \\ &= \frac{1}{T} \left[ \left( -\frac{V_m}{T}t^2 + V_m t \right) \Big|_0^{T/2} + \left( \frac{V_m}{T}t^2 - 2V_m t \right) \Big|_{T/2}^T \right] \end{aligned}$$

$$\begin{aligned}
 &= \frac{1}{T} \left[ \left( -\frac{V_m}{T} \right) \frac{\pi}{4} + V_m \frac{\pi}{2} - 0 + \frac{V_m}{T} \pi^2 - 2V_m T - \frac{V_m}{T} \frac{\pi}{4} + 2V_m \frac{\pi}{2} \right] \\
 &= -\cancel{\frac{V_m}{4}} + \cancel{\frac{V_m}{2}} + \cancel{V_m} - \cancel{2V_m} - \cancel{\frac{V_m}{4}} + \cancel{V_m} \\
 &= 0
 \end{aligned}$$

Note that;

- we shall observe that  $v(t)$  has half-wave symmetry

Hence;

$$a_0 = 0 \quad (\text{due to half-wave symmetry})$$

$$a_n = 0, b_n = 0 \quad \text{for even } n$$

$$a_n = \frac{4}{T} \int_0^{T/2} v(t) \cos n\omega_0 t \, dt \quad \text{for odd } n$$

$$b_n = \frac{4}{T} \int_0^{T/2} v(t) \sin n\omega_0 t \, dt \quad \text{for odd } n$$

- we calculate

$$\begin{aligned}
 a_n &= \frac{4}{T} \int_0^{T/2} \left( -\frac{2V_m}{T} + V_m \right) \cos n\omega_0 t \, dt \\
 &= -\frac{8V_m}{T^2} \int_0^{T/2} \underbrace{+ \cos n\omega_0 t}_{dv} \, dt + \frac{4V_m}{T} \int_0^{T/2} \cos n\omega_0 t \, dt \\
 &\quad \text{integration by parts} \\
 &= -\frac{8V_m}{T^2} \left[ + \frac{\sin n\omega_0 t}{n\omega_0} \Big|_0^{T/2} - \int_0^{T/2} \frac{\sin n\omega_0 t}{n\omega_0} \, dt \right] \\
 &\quad + \frac{4V_m}{T} \left. \frac{\sin n\omega_0 t}{n\omega_0} \right|_0^{T/2}
 \end{aligned}$$

$$= -\frac{8V_m}{T^2} \left[ \frac{\pi}{2} \frac{1}{n\omega_0} \sin(n\omega_0 \frac{\pi}{2}) + \frac{\cos n\omega_0 \pi}{(n\omega_0)^2} \right]_0^T$$

$$+ \frac{4V_m}{T} \frac{1}{n\omega_0} \sin(n\omega_0 \frac{\pi}{2})$$

$$= -\frac{2V_m}{n\pi} \sin(n\pi) + \frac{8V_m}{(n\omega_0)^2} \left( \frac{1}{\pi} \cos n\pi - 1 \right)$$

$$+ \frac{2V_m}{n\pi} \sin(n\pi), \quad n \text{ is odd}$$

$$= \frac{16V_m}{n^2 \pi^2}$$

$$= \frac{4V_m}{\pi^2 n^2}, \quad n \text{ is odd}$$

Similarly;

$$b_n = \frac{4}{T} \int_0^{T/2} \left( -\frac{2V_m}{T} + V_m \right) \sin n\omega_0 t dt$$

$$= -\frac{8V_m}{T^2} \int_0^{T/2} \underbrace{t \sin n\omega_0 t dt}_u + \frac{4V_m}{T} \int_0^{T/2} \sin n\omega_0 t dt$$

integration by parts

$$= -\frac{8V_m}{T^2} \left[ -t \frac{\cos n\omega_0 t}{n\omega_0} \Big|_0^{T/2} - \int_0^{T/2} -\frac{\cos n\omega_0 t}{n\omega_0} dt \right]$$

$$- \frac{4V_m}{T} \frac{\cos n\omega_0 t}{n\omega_0} \Big|_0^{T/2}$$

$$= \frac{8V_m}{T^2} \left[ \frac{\pi}{2} \frac{1}{n\omega_0} \cos n\pi - \frac{\sin n\omega_0 t}{(n\omega_0)^2} \Big|_0^{T/2} \right]$$

$$- \frac{4V_m}{n\omega_0 T} (\cos n\pi - 0), \quad n \text{ is odd}$$

$$= -\frac{2V_m}{\pi n} + 0 - 0 + \frac{4V_m}{\pi n}$$

$$= \frac{2V_m}{\pi n}, n \text{ is odd}$$

As a result;

$$A_n \angle -\theta_n = a_n - j b_n$$

$$= \frac{4V_m}{\pi^2 n^2} - j \frac{2V_m}{\pi n}, n \text{ is odd}$$

$$= \frac{2V_m}{\pi n} \left( \frac{2}{\pi n} - j \right)$$

$$= \frac{2 \cdot 378}{\pi n} \left( \frac{2}{\pi n} - j \right)$$

$$= \frac{756}{n} \left( \frac{2}{\pi n} - j \right)$$

Therefore;

$$v(t) = \sum_{n=1,3,5}^{\infty} A_n \cos(n\omega_0 t - \theta_n)$$

b.

$$A_1 = 756 (0.6366 - j) = 896.1980 \angle -57.5184^\circ$$

$$A_3 = 252 (0.2122 - j) = 257.6112 \angle -78.0195^\circ$$

$$A_5 = 151.2 (0.1273 - j) = 152.4207 \angle -82.7439^\circ$$

$$A_7 = 108 (0.0909 - j) = 108.4457 \angle -84.8035^\circ$$

$$A_9 = 84 (0.0707 - j) = 84.2097 \angle -85.9555^\circ$$

$$v(\tau/8) = 896.1980 \cos(\omega_0 \tau/8 - 57.5184^\circ)$$

$$+ 257.6112 \cos(3\omega_0 \tau/8 - 78.0195^\circ)$$

$$+ 152.4207 \cos(5\omega_0 \tau/8 - 82.7439^\circ)$$

$$+ 108.4457 \cos(7\omega_0 T/8 - 84.8035)$$

$$+ 84.2097 \cos(9\omega_0 T/8 - 85.9559)$$

$$= 896.1380 \cos(45 - 57.5184) + 257.6112 \cos(135 - 78.0195)$$

$$+ 152.4207 \cos(225 - 82.7439) + 108.4457 \cos(315 - 84.8035)$$

$$+ 84.2097 \cos(405 - 85.9559)$$

$$= 888.92 \checkmark$$

- We also calculate from the defining equation  
of  $v(t)$

$$v(T/8) = - \frac{2Vm}{T} \frac{T}{8} + Vm$$

$$= \frac{3}{4} Vm$$

$$= \frac{3}{4} 378 \pi$$


$$= 850.64 \checkmark$$

Hence ;


$$\frac{888.92}{850.64} \times 100 = 99.7957 \% \text{ of } v(t) \text{ is obtained}$$

by the first five terms.

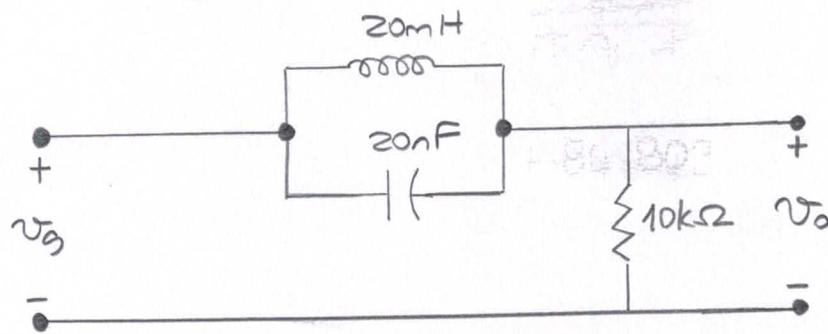Problem 2) Consider the following circuit



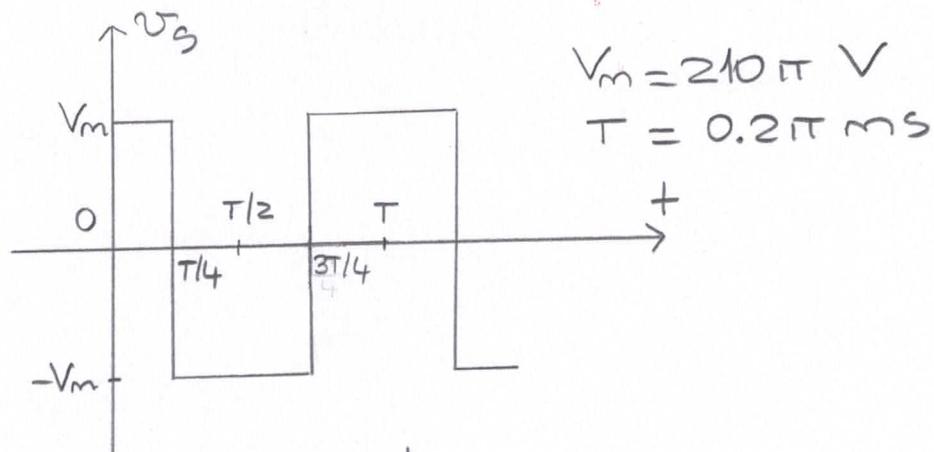The periodic square-wave voltage shown as



is applied to the above circuit.

- a. Derive the first nonzero terms in the Fourier series that represents the steady-state voltage,  $v_o$ .
- b. Which frequency component in the input voltage is eliminated from the output voltage?

**Solution.** Note that  $v_s$  does not have any symmetry, then

$$a_0 = \frac{1}{T} \int_0^T v_s(t) dt$$

and  $a_n = 0$ ,  $b_n = 0$  for even  $n$

$$a_n = \frac{2}{T} \int_0^{T/2} v_s(t) \cos n\omega_0 t dt, \text{ for odd } n$$

$$b_n = \frac{2}{T} \int_0^{T/2} v_s(t) \sin n\omega_0 t dt, \text{ for odd } n$$

-we calculate

$$\begin{aligned}
 a_0 &= \frac{1}{T} \left[ \left( \int_0^{T/4} V_m dt + \int_{T/4}^{3T/4} -V_m dt + \int_{3T/4}^T V_m dt \right) \right] \\
 &= \frac{V_m}{T} \left( + \int_0^{T/4} - + \int_{T/4}^{3T/4} + + \int_{3T/4}^T \right) \\
 &= \frac{V_m}{T} \left( \frac{T}{4} - 0 - 3 \frac{T}{4} + \frac{T}{4} + T - 3 \frac{T}{4} \right) \\
 &= 0
 \end{aligned}$$

and

$$\begin{aligned}
 a_n &= \frac{2}{T} \left[ \int_0^{T/4} V_m \cos n\omega_0 t dt + \int_{T/4}^{3T/4} -V_m \cos n\omega_0 t dt + \int_{3T/4}^T V_m \cos n\omega_0 t dt \right] \\
 &= \frac{2V_m}{T} \left( \frac{\sin n\omega_0 t}{n\omega_0} \Big|_0^{T/4} - \frac{\sin n\omega_0 t}{n\omega_0} \Big|_{T/4}^{3T/4} + \frac{\sin n\omega_0 t}{n\omega_0} \Big|_{3T/4}^T \right) \\
 &= \frac{2V_m}{n\omega_0 T} \left( \sin \frac{n\pi}{2} - 0 - \sin \frac{3n\pi}{2} + \sin \frac{n\pi}{2} + \sin \cancel{\frac{2\pi}{2}} \right. \\
 &\quad \left. - \sin \frac{3n\pi}{2} \right) \\
 &= \frac{2V_m}{2\pi n} \cancel{2} \left( \sin \frac{n\pi}{2} - \sin \frac{3n\pi}{2} \right) \\
 &= \begin{cases} 0, & \text{for even } n \\ (-1)^{\frac{n-1}{2}} \frac{4V_m}{\pi n}, & \text{for odd } n \end{cases}
 \end{aligned}$$

and

$$\begin{aligned}
 b_n &= \frac{2}{T} \left[ \int_0^{T/4} V_m \sin n\omega_0 t dt + \int_{T/4}^{3T/4} -V_m \cos n\omega_0 t dt + \int_{3T/4}^T V_m \cos n\omega_0 t dt \right] \\
 &= \frac{2V_m}{T} \left( -\frac{\cos n\omega_0 t}{n\omega_0} \Big|_0^{T/4} + \frac{\cos n\omega_0 t}{n\omega_0} \Big|_{T/4}^{3T/4} - \frac{\cos n\omega_0 t}{n\omega_0} \Big|_{3T/4}^T \right) \\
 &= \frac{2V_m}{n\omega_0 T} \left( -\cos \frac{n\pi}{2} + 1 + \cos \frac{3n\pi}{2} - \cos \frac{n\pi}{2} - \cancel{\cos \frac{2\pi}{2}} \right. \\
 &\quad \left. + \cos \frac{3n\pi}{2} \right)
 \end{aligned}$$

$$= \frac{ZV_m}{2\pi n} Z \left( -\cos \frac{n\pi}{2} + \cos \frac{3n\pi}{2} \right)$$

$= 0$  for all  $n$

Therefore :


$$a_1 = (-1)^0 \frac{4 \cdot 210\pi}{\pi \cdot 1} = 840, \quad b_1 = 0 \Rightarrow V_{S1} = 840 + j \cdot 0 \\ = 840 \angle 0^\circ$$

$$a_3 = (-1)^1 \frac{4 \cdot 210\pi}{\pi \cdot 3} = -280, \quad b_3 = 0 \Rightarrow V_{S3} = -280 + j \cdot 0 \\ = 280 \angle 180^\circ$$

$$a_5 = (-1)^2 \frac{4 \cdot 210\pi}{\pi \cdot 5} = 168, \quad b_5 = 0 \Rightarrow V_{S5} = 168 + j \cdot 0 \\ = 168 \angle 0^\circ$$

$$a_7 = (-1)^3 \frac{4 \cdot 210\pi}{\pi \cdot 7} = -120, \quad b_7 = 0 \Rightarrow V_{S7} = -120 + j \cdot 0 \\ = 120 \angle 180^\circ$$

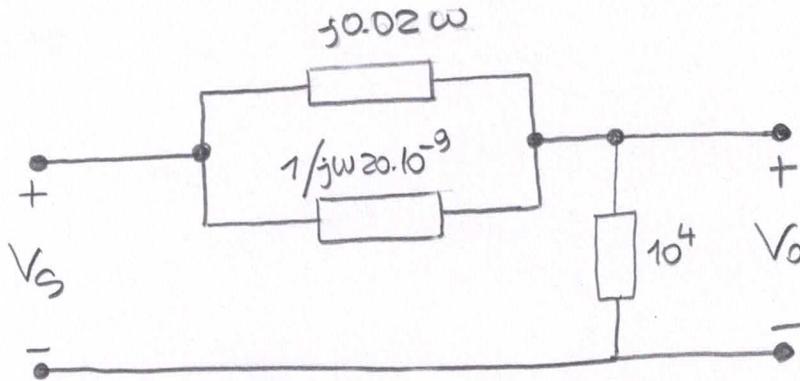It follows from phasor domain approach that we have



$$\frac{j0.02\omega}{j0.02\omega + \frac{1}{j\omega \cdot 2 \cdot 10^{-9}}} : \frac{j0.02\omega (1/j\omega \cdot 2 \cdot 10^{-9})}{j0.02\omega + \frac{1}{j\omega \cdot 2 \cdot 10^{-9}}} = \frac{j0.02\omega}{-4\omega^2 \cdot 10^{-10} + 1}$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{10^4}{10^4 + \frac{j0.02\omega}{-4\omega^2 \cdot 10^{-10} + 1}} = \frac{10^4 (-4\omega^2 \cdot 10^{-10} + 1)}{-4\omega^2 \cdot 10^{-6} + 10^4 + j0.02\omega}$$

$$= \frac{\omega^2 - 25 \cdot 10^8}{\omega^2 - j 5000\omega - 25 \cdot 10^8} \triangleq H(\omega)$$

Hence;

$$\omega_0 = \frac{2\pi}{0.2\pi \cdot 10^{-3}} = 10^4$$

$$H(1 \cdot 10^4) = \frac{10^8 - 25 \cdot 10^8}{10^8 - j 5 \cdot 10^7 - 25 \cdot 10^8} = \frac{-24 \cdot 10^8}{-24 \cdot 10^8 - j \cdot 5 \cdot 10^7} = \frac{240}{240 + j 5}$$

$$= 0.9996 - j 0.0208$$

$$= 0.9998 \angle -1.1935^\circ$$

$$H(3 \cdot 10^4) = \frac{9 \cdot 10^8 - 25 \cdot 10^8}{9 \cdot 10^8 - j 15 \cdot 10^7 - 25 \cdot 10^8} = \frac{-16 \cdot 10^8}{-16 \cdot 10^8 - j 15 \cdot 10^7} = \frac{160}{160 + j 15}$$

$$= 0.9913 - j 0.0929$$

$$= 0.9956 \angle -5.3558^\circ$$

$$H(5 \cdot 10^4) = \frac{25 \cdot 10^8 - 25 \cdot 10^8}{25 \cdot 10^8 - j 25 \cdot 10^7 - 25 \cdot 10^8} = 0$$

$$H(7 \cdot 10^4) = \frac{49 \cdot 10^8 - 25 \cdot 10^8}{49 \cdot 10^8 - j 35 \cdot 10^7 - 25 \cdot 10^8} = \frac{24 \cdot 10^8}{24 \cdot 10^8 - j 35 \cdot 10^7} = \frac{240}{240 - j 35}$$

$$= 0.9792 - j 0.1428$$

$$= 0.9835 \angle -8.2971^\circ$$

As a result;

$$V_{oi} = V_{gi} \cdot H(i \cdot 10^4), \quad i = 1, 3, 5, \dots$$

$$V_{01} = 840 \angle 0^\circ \cdot 0.9958 \angle -1.1935$$

$$= 839.8320 \angle -1.1935$$

$$v_{01}(t) = 839.8320 \cos(10^4 t - 1.1935) \quad \checkmark$$

$$V_{03} = 280 \angle 180^\circ \cdot 0.9956 \angle -5.3558$$

$$= 278.7680 \angle 174.6442$$

$$v_{03}(t) = 278.7680 \cos(3 \cdot 10^4 t + 174.6442) \quad \checkmark$$

$$V_{05} = 168 \angle 0^\circ = 0 \text{ V}, v_{05}(t) = 0 \quad \checkmark$$

$$V_{07} = 120 \angle 180^\circ \cdot 0.9895 \angle -8.2971$$

$$= 118.7400 \angle 171.7029$$

$$v_{07}(t) = 118.74 \cos(7 \cdot 10^4 t + 171.7029) \quad \checkmark$$

$$v_0(t) = 839.8320 \cos(10^4 t - 1.1935) + 278.7680$$

$$+ 278.7680 \cos(3 \cdot 10^4 t + 174.6442)$$

$$+ 0 + 118.74 \cos(7 \cdot 10^4 t + 171.7029) + \dots$$


b. The 5<sup>th</sup> harmonic frequency component in the input voltage is eliminated from the output voltage.

That is;


$$\omega = 5 \cdot 10^4 = 50 \text{ krad/s} \rightarrow \text{rejected}$$

Because, the circuit is a passive bandreject filter with a centre frequency of 50 krad/s

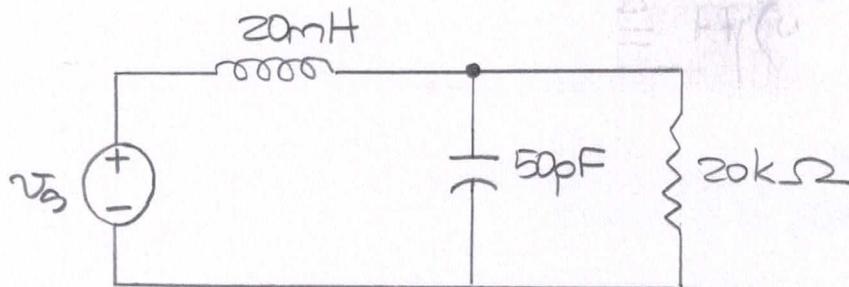**Problem 3)** A triangular-wave voltage source is applied to the circuit shown as



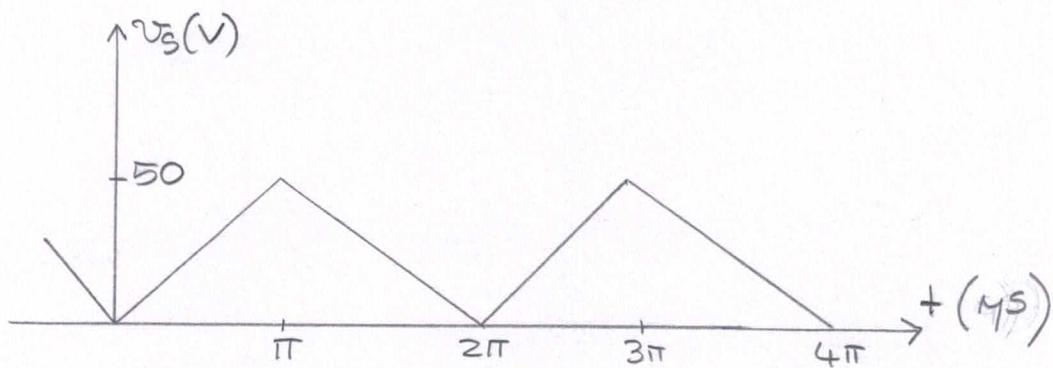The triangular-wave voltage is depicted as follows:



Estimate the average power delivered to the  $20k\Omega$  resistor when the circuit is in steady-state operation.

**Solution.** Note  $v_s$  is an even function which can be defined in one period of interval as follows:

$$v_s = \frac{1}{2\pi} \begin{cases} V_m t, & 0 \leq t < \pi \cdot 10^{-6} \\ V_m(-t + 2\pi \cdot 10^{-6}), & \pi \cdot 10^{-6} \leq t \leq 2\pi \cdot 10^{-6} \end{cases}$$

$$V_m = \frac{50 \cdot 10^6}{\pi}, \quad \omega_0 = \frac{2\pi}{2\pi \cdot 10^{-6}} = 10^6 \text{ rad/s}$$

$$\begin{aligned} a_v &= \frac{V_m}{2\pi} \left[ \int_0^{\pi \cdot 10^{-6}} t dt + \int_{\pi \cdot 10^{-6}}^{2\pi \cdot 10^{-6}} (-t + 2\pi) dt \right] \\ &= \frac{V_m}{2\pi \cdot 10^{-6}} \left( \frac{1}{2} t^2 \Big|_0^{\pi \cdot 10^{-6}} + \frac{1}{2} t^2 \Big|_{\pi \cdot 10^{-6}}^{2\pi \cdot 10^{-6}} + 2\pi t \Big|_{\pi \cdot 10^{-6}}^{2\pi \cdot 10^{-6}} \right) \\ &= \frac{V_m}{2\pi \cdot 10^{-6}} \left( \frac{1}{2} \pi^2 - 0 - \frac{1}{2} 4\pi^2 + \frac{1}{2} \pi^2 + 4\pi^2 - 2\pi^2 \right) 10^{-12} \\ &= \frac{V_m}{2\pi} \pi^2 \cdot 10^{-6} \\ &= 25 \text{ V} \end{aligned}$$

$$a_n = \frac{2}{T} \left[ \int_0^{T/2} V_m + \underbrace{\cos(n\omega_0 t)}_{u} dt + \int_{T/2}^T V_m (-t + 2\pi) \cos(n\omega_0 t) dt \right]$$

-using integration by parts gives

$$\begin{aligned} a_n &= \frac{2V_m}{T} \left( \frac{+ \sin n\omega_0 t}{n\omega_0} \Big|_0^{T/2} - \int_0^{T/2} \frac{\sin n\omega_0 t}{n\omega_0} dt \right. \\ &\quad - \frac{+ \sin n\omega_0 t}{n\omega_0} \Big|_{T/2}^T + \int_{T/2}^T \frac{\sin n\omega_0 t}{n\omega_0} dt \\ &\quad \left. + 2\pi \frac{\sin n\omega_0 t}{n\omega_0} \Big|_{T/2}^T \right) \end{aligned}$$

$$= \frac{2V_m}{T} \left( 0 - 0 + \frac{\cos n\omega_0 t}{(n\omega_0)^2} \Big|_0^{T/2} - 0 + 0 - 2\pi \frac{\cos n\omega_0 t}{(n\omega_0)^2} \Big|_{T/2}^T \right)$$

$$= \frac{2V_m}{T(n\omega_0)^2} - \frac{\cos n\omega_0 t}{(n\omega_0)^2} \Big|_{T/2}^T + 0 - 0$$

$$= \frac{2V_m}{T(n\omega_0)^2} (\cos n\pi - 1 - \cos n2\pi + \cos n\pi)$$


$$= \frac{2V_m}{T(n\omega_0)^2} 2(\cos n\pi - 1)$$

$$= \begin{cases} 0, & \text{for even } n \\ -\frac{2V_m}{\pi^2 n^2}, & \text{for odd } n \end{cases}$$

and b

$$b_n = 0, \text{ for all } n$$

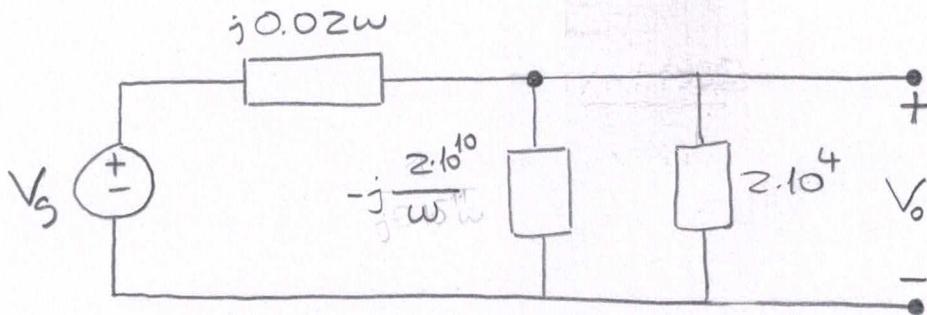-using phasor domain approach allows to get



$$-\frac{-j \frac{2 \cdot 10^{10}}{\omega}}{2 \cdot 10^4} \parallel 2 \cdot 10^4 \Rightarrow \frac{-j \frac{4 \cdot 10^{14}}{\omega}}{-j \frac{2 \cdot 10^{10}}{\omega} + 2 \cdot 10^4} = \frac{-j 4 \cdot 10^{14}}{2 \cdot 10^4 \omega - j 2 \cdot 10^{10}}$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{-j 4 \cdot 10^{14} / (2 \cdot 10^4 \omega - j 2 \cdot 10^{10})}{j \cdot 0.02\omega - \frac{j 4 \cdot 10^{14}}{2 \cdot 10^4 \omega - j 2 \cdot 10^{10}}}$$

$$= \frac{-j 4 \cdot 10^{14}}{j \cdot 0.02\omega (2 \cdot 10^4 \omega - j 2 \cdot 10^{10}) - j 4 \cdot 10^{14}}$$

$$= \frac{-j 4 \cdot 10^{14}}{j 4 \cdot 10^2 \omega^2 + 4 \cdot 10^8 \omega + j 4 \cdot 10^{14} \omega}$$

$$= \frac{-10^{12}}{\omega^2 - j 10^6 \omega - 10^{12}}$$

$$\triangleq H(\omega)$$

Hence;

$$H(1 \cdot 10^6) = \frac{-10^{12}}{10^{12} - j \cdot 10^{12} - 10^{12}} = -j = 1 \angle -90^\circ$$

$$H(3 \cdot 10^6) = \frac{-10^{12}}{9 \cdot 10^{12} - j 3 \cdot 10^{12} - 10^{12}} = \frac{-1}{8 - j 3}$$

$$= -0.1056 - j 0.0411$$

$$= 0.1170 \angle -159.4440^\circ$$

$$H(5 \cdot 10^6) = \frac{-10^{12}}{25 \cdot 10^{12} - j 5 \cdot 10^{12} - 10^{12}} = \frac{-1}{24 - j 5}$$

$$= -0.0399 - j 0.0083$$

$$= 0.0408 \angle -168.2317^\circ$$

and

$$H(0) = \frac{-10^{12}}{0 - 0 - 10^{12}} = 1$$

$$a_1 = -\frac{200}{\pi^2} = -20.2642 \Rightarrow V_{S1} = -20.2642 + j \cdot 0 = 20.2642 \angle 180^\circ$$

$$a_3 = -\frac{200}{9\pi^2} = -2.2516 \Rightarrow V_{S3} = -2.2516 + j \cdot 0 = 2.2516 \angle 180^\circ$$

$$a_5 = -\frac{200}{25\pi^2} = -0.8106 \Rightarrow V_{S5} = -0.8106 + j \cdot 0 = 0.8106 \angle 180^\circ$$

$$a_7 = -\frac{200}{49\pi^2} = -0.4136 \Rightarrow V_{S7} = -0.4136 + j \cdot 0 = 0.4136 \angle 180^\circ$$

Hence;

$$V_o(t) = 25 + 20.2642 \cos(10^6 t + 90^\circ) - 0.2634 \cos(3 \cdot 10^6 t - 159.4440^\circ) - 0.0331 \cos(5 \cdot 10^6 t - 168.2317^\circ) - \dots$$

- it appears that only the first four terms are effective in the rms value of  $v_0(t)$

That is ;

$$V_{\text{rms}} = \sqrt{25^2 + \frac{1}{2} (20.264^2 + 0.2634^2 + 0.0331^2)}$$
$$= 28.8159 \text{ V (rms)}$$

As a result ;

$$P_{\text{av}} = \frac{\frac{28.8159^2}{2}}{2 \cdot 10^4} = 0.0415 \text{ W}$$

**Problem 4)** The voltage and current at the terminals of a network are

$$v = 80 + 200 \cos(500t + 45) + 60 \sin 1500t \text{ V}$$

$$i = 10 + 6 \sin(500t + 75) + 3 \cos(1500t + 30) \text{ A}$$

The current is in the direction of the voltage drop across the terminals.

- What is the average power at the terminals?
- What is the rms value of the voltage?
- What is the rms value of the current?

**Solution:** a. We shall rewrite  $v$  and  $i$  in Fourier series representation of trigonometric form as

$$v = 80 + 200 \cos(500t + 45) + 60 \cos(1500t - 90)$$

$$i = 10 + 6 \cos(500t - 15) + 3 \cos(1500t + 30)$$

-we know that

$$P = V_{dc} I_{dc} + \frac{1}{2} \sum_{n=1}^{\infty} V_n I_n \cos(\theta_{vn} - \theta_{in})$$
$$= 80 \cdot 10 + \frac{1}{2} \left( 200 \cdot 6 \cos(60) + 60 \cdot 3 \cos(-120) \right)$$
$$= 800 + \frac{1}{2} (600 - 50)$$
$$= 1055 \text{ W}$$

b.


$$V_{rms} = \sqrt{80^2 + \left(\frac{200}{\sqrt{2}}\right)^2 + \left(\frac{60}{\sqrt{2}}\right)^2}$$

$$= 167.9286 \text{ V}$$

c.

$$I_{rms} = \sqrt{10^2 + \left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{3}{\sqrt{2}}\right)^2}$$
$$= \sqrt{100 + 22.5}$$
$$= 11.0680 \text{ A}$$

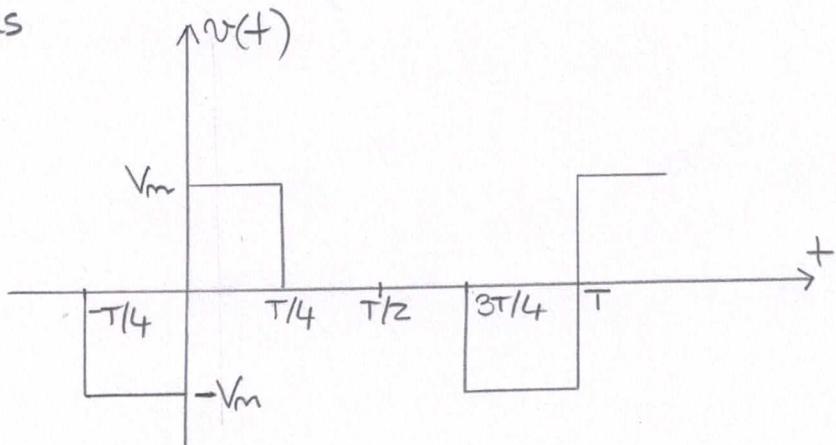Problem 5) Use the exponential form of the Fourier series to write an expression for the voltage shown as



Solution. We shall write

$$v(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t}, \quad \omega_0 = \frac{2\pi}{T}$$

with

$$C_n = \frac{1}{T} \int_{-T/4}^{3T/4} v(t) e^{-jn\omega_0 t} dt, \quad n \neq 0$$
$$= \frac{1}{T} \left[ \int_0^{T/4} V_m e^{-jn\omega_0 t} dt + \int_{-T/4}^0 (-V_m) e^{-jn\omega_0 t} dt \right]$$
$$= \frac{V_m}{T} \left( \frac{e^{-jn\omega_0 t}}{-jn\omega_0} \Big|_0^{T/4} - \frac{e^{-jn\omega_0 t}}{-jn\omega_0} \Big|_{-T/4}^0 \right)$$
$$= \frac{V_m}{-jn2\pi} \left( e^{-jn\frac{\pi}{2}} - 1 - 1 + e^{jn\frac{\pi}{2}} \right)$$

$$= -\frac{V_m}{jn2\pi} \left( 2\cos \frac{n\pi}{2} - 2 \right)$$

$$= -\frac{V_m}{jn\pi} \left( 1 - \cos \frac{n\pi}{2} \right)$$

and

$$C_0 = \frac{1}{T} \int_{-T/4}^{3T/4} v(t) dt$$
$$= \frac{1}{T} \left( \int_0^{T/4} V_m dt + \int_{-T/4}^0 (-V_m) dt \right)$$
$$= \frac{V_m}{T} \left( \frac{T}{4} \Big|_0^{T/4} - \frac{T}{4} \Big|_{-T/4}^0 \right)$$
$$= \frac{V_m}{T} \left( \frac{T}{4} - 0 - 0 + \frac{T}{4} \right)$$
$$= 0$$

Hence;

$$C_n = \begin{cases} 0, & \text{if } n \text{ is odd or zero} \\ \frac{V_m}{jn\pi} [1 - (-1)^{n/2}], & \text{if } n \text{ is even} \end{cases}$$

OR a result;

$$v(n) = \begin{cases} \frac{2V_m}{jn\pi} & \text{if } n \text{ is even but } \frac{n}{2} \text{ is odd} \\ 0 & \text{else} \end{cases}$$

As a result;

$$\begin{aligned} v(t) &= \sum_{\substack{n \text{ is even} \\ \frac{n}{2} \text{ is odd}}} \frac{2V_m}{jn\pi} e^{jn\omega_0 t} \\ &= \sum_{\substack{k=1, 3, 5, \dots \\ k=-1, -3, -5, \dots \\ k \neq 0}} \frac{2V_m}{j2k\pi} e^{j2k\omega_0 t} \end{aligned}$$