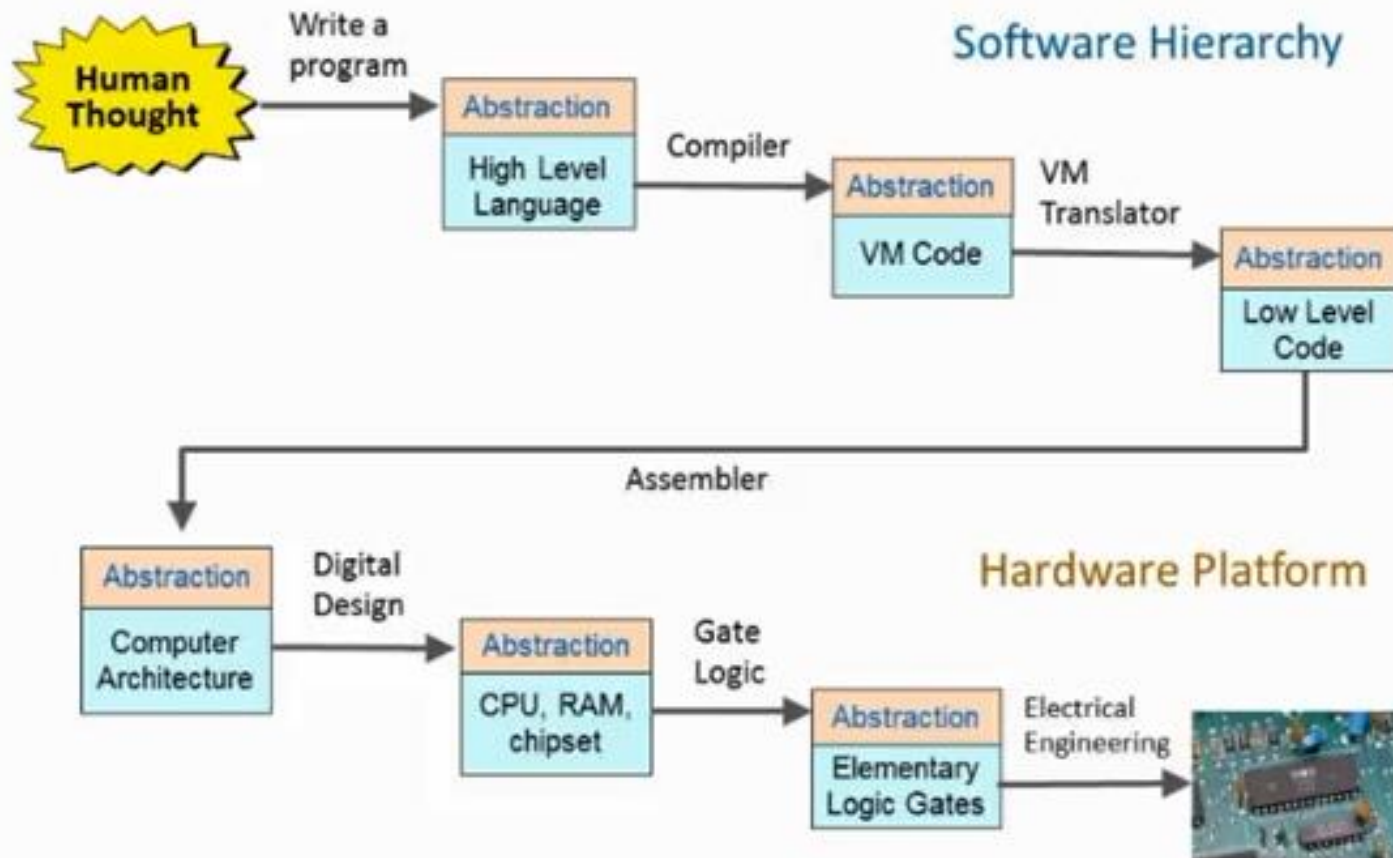


Computer Architecture

Big Picture


NAND TO APPS

Nand to Tetris: the big picture



NAND TO APPS

Nand to Tetris: the big picture

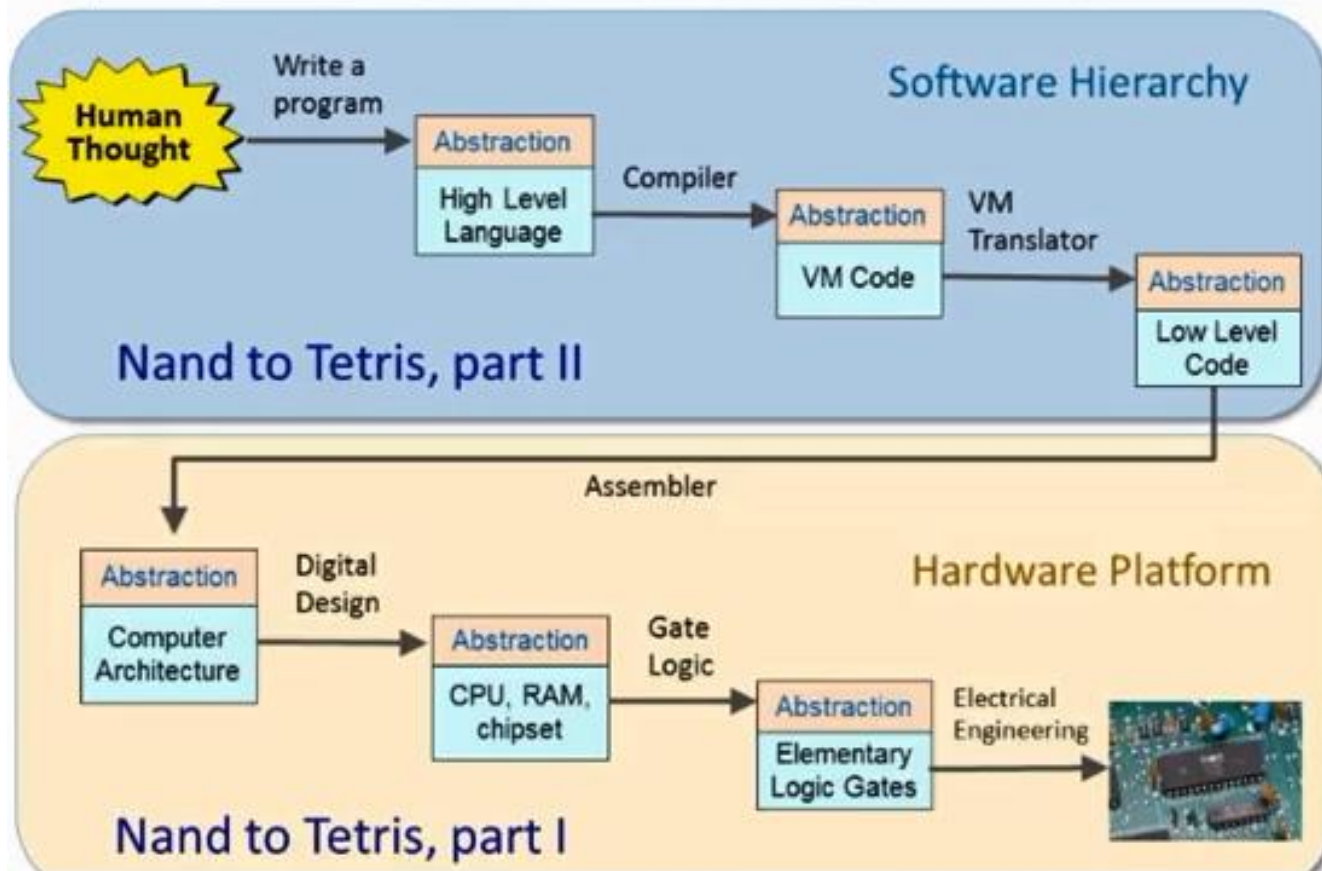

Hello World

```
// First Example in Programming 101
Class Main {
    function void main() {
        do Output.printString("Hello World!");
        do Output.println(); // New line
        return;
    }
}
```

How do these letters do anything?


```
// First Example in Programming 101
Class Main {
    function void main() {
        do Output.printString("Hello World!");
        do Output.println(); // New line
        return;
    }
}
```

p
112

r
114

i
105

Nand to Tetris, Part I

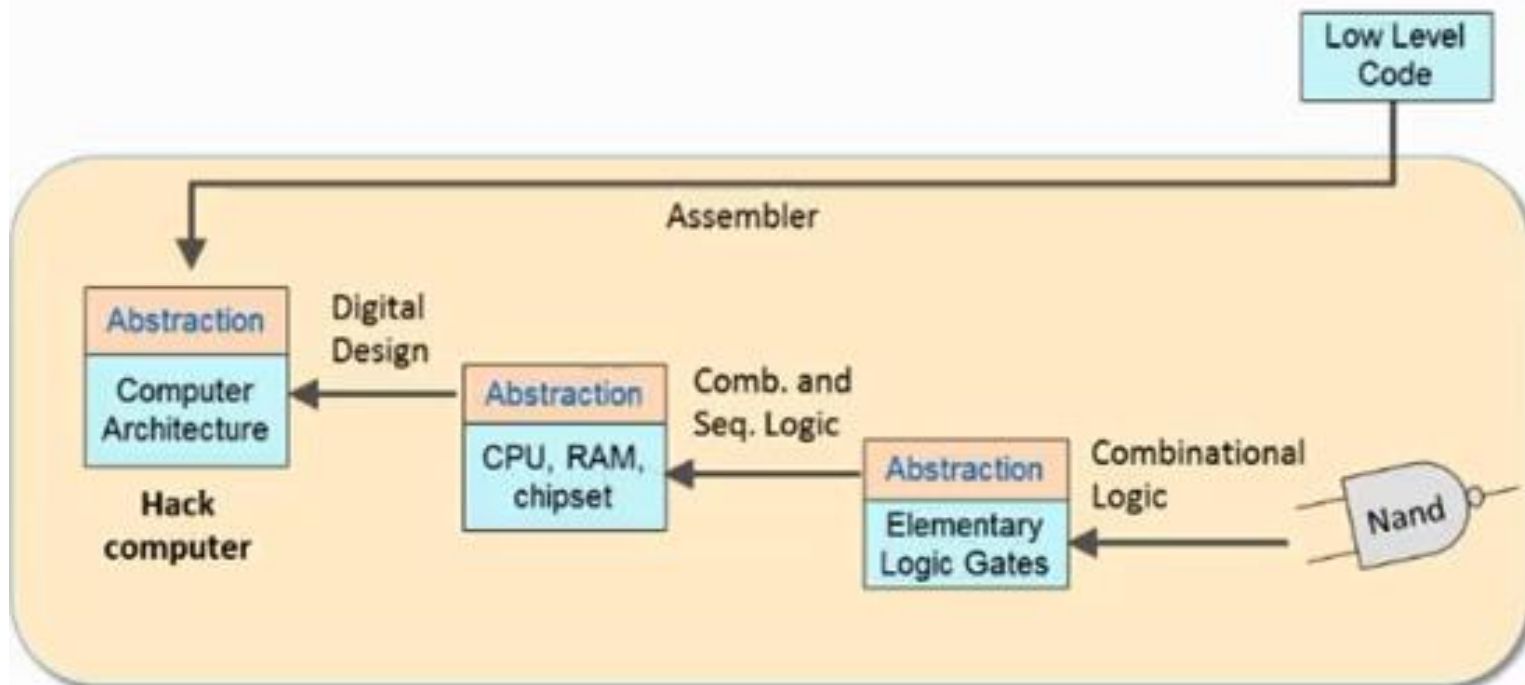

Hardware Part

Building a chip: design


chip abstraction

Xor: outputs 1 if exactly one of its inputs is 1, otherwise outputs 0.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0




chip diagram

 

Hardware Part

Building a chip: design

chip diagram

 

specify

HDL program

```
CHIP Xor {
  IN a, b;
  OUT out;

  PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aandnotb);
    And (a=nota, b=b, out=notaandb);
    Or (a=aandnotb, b=notaandb, out=out);
}
```

 

Nand to Tetris, Part I

You have built a complete functioning computer

- That can run anything including games like Tetris
- Using only modest Nand gates



a	b	Nand
0	0	1
0	1	1
1	0	1
1	1	0



Low level languages

Programming at the end of Part I: Hack

Hack assembly code (source language)

```
// Computes RAM[1]=1+...+RAM[0]
@i
M=1    // i = 1
@sum
M=0    // sum = 0

(LOOP)
@i      // if i>RAM[0] goto STOP
D=M
@R0
D=D-M
@STOP
D;JGT
@i      // sum += i
D=M
@sum
M=D+M
@i      // i++
M=M+1
@LOOP  // goto LOOP
0;JMP
...
```

Hack binary code

```
0000000000010000
1110111111001000
0000000000010001
1110101010001000
0000000000010000
1111110000010000
0000000000000000
1111010011010000
0000000000010010
1110001100000001
0000000000010000
1111110000010000
0000000000010001
1111000010001000
0000000000010000
1111110111001000
0000000000000100
1110101010000111
...
```

- How can we construct hardware units for basic operations?

Boolean Logic

Boolean Values



F

T

N

Y

0

1

Boolean Operation

(x AND y)

$x \wedge y$

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

(x OR y)

$x \vee y$

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

NOT(x)

$\neg x$

x	NOT
0	1
1	0

$$\text{NOT}(0 \text{ OR } (1 \text{ AND } 1)) = \text{NOT}(0 \text{ OR } 1) = \text{NOT}(1) = 0$$

Boolean Identities

Boolean Identities

- $(x \text{ AND } y) = (y \text{ AND } x)$
 - $(x \text{ OR } y) = (y \text{ OR } x)$
 - $(x \text{ AND } (y \text{ AND } z)) = ((x \text{ AND } y) \text{ AND } z)$
 - $(x \text{ OR } (y \text{ OR } z)) = ((x \text{ OR } y) \text{ OR } z)$
 - $(x \text{ AND } (y \text{ OR } z)) = (x \text{ AND } y) \text{ OR } (x \text{ AND } z)$
 - $(x \text{ OR } (y \text{ AND } z)) = (x \text{ OR } y) \text{ AND } (x \text{ OR } z)$
 - $\text{NOT}(x \text{ AND } y) = \text{NOT}(x) \text{ OR } \text{NOT}(y)$
 - $\text{NOT}(x \text{ OR } y) = \text{NOT}(x) \text{ AND } \text{NOT}(y)$
- Commutative Laws
- Associative Laws
- Distributive Laws
- De Morgan Laws

De Morgans Teorem

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

- ◆ Example: Find the complement of $Z = A'B'C + A'BC + AB'C + ABC'$

$$\begin{aligned}
 Z' &= (A'B'C + A'BC + AB'C + ABC')' \\
 &= (A'B'C)' \cdot (A'BC)' \cdot (AB'C)' \cdot (ABC')' \\
 &= (A+B+C') \cdot (A+B'+C') \cdot (A'+B+C') \cdot (A'+B'+C)
 \end{aligned}$$

Boolean Algebra

- Simplifying boolean expression via boolean algebra

Boolean Algebra

$$\begin{aligned} & \text{NOT}(\text{NOT}(x) \text{ AND } \text{NOT}(x \text{ OR } y)) = \\ & \text{NOT}(\text{NOT}(x) \text{ AND } (\text{NOT}(x) \text{ AND } \text{NOT}(y))) = \\ & \text{NOT}((\text{NOT}(x) \text{ AND } \text{NOT}(x)) \text{ AND } \text{NOT}(y)) = \\ & \text{NOT}(\text{NOT}(x) \text{ AND } \text{NOT}(y)) = \\ & \text{NOT}(\text{NOT}(x)) \text{ OR } \text{NOT}(\text{NOT}(y)) = \\ & x \text{ OR } y \end{aligned}$$

Double Negation

- Same conclusion with truth table..

Boolean Algebra

$\text{NOT}(\text{NOT}(x) \text{ AND } \text{NOT}(x \text{ OR } y)) =$

x	y	
0	0	0
0	1	1
1	0	1
1	1	1


$= x \text{ OR } y$

Boolean Function

Boolean Functions

$$f(x, y, z) = (x \text{ AND } y) \text{ OR } (\text{NOT}(x) \text{ AND } z)$$

x	y	z	f
0	0	0	
0	0	1	1
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

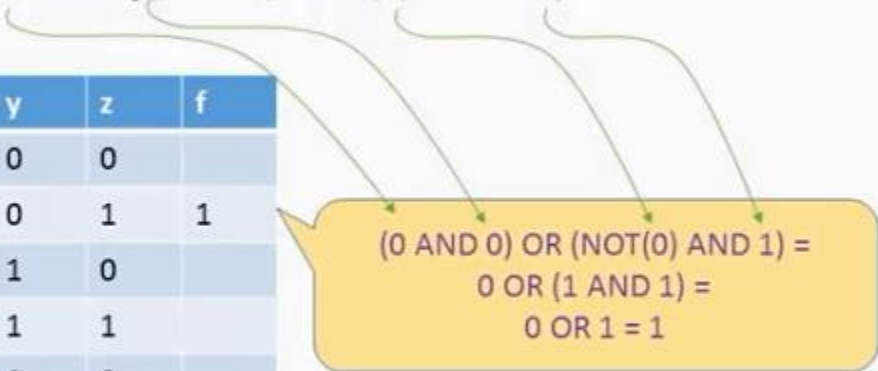

$(0 \text{ AND } 0) \text{ OR } (\text{NOT}(0) \text{ AND } 1) =$
 $0 \text{ OR } (1 \text{ AND } 1) =$
 $0 \text{ OR } 1 = 1$

Boolean Function

Boolean Functions

$$f(x, y, z) = (x \text{ AND } y) \text{ OR } (\text{NOT}(x) \text{ AND } z)$$

Formula

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Truth table

Truth Table to Boolean Expression

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

(NOT(x) AND NOT(y) AND NOT(z))

OR

(NOT(x) AND y AND NOT(z))

OR

(x AND NOT(y) AND NOT(z))

- Finding the shortest expression NP hard problem

Truth Table to Boolean Expression

$(\text{NOT}(x) \text{ AND } \text{NOT}(y) \text{ AND } \text{NOT}(z))$

OR

$(\text{NOT}(x) \text{ AND } y \text{ AND } \text{NOT}(z))$

OR

$(x \text{ AND } \text{NOT}(y) \text{ AND } \text{NOT}(z))$

=

$(\text{NOT}(x) \text{ AND } \text{NOT}(z)) \text{ OR } (x \text{ AND } \text{NOT}(y) \text{ AND } \text{NOT}(z))$

=

$(\text{NOT}(x) \text{ AND } \text{NOT}(z)) \text{ OR } (\text{NOT}(y) \text{ AND } \text{NOT}(z))$

=

$\text{NOT}(z) \text{ AND } (\text{NOT}(x) \text{ OR } \text{NOT}(y))$

Theorem

Any Boolean function can be represented using an expression containing AND, OR and NOT operations.

Theorem

Any Boolean function can be represented using an expression containing AND and NOT operations.

Proof:

$$(x \text{ OR } y) = \text{NOT}(\text{NOT}(x) \text{ AND } \text{NOT}(y))$$

Question

What would be the logical equivalent of $\text{NAND}(x,x)$?

Remember $\text{NAND}(x,x)$ is defined to be $\text{NOT}(x \text{ AND } x)$. Here is the truth table.

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

- ☐ x
- ☐ $\text{OR}(x,x)$
- ☐ $\text{AND}(x,x)$
- ☐ $\text{NOT}(x)$

Theorem

Any Boolean function can be represented using an expression containing only NAND operations.

Proof:

$$1) \text{ NOT}(x) = (x \text{ NAND } x)$$

$$2) (x \text{ AND } y) = \text{NOT}(x \text{ NAND } y)$$


$$3) (x \text{ OR } y) = \text{NOT}(x) \text{ NAND } \text{NOT}(y)$$

Desired AND Gate



$$Q = A \text{ AND } B$$

NAND Construction

 

$$= (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$$

Truth Table


Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

Desired OR Gate



$$Q = A \text{ OR } B$$

NAND Construction

 

$$= (A \text{ NAND } A) \text{ NAND } (B \text{ NAND } B)$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates


- Now we are going from abstract boolean logic to computer parts

Gate Logic

- A technique for implementing Boolean functions using logic gates
- Logic gates:
 - Elementary (Nand, And, Or, Not, ...)
 - Composite (Mux, Adder, ...)

Elementary logic gates: Nand

gate diagram:

 


functional
specification:

if (a==1 and b==1)
then out=0 else out=1


truth table:

a	b	out
0	0	1
0	1	1
1	0	1
1	1	0


Elementary logic gates: And, Or, Not

 
 
```
if (a==1 and b==1)
then out=1 else out=0
```



 
```
if (a==1 or b==1)
then out=1 else out=0
```




```
if (in==0)
then out=1 else out=0
```

Composite gates

 

 
```
if (a==1 and b==1 and c==1)
  then out=1 else out=0
```




Gate Interface / Gate Implementation


gate interface

 

 
```
if (a==1 and b==1 and c==1)
  then out=1 else out=0
```



Circuit implementations

 

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

 

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1

- **HARDWARE DESCRIPTION LANGUAGES**

Hardware Part

Building a chip: design


chip abstraction

Xor: outputs 1 if exactly one of its inputs is 1, otherwise outputs 0.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0




chip diagram

 

Hardware Part

Building a chip: design

chip diagram

 

specify

HDL program

```
CHIP Xor {
  IN a, b;
  OUT out;

  PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aandnotb);
    And (a=nota, b=b, out=notaandb);
    Or (a=aandnotb, b=notaandb, out=out);
}
```

- We can build the chip via using computers

Building a chip: simulation / testing

HDL program + test script

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, out=andab);  
    Or (a=nota, b=notb, out=out);  
}  
  
output-file And.out;  
output-list a b out;  
set a 0, set b 0, eval,  
output;  
set a 0, set b 1, eval,  
output;  
set a 1, set b 0, eval,  
output;  
set a 1, set b 1, eval,  
output;
```




simulate

Hardware Simulator



Design: from requirements to interface

 

outputs 1 if one, and only one, of its inputs, is 1.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Requirement:

Build a gate that delivers this functionality

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {
```

```
  IN a, b;
```


```
  OUT out;
```

```
  PARTS:
```

```
    // Implementation missing
```

```
}
```

 Design: from requirements to gate diagram



outputs 1 if one, and only one, of its inputs, is 1.

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Requirement:

Build a gate that delivers this functionality




General idea:


out=1 when:

a And Not(b)

Or

b And Not(a)

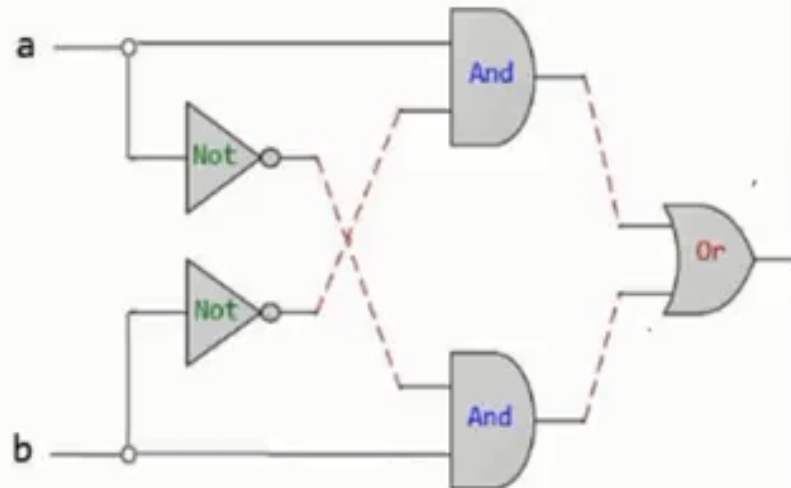

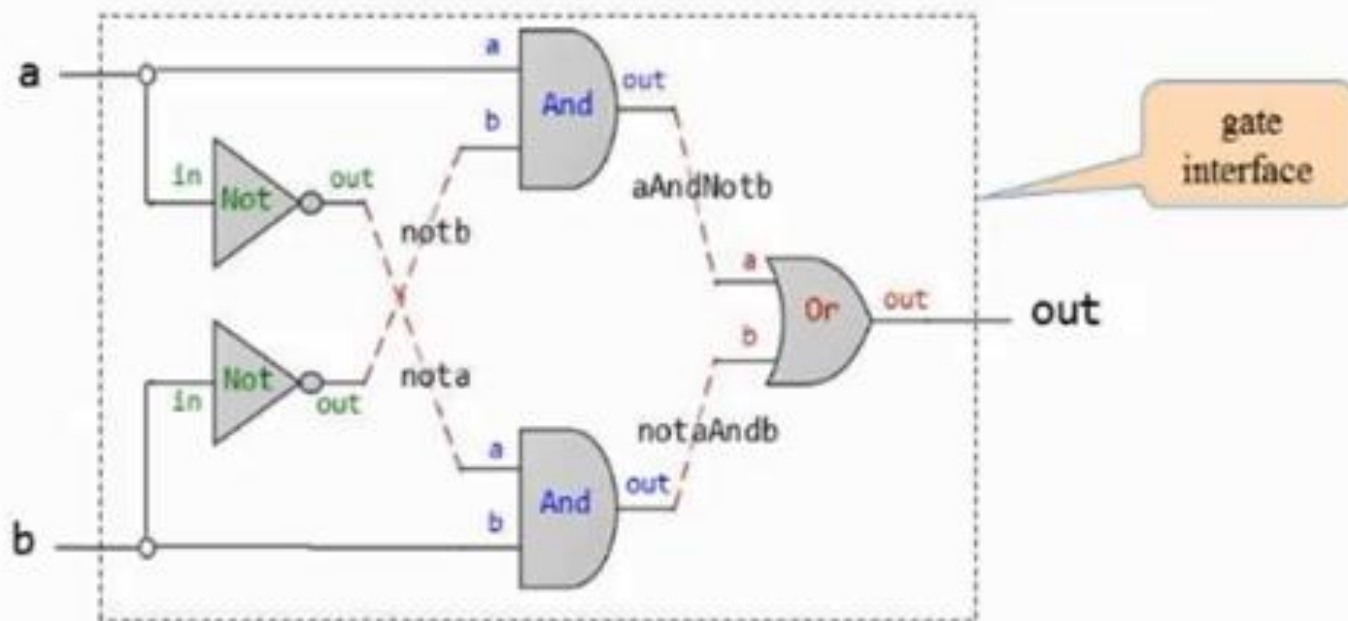

interface

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */
```

```
CHIP Xor {
```

```
  IN a, b;
```

```
  OUT out;
```

```
  PARTS:
```

```
  Not (in=a, out=nota);
```

```
  Not (in=b, out=notb);
```

```
  And (a=a, b=notb, out=aAndNotb);
```


```
  And (a=nota, b=b, out=notaAndb);
```

```
  Or (a=aAndNotb, b=notaAndb, out=out);
```

implementation

```
/** Xor gate: out = (a And Not(b)) Or (Not(a) And b) */
```
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```




- HDL is a functional / declarative language
- The order of HDL statements is insignificant
- Before using a chip part, you must know its interface. For example:
Not(in= ,out=), And(a= ,b= ,out=), Or(a= ,b= ,out=)

Hardware simulation in a nutshell



simulate

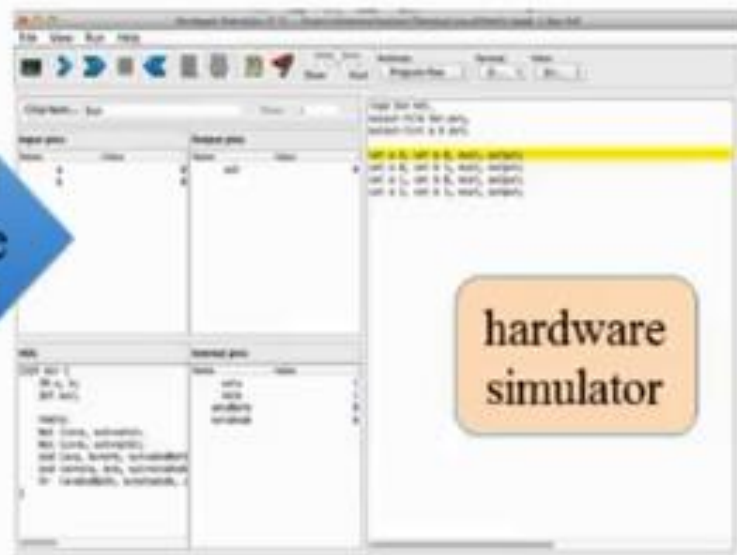


Simulation options:

- Interactive

Interactive simulation (using Xor as an example)

Xor.hdl
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=aAndNotb);  
    And (a=nota, b=b, out=notaAndb);  
    Or (a=aAndNotb, b=notaAndb, out=out);  
}
```



Simulation process:

- Load the HDL file into the hardware simulator
- Enter values (0's and 1's) into the chip's input pins (e.g. a and b)
- Evaluate the chip's logic
- Inspect the resulting values of:
 - The output pins (e.g. out)
 - The internal pins (e.g. nota, notb, aAndNotb, notaAndb)

Interactive simulation

Hardware Simulator (2.5) - /Users/shimonschocken/Desktop/nand2tetris/week 1/Xor.hdl

File View Run Help

Chip Name: Xor

2. evaluate the chip logic

1. manipulate input pins

Input pins		Output pins	
Name	Value	Name	Value
a	0	out	1
b	1		

HDL

```
CHIP Xor {
  IN a, b;
  OUT out;

  PARTS:
    Not (in=a, out=nota);
    Not (in=b, out=notb);
    And (a=a, b=notb, out=aAndNotb);
    And (a=nota, b=b, out=notaAndb);
    Or (a=aAndNotb, b=notaAndb, out=out);
}
```

Internal pins

Name	Value
nota	1
notb	0
aAndNotb	0
notaAndb	1

HDL code

Main Parts of CPU

- A basic 16 bit computer processing unit has following parts:


<u>Elementary logic gates</u>	<u>16-bit variants</u>	<u>Multi-way variants</u>
▢ Not	▢ Not16	▢ Or8Way
▢ And	▢ And16	▢ Mux4Way16
▢ Or	▢ Or16	▢ Mux8Way16
▢ Xor	▢ Mux16	▢ DMux4Way
▢ Mux		▢ DMux8Way
▢ DMux		

Implement Function via Basic Gates

- In a **decoder** when we give 0,0,0 to the input the first output becomes 1 the others become 0; when we give 0,0,1 to the input the first output becomes 1 the others become 1; it goes like this...
- Boolean Expressions for outputs:
- $O_7=ABC$; $O_6=ABC'$; $O_5=AB'C$; $O_4=AB'C'$; $O_3=A'BC$; $O_2=A'BC'$; $O_1=A'B'C$; $O_0=A'B'C'$
- The truth table and chip design is below

3 to 8 Decoder – Truth Table




A	B	C	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

2 bit adder

- The boolean expressions of outputs $S = A'B + B'A = A \oplus B$; $C = AB$

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

   

2-bit adder with nand gates

- $S = A'B + AB' = \text{XOR } B$; $C = AB$
- we can represent all boolean expressions using NAND

✓ $\text{NOT}(x) = (x \text{ NAND } x)$;

✓ $(x \text{ AND } y) = \text{NOT}(x \text{ NAND } y)$;

✓ $(x \text{ OR } y) = \text{NOT}(x) \text{ NAND } \text{NOT}(y)$

$$A'B = \text{NOT}(A' \text{ NAND } B)$$

$$AB' = \text{NOT}(A \text{ NAND } B')$$

$$A'B + AB' = \text{NOT NOT}(A' \text{ NAND } B) \text{ NAND } \text{NOT NOT}(A \text{ NAND } B')$$

$$A'B + AB' = (A' \text{ NAND } B) \text{ NAND } (A \text{ NAND } B')$$

★ $S = ((A \text{ NAND } A) \text{ NAND } B) \text{ NAND } (A \text{ NAND } (B \text{ NAND } B))$

★ $C = AB = \text{NOT}(A \text{ NAND } B) = (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$

$$S = ((A \text{ NAND } A) \text{ NAND } B) \text{ NAND } (A \text{ NAND } (B \text{ NAND } B))$$

$$C = (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$$

★ Circuit Design with NAND:

 


Figure 1